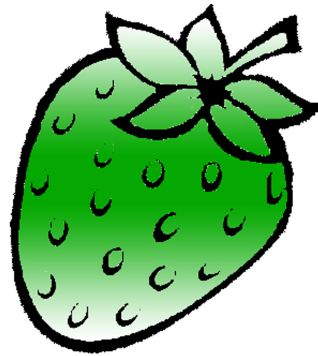


# STRAWBERRY



 /strawberrydevelopers

 /strawberry\_app

*For more visit:*


*Strawberrydevelopers.weebly.com*

# Zener Diode and Zener Voltage Regulator


# Function of Voltage Regulator

Regulated power supply = output dc is constant (stable) at different loads or at varying ac supply conditions

## Zener diode

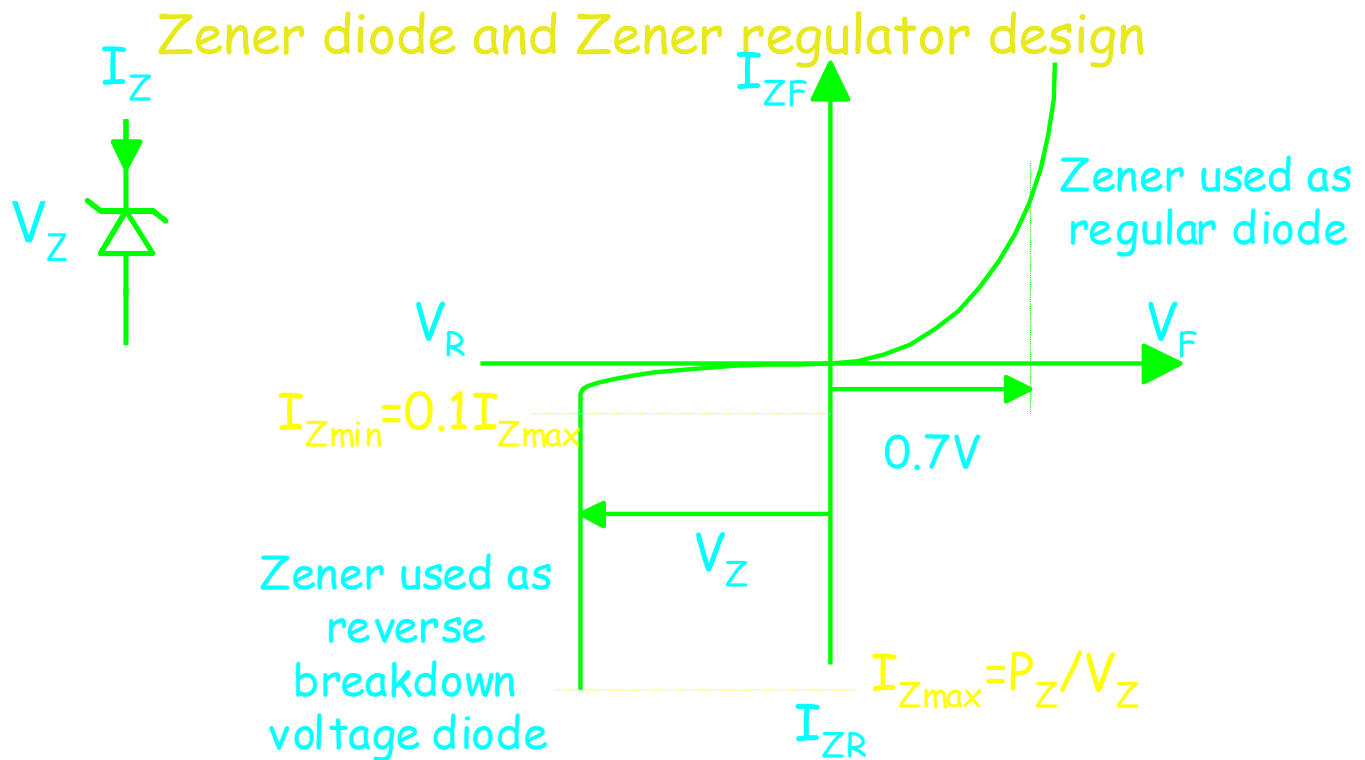

## Zener diode design conditions


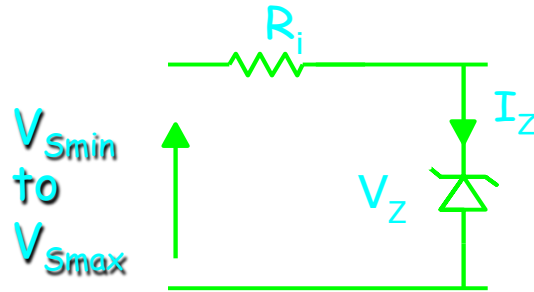


- Whether input voltage is  $V_{Smin}$  or  $V_{Smax}$ , the output voltage will be constant at Zener breakdown voltage  $V_Z$
- Constant output voltage is the regulated output voltage and the circuit is Zener regulator circuit.
- Zener current will become less  $I_{Zmin}$  at  $V_{Smin}$  and it will increase to  $I_{Zmax}$  at  $V_{Smax}$
- Minimum Zener current  $I_{Zmin}$  should not be less than 10%  $I_{Zmax}$  to maintain constant  $V_Z$
- Maximum Zener current  $I_{Zmax}$  should not be more than  $P_Z/V_Z$  not to burn the Zener diode


# Basic Zener Regulator

- If  $V < V_Z$
- The Zener diode is "off" else the Zener diode is "on"

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

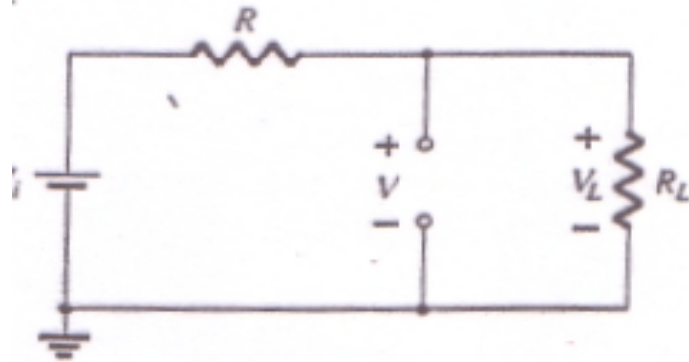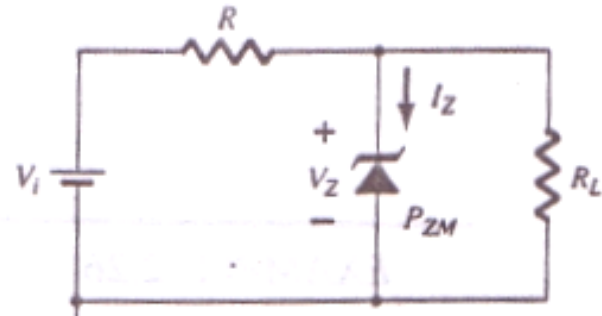

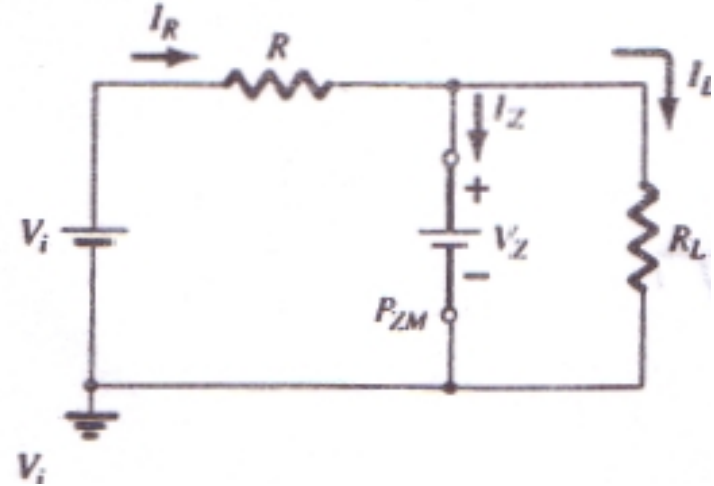- If  $V > V_Z$
- If the Zener is on
- Then  $V_L = V_Z$  (i.e the load voltage is held fixed ' LOCKED ' to the zener voltage  $V_Z$ )
- $I_Z = I_R - I_L$




**NOTE :**

The maximum power dissipation for the zener diode is fixed and given by,


$$P_D = V_Z I_{Z \max}$$
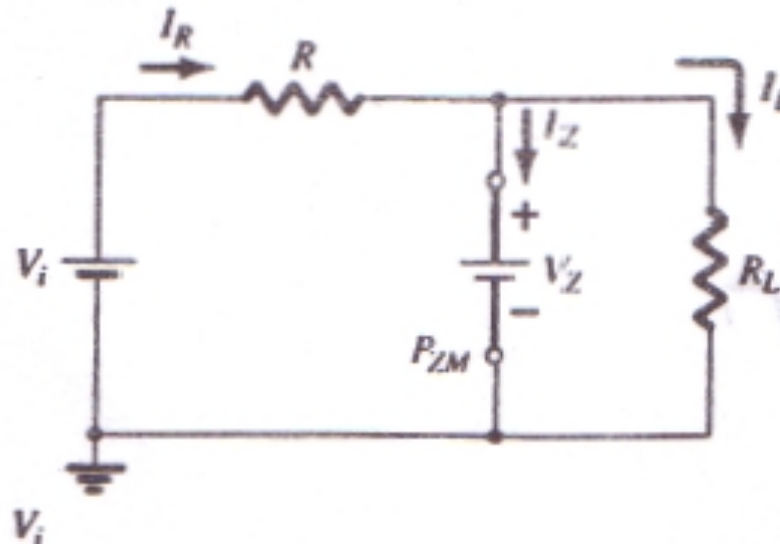
# Working of Zener Regulator under varying $V_{in}$



$V_{in}$ increases	→	$I = I_L + I_Z$ increases	→	$I_L$ is constant ( $V_Z/R_L$ )	→	So $I_Z$ increases ( $I_Z = I - I_L$ )	→	As long $I_Z < I_{Zmax}$ , $V_Z$ is constant i.e. output voltage is constant
$V_{in}$ decreases	→	$I = I_L + I_Z$ decreases	→	$I_L$ is constant ( $V_Z/R_L$ )	→	So $I_Z$ decreases ( $I_Z = I - I_L$ )	→	As long $I_Z > I_{Zmin}$ , $V_Z$ is constant i.e. output voltage is constant
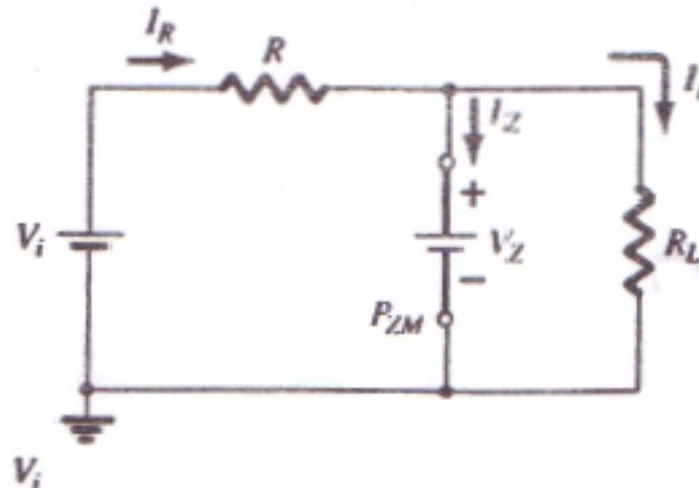
# Working of Zener Regulator under varying Load ( $R_L$ )




$R_L$ increases $I_L$ decreases	$\rightarrow$	$I = \frac{V_{in} - V_Z}{R}$ constant	$\rightarrow$	$I_Z = I - I_L$ $I_Z$ increases	$\rightarrow$	As long $I_Z < I_{Zmax}$ , $V_Z$ is constant i.e. output voltage is constant.
$R_L$ decreases $I_L$ increases	$\rightarrow$	$I = \frac{V_{in} - V_Z}{R}$ constant	$\rightarrow$	$I_Z = I - I_L$ $I_Z$ decreases	$\rightarrow$	As long $I_Z > I_{Zmin}$ , $V_Z$ is constant i.e. output voltage is constant.


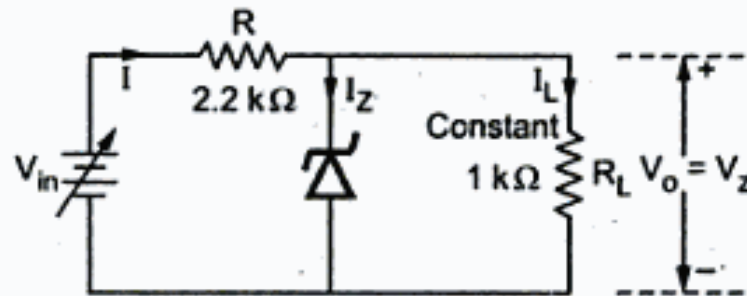
# Problem 1

For a zener regulator shown in the Fig. calculate the range of input voltage for which output will remain constant.


$$V_Z = 6.1V, I_{Zmin} = 2.5 \text{ mA}, I_{Zmax} = 25 \text{ mA}, r_Z = 0 \Omega$$



$$R_L = 1 \text{ k}\Omega, V_Z = 6.1 \text{ V}$$

$$I_L = \frac{V_Z}{R_L} = \frac{6.1}{1 \times 10^3} = 6.1 \text{ mA constant}$$

# Solution Example 1

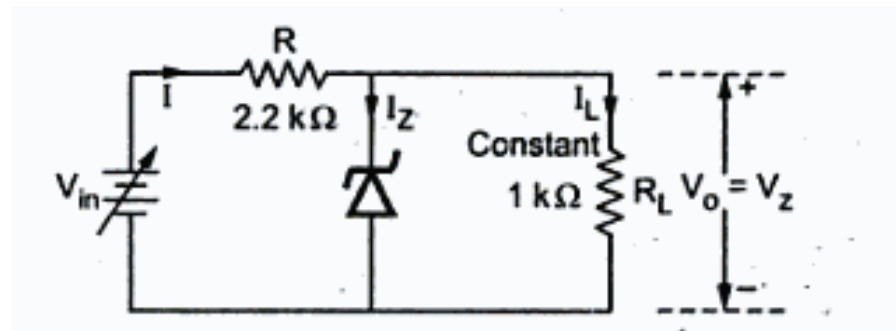

$$\text{For } V_{in(\min)}, \quad I_Z = I_{Z\min} = 2.5 \text{ mA}$$

$$I = I_{Z\min} + I_L = 2.5 + 6.1 = 8.6 \text{ mA}$$

$$V_{in(\min)} = V_Z + IR = 6.1 + 8.6 \times 10^{-3} \times 2.2 \times 10^3 = 25.02 \text{ V}$$

$$\text{For } V_{in(\max)}, \quad I_Z = I_{Z\max} = 25 \text{ mA}$$


$$I = I_{Z\max} + I_L = 25 + 6.1 = 31.1 \text{ mA}$$

$$\therefore V_{in(\max)} = V_Z + IR = 6.1 + 31.1 \times 10^{-3} \times 2.2 \times 10^3 = 74.52 \text{ V}$$

Thus the range of input voltage is **25.02 V to 74.52 V**, for which output will be constant.
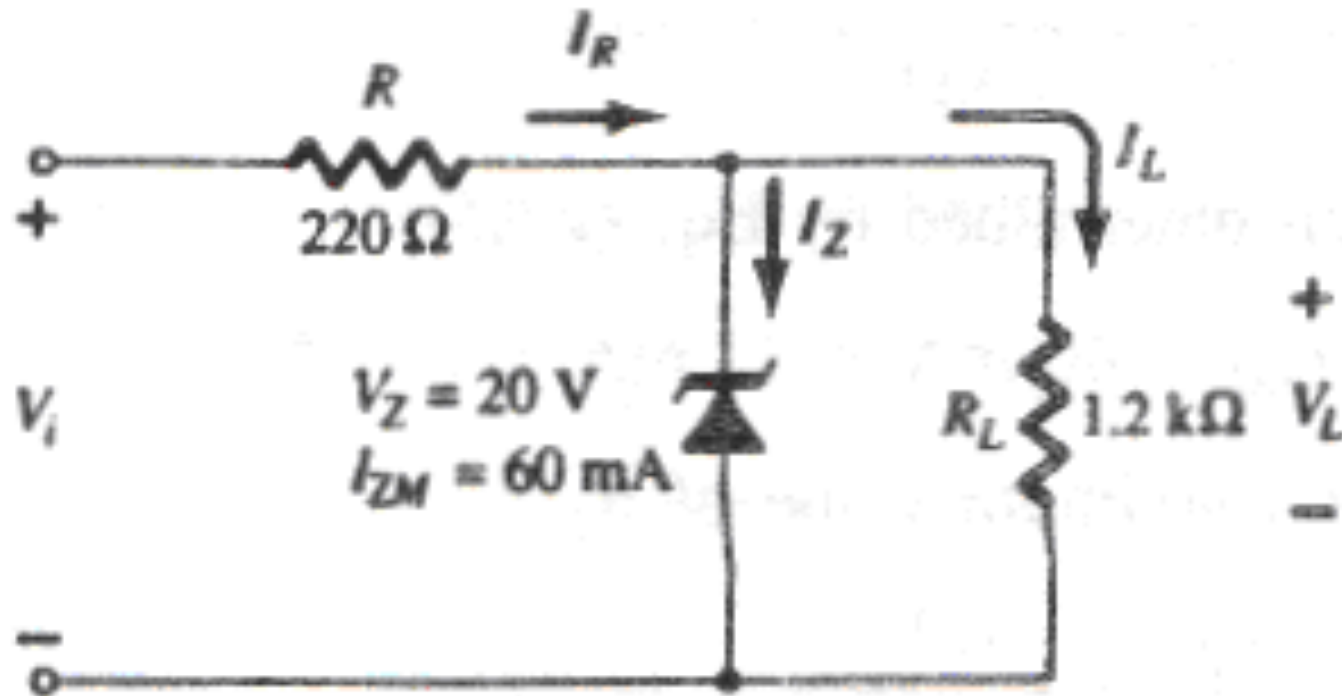
# Example 2

- Determine the range of values of  $V_i$  that will maintain the Zener diode in the "on" state




# Solution - Example 2

If  $V < V_Z$  Zener diode is in Off state

By Voltage Divider Theorem

$$V_Z = V_L = \frac{R_L V_i}{R + R_L}$$

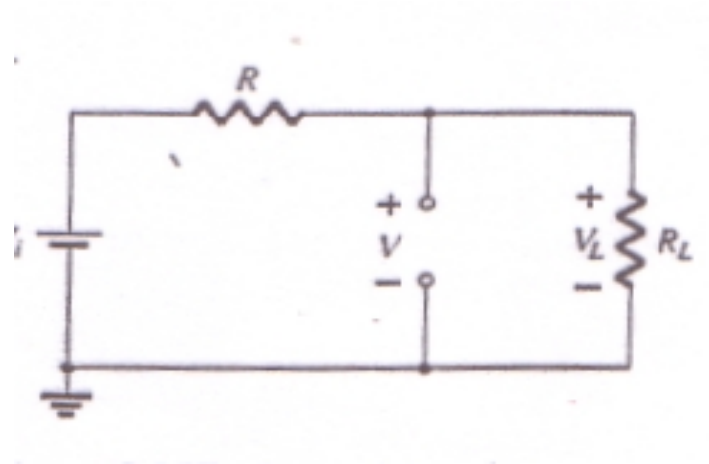


$$V_{i \min} = \frac{(R_L + R)V_Z}{R_L} = 23.67V$$

# Solution (Example 2)

$$I_Z = 60\text{mA}$$

$$V_L = 20\text{V}$$
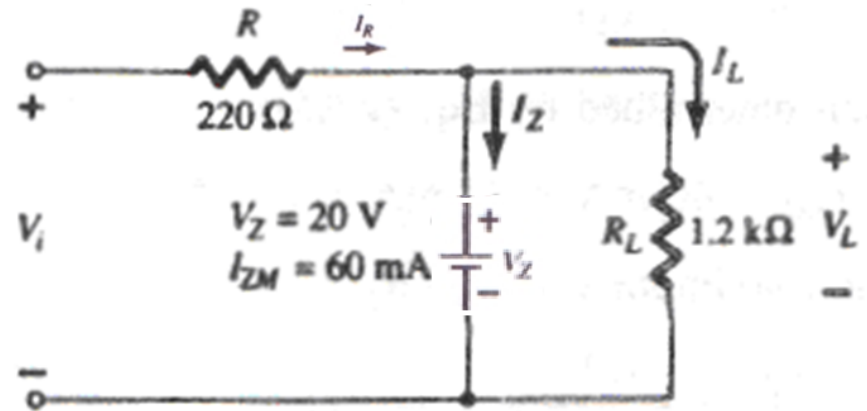
$$\begin{aligned} I_L &= V_L / R_L \\ &= 20 / 1.2\text{K} \\ &= 16.67\text{mA} \end{aligned}$$




$$I_{R_{\max}} = I_{ZM} + I_L = 76.67\text{mA}$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z = 36.87\text{V}$$

# Example 3

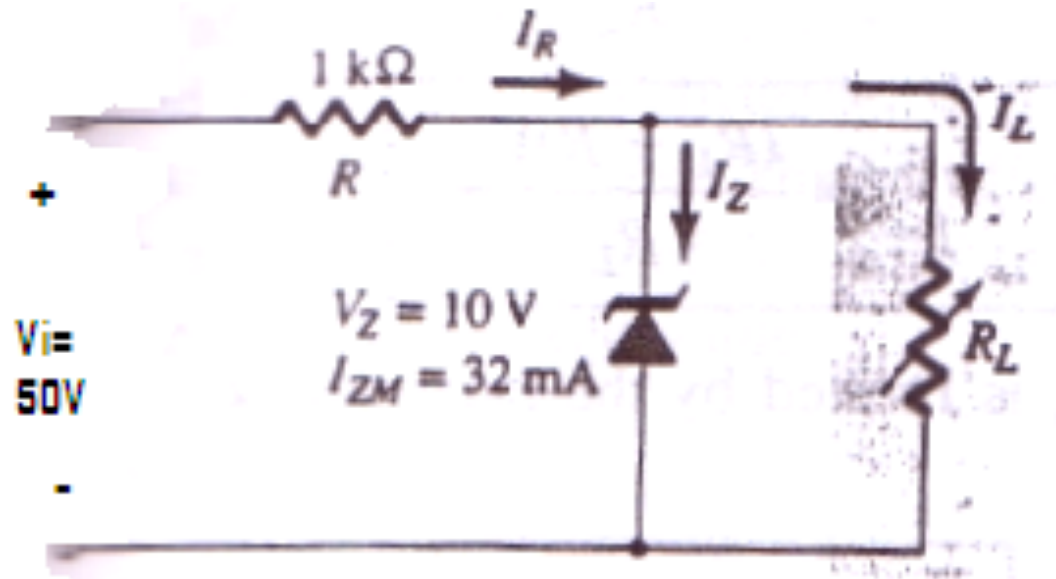- (a) For the network shown, determine the range of  $R_L$  and  $I_L$  that will result in  $V_Z$  being maintained at 50 V
- (b) Determine the maximum wattage rating of the diode



# Solution (Example 3)

$$R_{L\min} = \frac{RV_Z}{V_i - V_Z} = 250\Omega$$


$$V_R = V_i - V_Z = 40V$$

$$I_R = \frac{V_R}{R} = 40mA$$

$$I_{L\min} = I_R - I_{ZM} = 8mA$$



$$R_{L\max} = \frac{V_Z}{I_{L\max}} = 1.25k\Omega$$

$$P_{\max} = V_Z I_{ZM} = 320mW$$

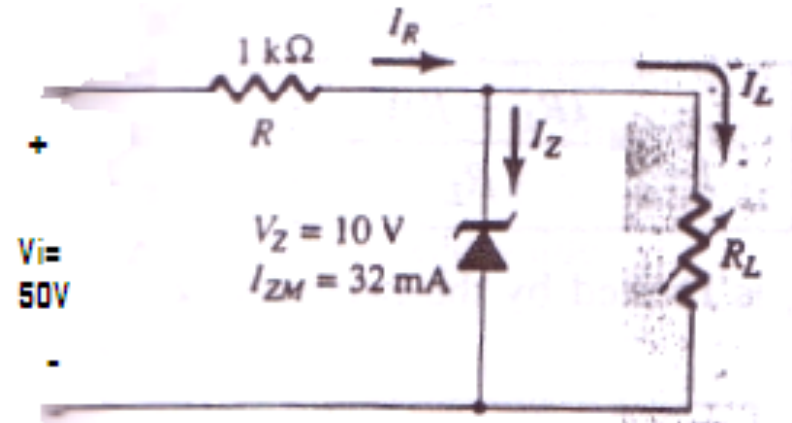

# Analysis for fixed applied DC voltage and load resistor.

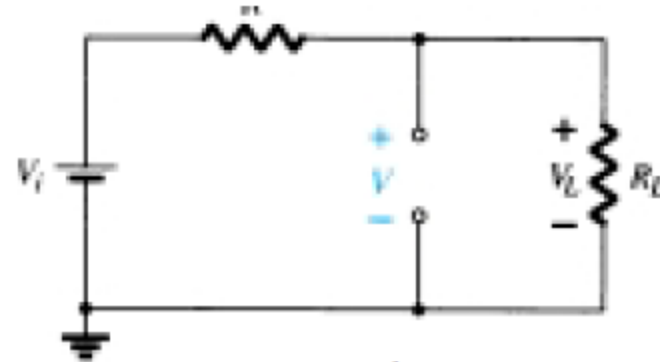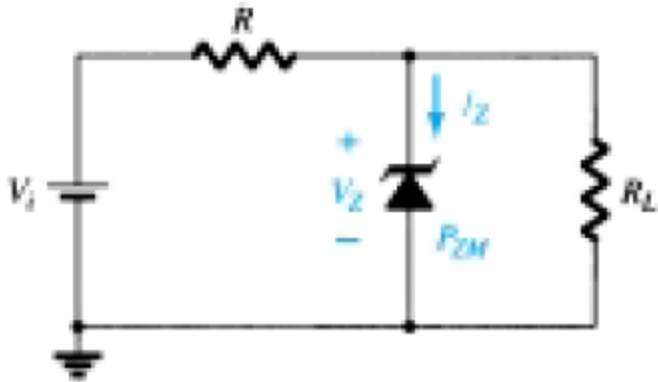1. Determine the state of the Zener diode by removing it from the network and calculating the voltage across the resulting open circuit.



Determining the state of the Zener diode.

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

2. Substitute the appropriate equivalent circuit and solve for the desired unknowns.


If  $V \geq V_Z$ , the Zener diode is “on”

If  $V < V_Z$ , the diode is “off”



# Example 4a

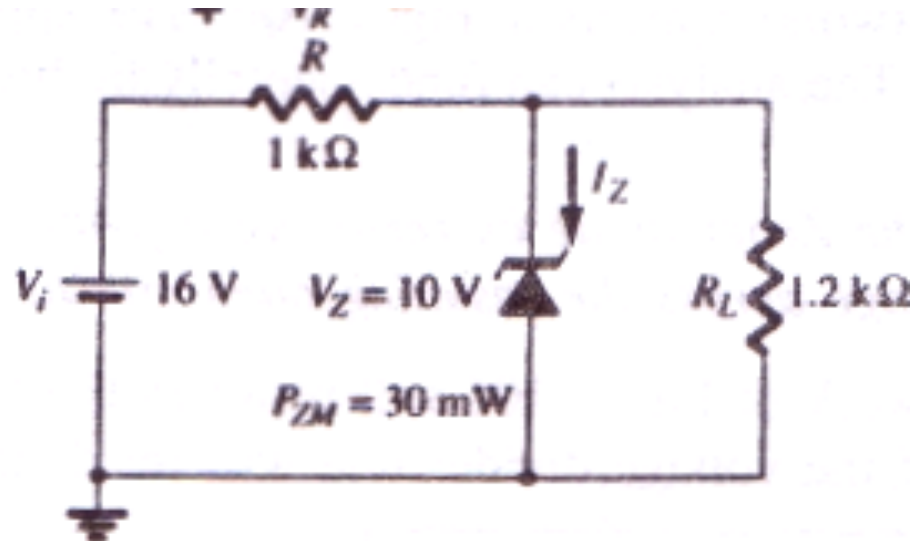- (a) For the Zener diode network shown, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ .
- (b) Repeat part (a) with  $R_L = 3 \text{ k}\Omega$ .



# Solution (Example 4a)

- $$V = \frac{R_L V_i}{R + R_L} = 8.73 \quad V$$


- Since  $V < V_Z$  then the diode is off and the circuit becomes

$$V_L = V = 8.73 \quad V$$

$$V_R = V_i - V_L = 7.27 \quad V$$

$$I_Z = 0 \quad A$$


$$P_Z = V_Z I_Z = 0 \quad W$$

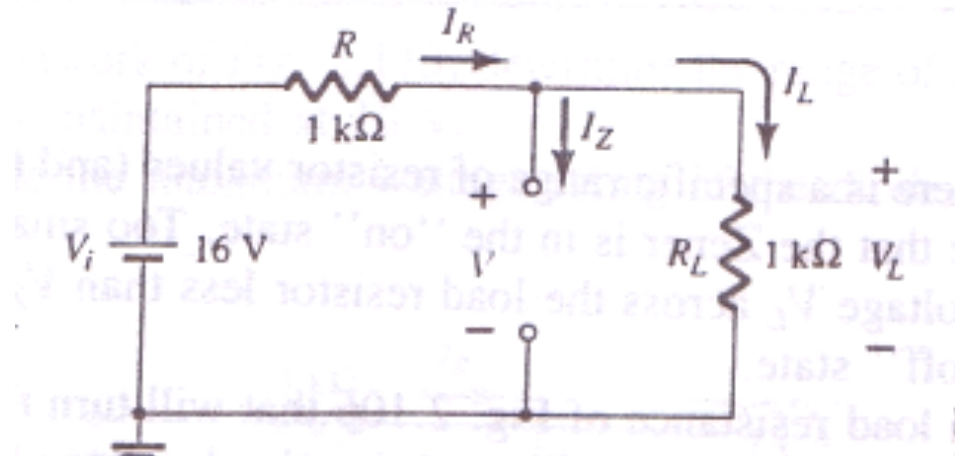
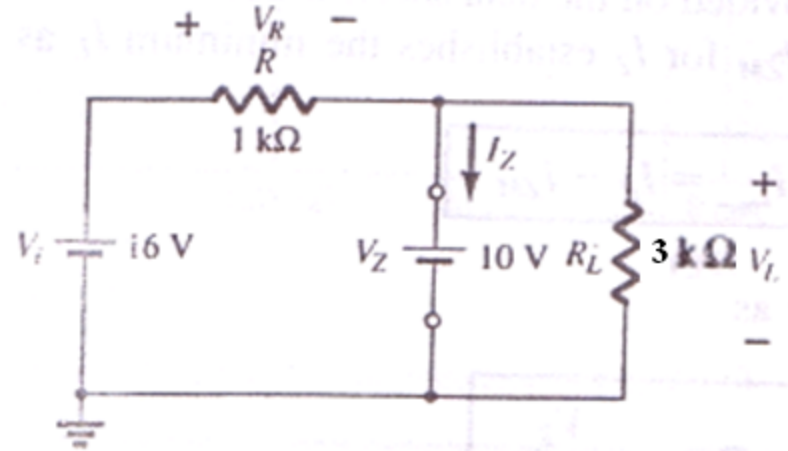
# Solution (Example 4 b)

$$V = \frac{R_L V_i}{R + R_L} = \frac{3 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 12 \text{ V}$$

- **Since  $V > V_Z$**
- **Now the diode is on and the circuit becomes**



# Solution (Example 4 b)


$$V_L = V_Z = 10 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 10 \text{ V} = 6 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{10 \text{ V}}{3 \text{ k}\Omega} = 3.33 \text{ mA}$$

$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$
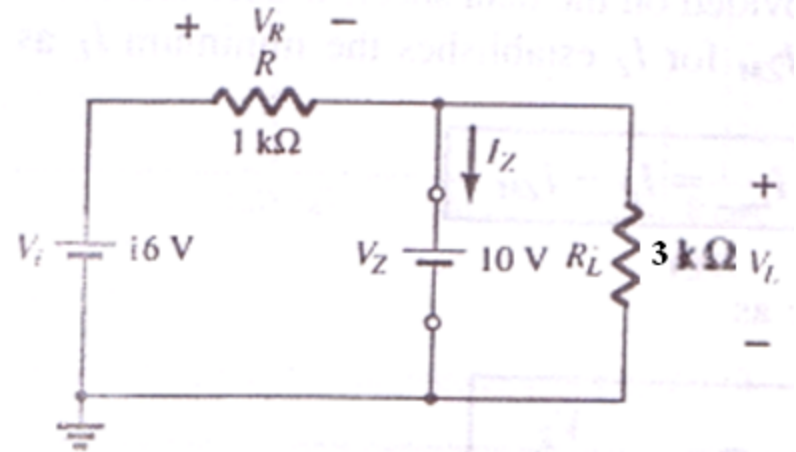
$$\begin{aligned} I_Z &= I_R - I_L \text{ [Eq. (2.18)]} \\ &= 6 \text{ mA} - 3.33 \text{ mA} \\ &= \mathbf{2.67 \text{ mA}} \end{aligned}$$



The power dissipated,

$$P_Z = V_Z I_Z = (10 \text{ V})(2.67 \text{ mA}) = \mathbf{26.7 \text{ mW}}$$

which is less than the specified  $P_{ZM} = 30 \text{ mW}$ .