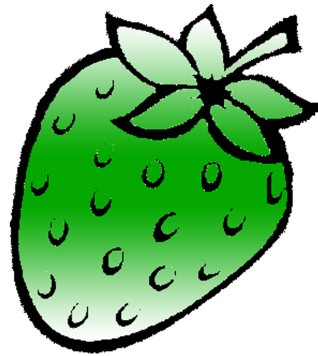


STRAWBERRY



 /strawberrydevelopers

 /strawberry_app


For more visit:

Strawberrydevelopers.weebly.com

Unit 3

The Bipolar Junction Transistor



Bipolar junction transistors (BJTs)

 


Contents

- Basic Bipolar Junction Transistor,
- Transistor Structures (NPN and PNP)
- Modes of Operation
- Symbol and Conventions
- Current Voltage Characteristics
- Non ideal Transistor
- Leakage current
- Breakdown
- DC analysis of transistor circuit
- CE, CB, CC Configurations
- Basic Transistor action as a switch, as an amplifier
- Transistor Biasing
- Bias Stability
- Different Biasing Circuits
- Understanding Manufacturers Specification

 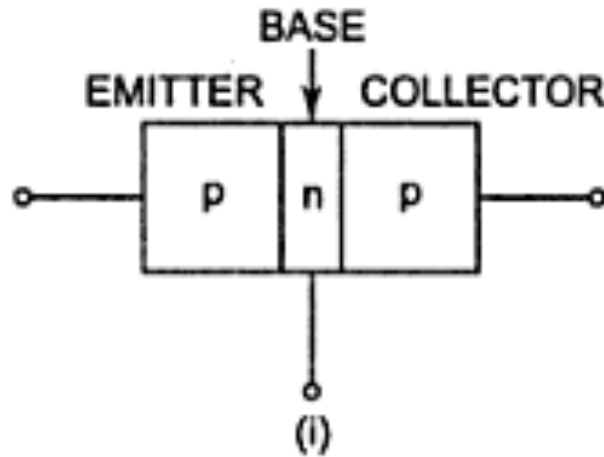
Basic Bipolar Junction Transistor Transistor Structures



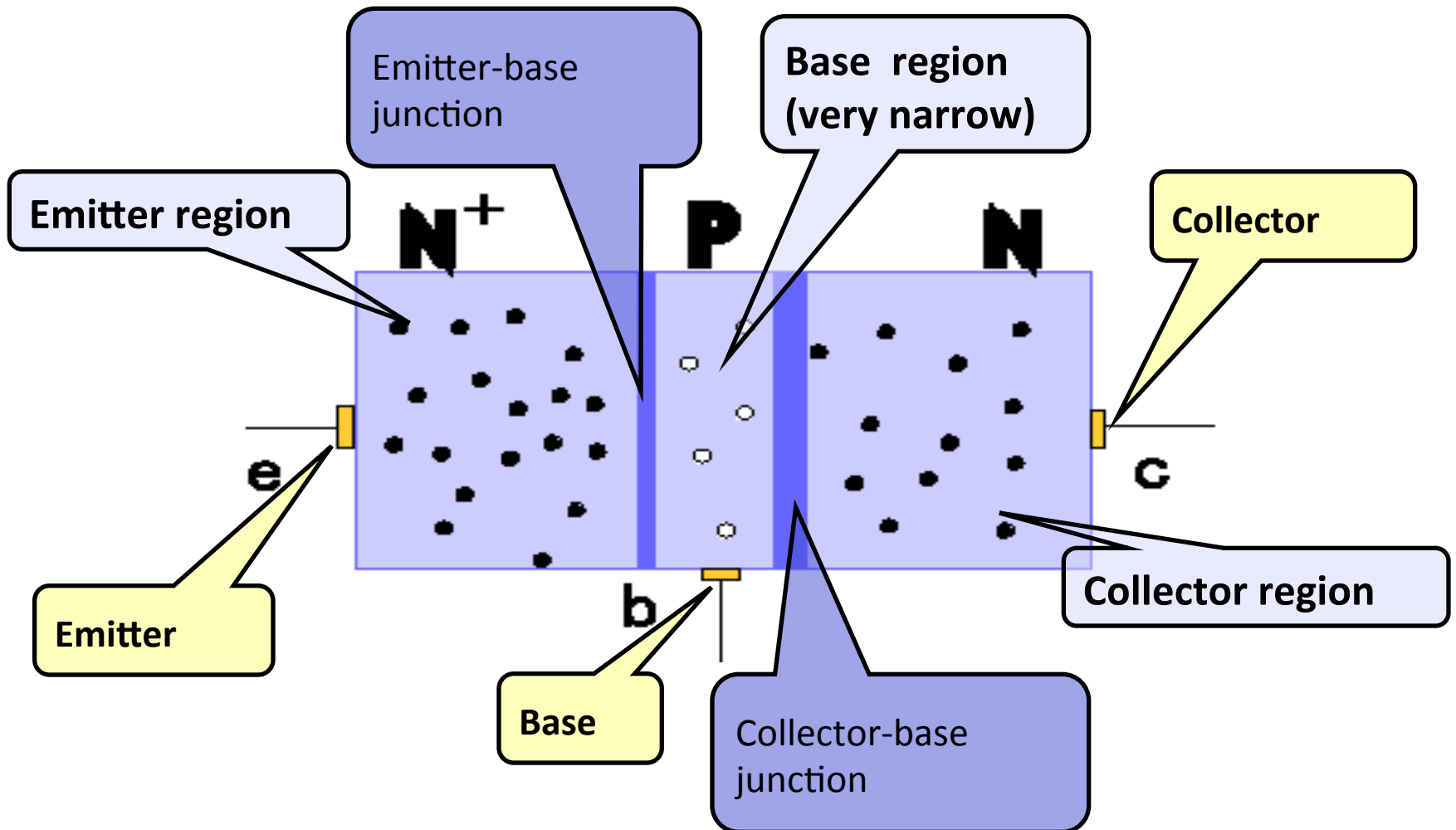Construction of Bipolar junction transistors



 
Construction of Bipolar junction transistors





NPN BJT shown

- 3 terminals: emitter, base, and collector
- 2 junctions: emitter-base junction (EBJ) and collector-base junction (CBJ)


Unbiased npn Transistor

 

BJT



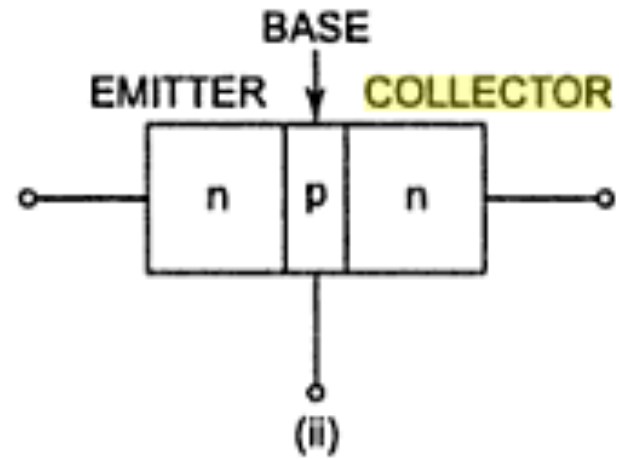
 


p-n-p transistor

 

n-p-n transistor

Standard Transistor Symbols

 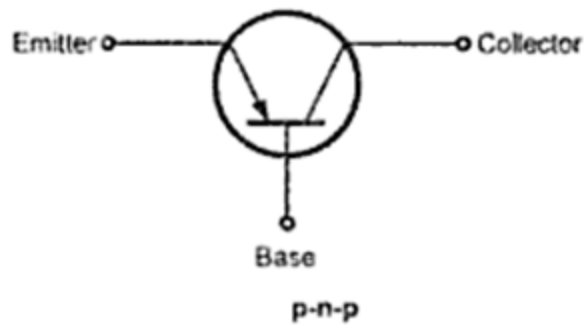  

Q: Explain the saturation, cutoff and active modes of transistor

Biased transistor

- In order to operate the transistor as an amplifier or switch, the two pn junctions have to be biased properly with external voltages.
- Depending on the external voltage polarity used, the transistor works in one of the three regions.

Region	Emitter base junction	Collector base junction
Active	Forward biased	Reverse biased
Cut-off	Reverse biased	Reverse biased
Saturation	Forward biased	Forward biased


Transistor Biasing

- Transistor as Amplifier – Active Region
- Transistor as ON switch – Saturation Region
- Transistor as OFF switch – Cutoff Region


Working of a npn transistor in Active mode

Biased Transistor

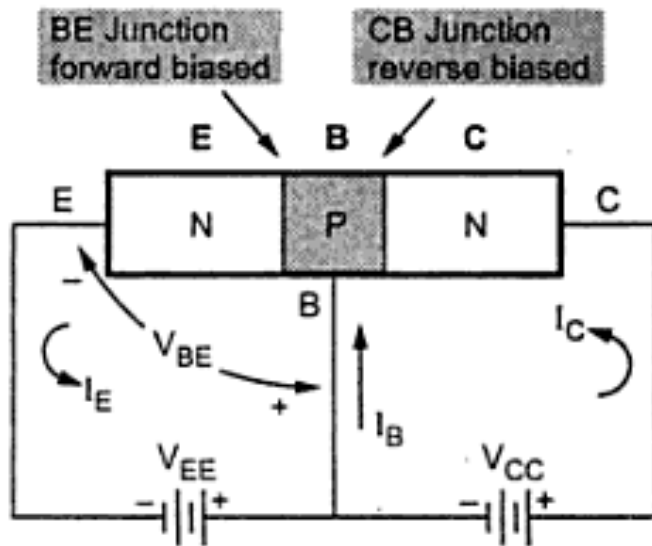Circuit connections for **active region** for npn and pnp transistor




(a) npn

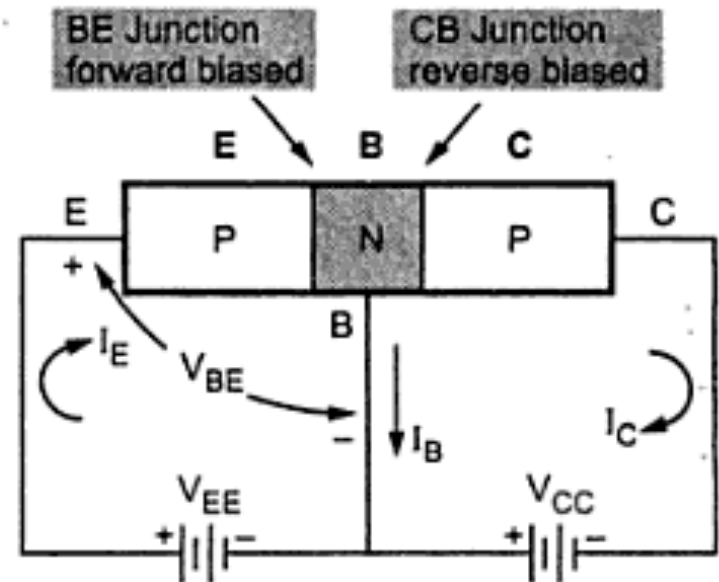

(b) pnp


Transistor forward-reverse **bias**

Working of a npn transistor

 


Basic connection of npn transistor

Working of a pnp transistor

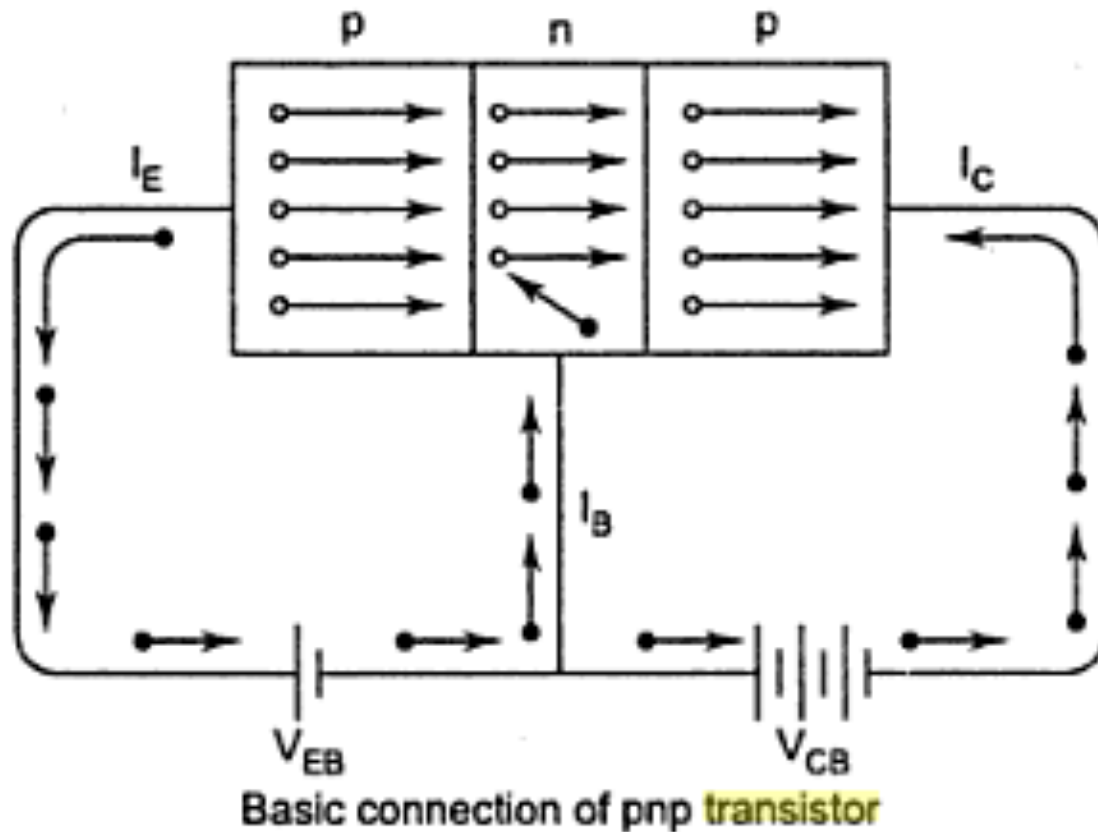


Transistor Current Relation

 

Basic connection of pnp transistor

Transistor Current Relation

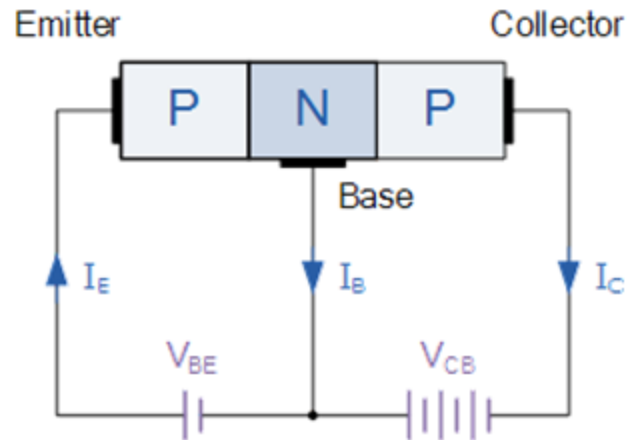

Relation between different currents in a transistor

The emitter current is equal to the sum of the collector and base currents, i.e.,

$$I_E = I_B + I_C$$

$$I_C = \alpha_{dc} I_E$$

α_{dc} is called emitter to collector current gain $\alpha_{dc} = \frac{I_C}{I_E}$


In many circuits, $I_C \approx I_E$, $\alpha_{dc} = 1$

Typical value of $\alpha_{dc} = 0.96$ to 0.995





Transistor Current Relation (Cont.)

$$I_C = \alpha_{dc} I_E + I_{CBO}$$

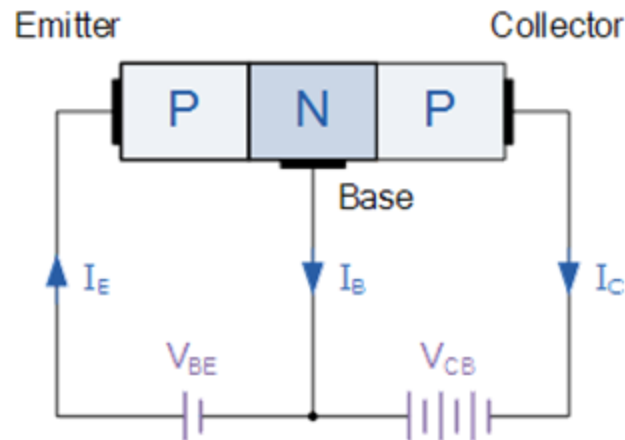I_{CBO} is called the reverse leakage current which flows as the CB junction is reverse biased.




Transistor Current Directions

 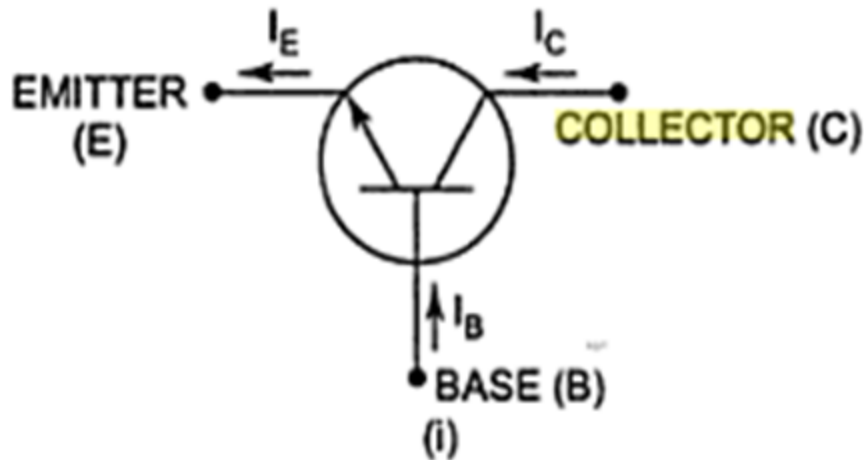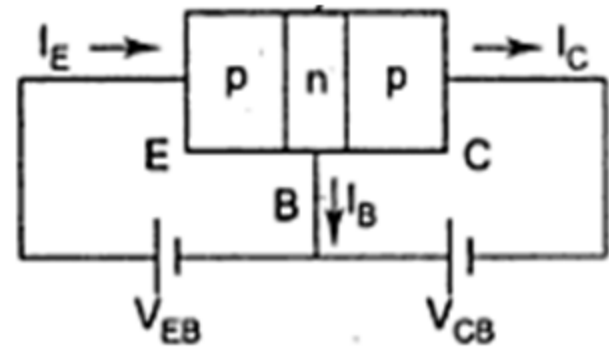 


$$I_E = I_B + I_C$$

 Transistor Voltage Source Connections and Terminal Voltages



 Voltage source connections for n-p-n transistor



Active


CB junction : Forward Biased

EB junction : Reverse biased

$V_{CC} > V_{BB}$: Active Mode


$V_{CC} < V_{BB}$: Saturation mode

 Transistor Voltage Source Connections and Terminal Voltages




Voltage source connection for p-n-p transistor

PNP Transistor

 

Transistor Voltage Source Connections and Terminal Voltages

n-p-n Transistor

 


$$V_{CC} > V_{BB} \text{ (ACTIVE)}$$

$$-V_{CB} - V_{BE} + V_{CE} = 0$$

$$V_{CB} = V_{CE} - V_{BE}$$

PNP Transistor

 

$$V_{BE} > 0.7 \text{ V}$$

$V_{CE} > 0.7 \text{ V}$, CB junction is Reverse biased, **ACTIVE MODE**

$V_{CE} < 0.7 \text{ V}$, CB junction is Forward biased, **SATURATION**


Transistor Configurations

DIFFERENT TYPES OF TRANSISTOR CONFIGURATION


There are three types of transistor configuration possible, namely :

- (i) Common base (CB) configuration
- (ii) Common emitter (CE) configuration
- (iii) Common collector (CC) configuration


Transistor Configurations

 

 (a) Common base configuration
with *npn* transistor



 (a) Common emitter circuit
of *npn* transistor



(b) Common collector circuit
of *pnp* transistor


Transistor Characteristic

Characteristic of CB

There are two important characteristics of **CB**. Configuration namely :


- (1) Input characteristics.
- (2) Output characteristics.

Input Characteristic

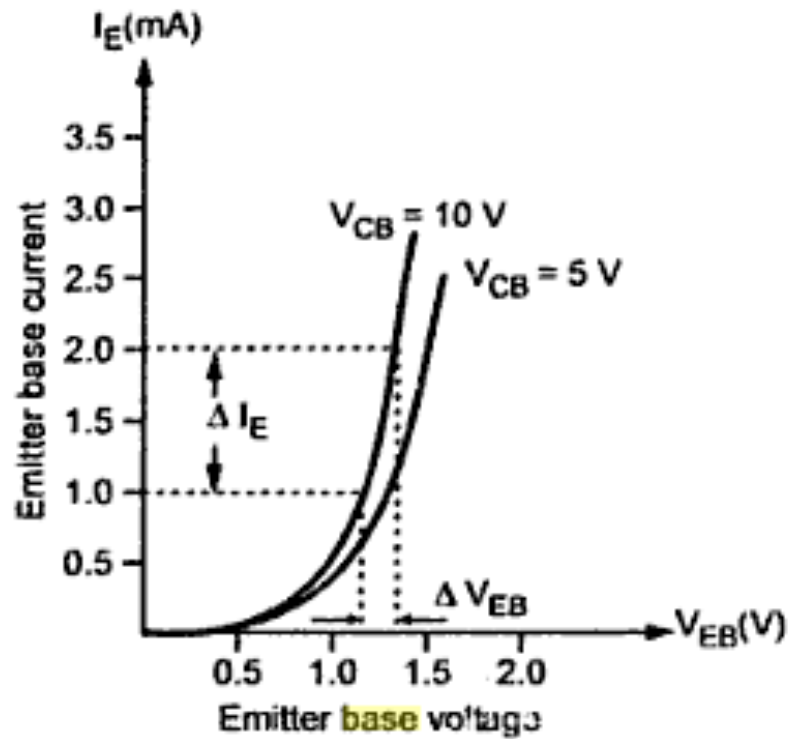

Input characteristics of transistor in CB configuration

Output Characteristic

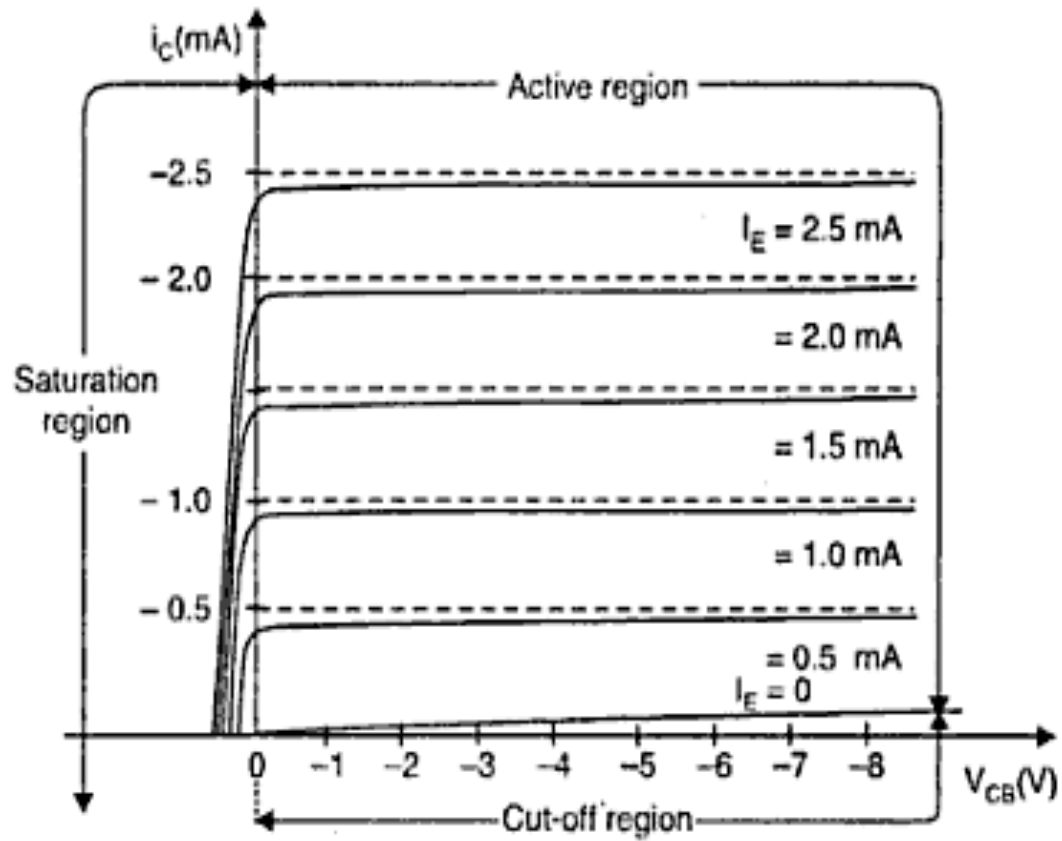


Operating Regions

- Active Region
- Cutoff Region
- Breakdown Region
- Saturation Region

Parameters

- Dynamic Input Resistant (r_i)
- Dynamic Output Resistance (r_o)
- Dc current gain (α_{dc})
- Short Circuit Current Gain (α or h_{fb})

COMMON BASE CONFIGURATION

 

Emitter current amplification factor (α)

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \text{at constant } V_{CB}$$

$$I_E = I_C + I_B$$

$$\text{or } \Delta I_E = \Delta I_C + \Delta I_B,$$

CB current gain or current transfer ratio:

$$\alpha = \frac{I_C}{I_E} < 1$$

For example, $\alpha = 0.99$, indicates that 99% of the electrons from the emitter arrive at the collector to form I_C while only 1% combined with the hole in the base to form I_B


Total collector current of a common base (CB) configuration

total collector current

$$I_C = \alpha I_E + I_{\text{leakage}}$$

$$I_C = \alpha I_E + I_{CBO}$$

 Here, I_{CBO} (leakage current) is due to minority charge carriers i.e., collector base junction open emitter (or $I_E = 0$).



Reverse leakage current in CB configuration.

Common Base Configuration

The relationship between the output I_C and the input I_E can be found as:

$$I_C = \alpha I_E + I_{CB0} \approx \alpha I_E$$

The base current I_B is:

$$I_B = I_E - I_C \approx I_E - \alpha I_E = (1 - \alpha)I_E$$

Summary :

$$\begin{cases} I_C = \alpha I_E \\ I_B = I_E - I_C = (1 - \alpha)I_E \end{cases}$$

Characteristic of CE


There are two important characteristics of **CE** configuration namely :

- (1) Input characteristics.
- (2) Output characteristics.


Common-Emitter NPN Transistor

Reverse bias the CBJ

Forward bias the BEJ

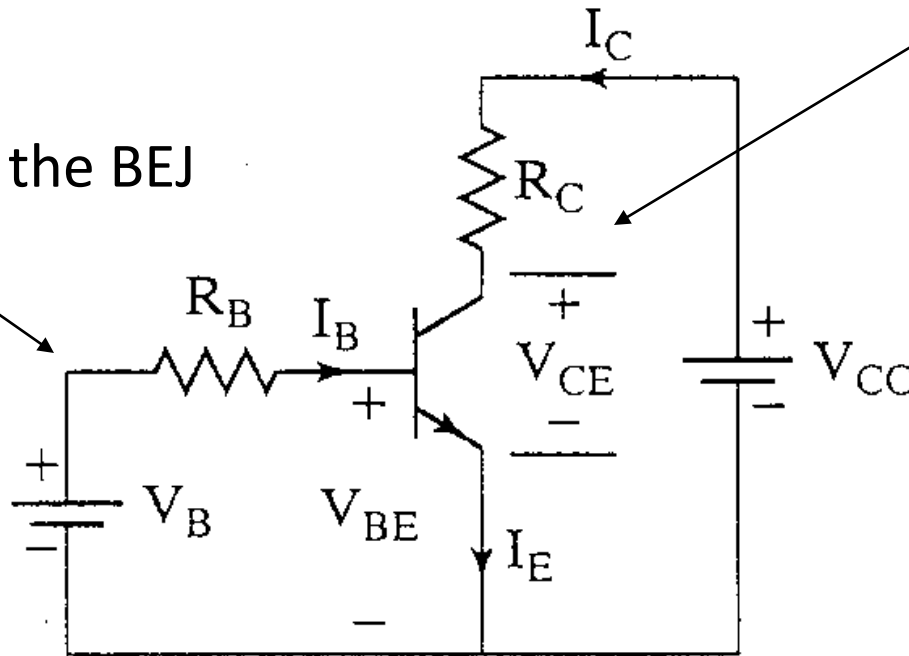


Input Characteristic of CE

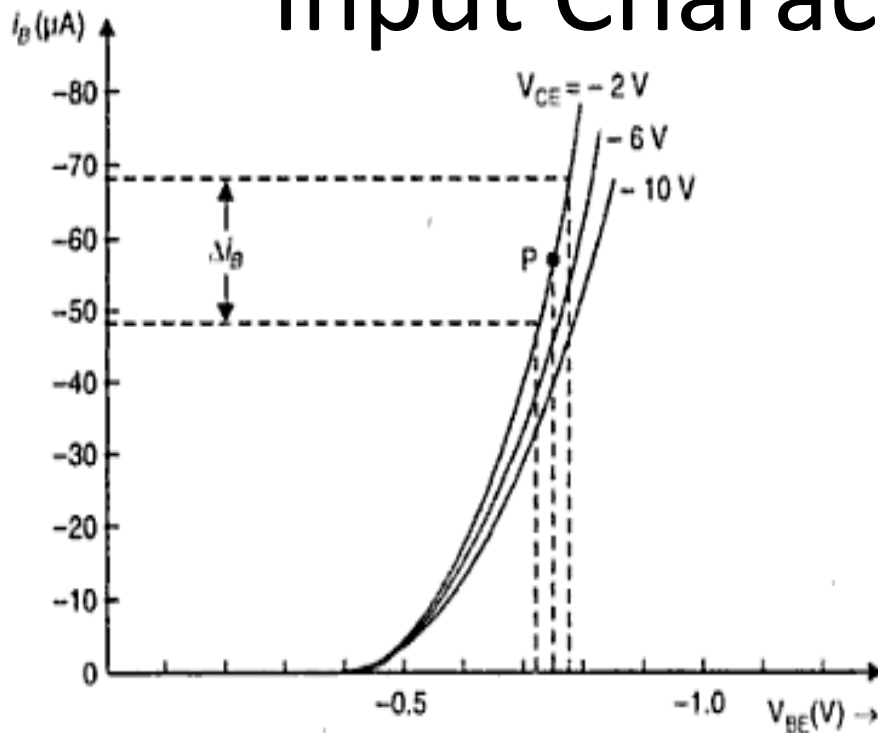

Common-emitter input characteristics of a PNP transistor.

 
- Plot I_B as $f(V_{BE}, V_{CE})$
- As V_{CE} increases, more V_{BE} required to turn the BE on so that $I_B > 0$.
- Looks like a pn junction volt-ampere characteristic.




Input Resistance.

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B} \text{ at constant } V_{CE}$$


Output Characteristic of CE

 

(i)

 

(ii)

 

(iii)


Output resistance.

$$\text{Output resistance, } r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$

Output Characteristics

Q : Explain the three regions of operation of CE BJT

 - Plot I_C as $f(V_{CE}, I_B)$
- Cutoff region (off)
 - both BE and BC reverse biased
- Active region
 - BE Forward biased
 - BC Reverse biased
- Saturation region (on)
 - both BE and BC forward biased



CE Configuration

Base current amplification factor (β)

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{\text{Variation in collector current}}{\text{Variation in base current}}$$

Relation between α and β

Q : Derive the relation between α and β hence find the value of β if $\alpha = 0.95$

We know that

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\Delta I_E = \Delta I_C + \Delta I_B$$

$$\frac{\Delta I_E}{\Delta I_C} = \frac{\Delta I_C}{\Delta I_C} + \frac{\Delta I_B}{\Delta I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

Therefore, above relation shows that as α approaches to unity, β approaches to infinity. In other words, the current gain in common emitter configuration is very high.

Q : Find the value of α if β of the transistor is 49.

Find the value of I_C of the transistor using both α and β rating of the transistor

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\alpha = \frac{49}{1 + 49} = .98$$

$$I_C = \alpha I_E = .98 (12 \text{ mA}) = 11.76 \text{ mA}$$

$$I_C = \beta I_B = 49 (240 \text{ } \mu\text{A}) = 11.76 \text{ mA.}$$

Q : A certain transistor has $\alpha = .98$, $I_{CO} = 5 \mu\text{A}$, $I_B = 100 \mu\text{A}$. Find the values of collector current and emitter current.

Solution : Given $\alpha = .98$

$$I_{CO} = 5 \mu\text{A}$$

$$I_B = 100 \mu\text{A}$$

We know that the collector current given by the relation,

$$I_C = \beta I_B + (1 + \beta) I_{CO} \text{ and}$$

From relation, $\beta = \frac{\alpha}{1 - \alpha} = \frac{.98}{1 - .98} = 49.$

Then

$$\begin{aligned} I_C &= 49.100 \times 10^{-6} + (1 + 49) 5 \times 10^{-6} \\ &= 4900 \times 10^{-6} + 250 \times 10^{-6} \text{ A} \\ &= 5150 \times 10^{-6} \text{ A} \\ &= 5.150 \text{ mA} \quad \text{Ans.} \end{aligned}$$


Also we know that the emitter current

$$I_E = I_C + I_B$$


$$I_E = 5.150 \text{ mA} + 100 \mu\text{A}$$

$$I_E = 5.25 \text{ mA.}$$

Common Collector (CC) Configuration

 

 (a) Common collector circuit of *n-p-n* transistor



(b) Common collector circuit of *p-n-p* transistor

Current amplification factor (γ)

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

**Q : Derive the relation between α and β
hence find the value of β if $\alpha = 0.95$**

Relation between γ and α

We know that

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\Delta I_E = \Delta I_C + \Delta I_B$$

$$\gamma = \frac{1}{1 - \alpha}$$

Comparison of the configurations

Parameters	C-B configurations	C-E configuration	C-configuration
1. Input dynamic resistance	Very low (20 Ω)	Low (1 K Ω)	Very high (1 M Ω)
2. Output dynamic resistance	Very high (1 M Ω)	High (10 K Ω)	Very low (25 Ω)
3. Current gain	Less than unity	Large (50 to 100)	Very high (150)
4. Voltage gain	Very high (150)	Large (100 to 125)	Less than unity.

CE Configuration widely used in amplifier circuit ?

CE Configuration is mostly used due to :

- High Voltage Gain
- High Current Gain
- High Power Gain

Q: With the help of neat diagram, explain the construction , characteristics and working of typical BJT used for voltage amplification

Ans: (points)

Construction of Transistor.

Transistor as an amplifier uses active mode of biasing.

***Active mode of biasing – Emitter Base junction is Forward Biased
and Collector Base junction is Reverse Biased .***


Transistor configuration used for amplifier is Common Emitter configuration.

Draw the circuit diagram.

Draw the output characteristic of Transistor in CE mode and explain the working

Transistor as an amplifier

 Q: Draw and Explain the Transistor as an amplifier




A basic **transistor** amplifier in common-base configuration.

A signal source V_s is connected in input circuit.

Input impedance of the transistor is $1\text{ k}\Omega$, output impedance is $10\text{ k}\Omega$.

 Q: Draw and Explain the Transistor as an amplifier



Signal V_s is superimposed on dc voltage V_{BB}

V_{BE} varies with time.

I_B varies with time as a result collector current I_C and emitter current I_E varies with time.

This varying , collector current I_C passes through R_L and a varying output voltage is developed across it.

Example:

To understand how a signal voltage is magnified

Input signal voltage $V_s = 20 \text{ mV (rms)}$

Input impedance of the transistor is $1\text{K}\Omega$, output impedance is $10\text{K}\Omega$.

$$I_B = \frac{20 \times 10^{-3}}{1 \times 10^3} = 20 \mu\text{A}$$

Dc current gain of transistor (β) of CE transistor is 100

$$I_C = \beta I_B = 100 \times 20 \mu\text{A} = 2 \text{ mA}$$

Output resistance of transistor is very high,

therefore output voltage V_o is approximately:

$$V_o = I_C R_L = 2 \text{ mA} \times 5 \text{ k}\Omega = 10 \text{ V}$$

Q: Draw and Explain the Transistor as an amplifier


Voltage Amplification :

$$A_v = \frac{V_o}{V_s} = \frac{10}{20 \text{ mV}} = 500$$


Thus, Transistor Amplifying action is basically due to its capability of transferring its signal current from low resistance circuit to a high resistance circuit

Transfer + Resistor = TRANSISTOR


Graphical method

 

Transistor as a Switch

 

(a) npn transistor (open switch)

 


(b) npn transistor (closed switch)

Switch condition	I_C		V_{CE}	
	Ideal	Practical	Ideal	Practical
OFF	0	I_{CO}	Open circuit	Maximum V_{CC}
ON	∞	$I_{C(sat)}$	0	$V_{CE(sat)}$

Operating Point


Values of V_{CE} and I_C in the absence of ac input signal (V_s) is called OPERATING POINT

 OPERATING POINT = (I_C, V_{CE}) values of the given circuit with the applied DC bias for no input signal



CE-Configuration circuit.

 Example: To find operating point for the given circuit.



CE-Configuration circuit.

Applying KVL to the input section and neglecting V_{BE}

$$V_{BB} = R_B I_B$$

$$I_B = \frac{V_{BB}}{R_B} = \frac{2}{10} = .2\text{ mA}$$

$$I_C = \beta I_b = 100 \times .2 = 20\text{ mA}$$

Contd:

Applying KVL to the output section:


$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} + I_C R_C = 10$$

$$V_{CE} = 10 - 20 \times 200 \times 10^{-3} = 6 \text{ V}$$

Operating point defined by :
 
$$I_C = 20 \text{ mA and } V_{CE} = 6 \text{ V}$$





Q: Explain the DC load line analysis of a transistor, Dependency of Q point , temperature , β

DC Load Line

- It is a straight line drawn on the output characteristic of the transistor.
- DC Load Line is used for analyzing the performance of an AMPLIFIER,
- It is a graph of Collector current (I_c) versus Collector Emitter voltage (V_{ce}) for a given value of R_c and V_{cc} .
- It is a graphical representation of all the possible operating points for the given circuit with the given DC biasing.

How to plot a DC load line?

  

Step 1. Applying KVL in the output of circuit.



$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CC} = I_C R_C + V_{CE}$$

Step 2. On putting $V_{CE} = 0$, we get

$$I_C = \frac{V_{CC}}{R_C} = \frac{20}{10 \text{ k}\Omega} = 2 \text{ mA.}$$

How to plot a DC load line?

  

Step 3. On putting $I_C = 0$ in eqn. we get,

$$V_{CE} = V_{CC} = 20 \text{ V}$$

Step 4. Join these values (i.e., $I_C = 2 \text{ mA}$ and $V_{CE} = 20 \text{ V}$) as shown in Fig.


To find the Q point for previous problem?

Applying KVL to the input section and neglecting V_{BE}

$$V_{BB} = I_B R_B$$

$$I_B = \frac{V_{BB}}{R_B} = \frac{10}{47 \text{ k}\Omega} = .213 \text{ mA}$$
 
$$I_C = \beta I_B = 100 \times .213 = 21.3 \text{ mA}$$




Applying KVL to the output section:

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = 20 - .213 \times 10^{-3} \times 10 \times 10^3$$

$$V_{CE} = 17.87 \text{ V.}$$

 

The quiescent point (17.87 V, .213 mA) is shown in Fig.

Q: Dependency of Q point on temperature and β

STABILIZATION

OPERATING POINT is the zero signal values of
 (I_C, V_{CE}) .

If either of the two changes, the operating point is shifted.

Causes of unstabilization?

- A transistor is said to be unstabilized when its operating point is shifted, due to changes in collector current.
- The Collector current in a transistor changes rapidly due to following reasons:

1. *Inherent variations of transistor parameters:*

If the transistor is replaced by another one of the same type.
(Because no two transistor can have same transistor parameters (i.e. β)

2. *The temperature changes affects I_c .*

How does Temperature change affect I_c .

$$I_c = \beta I_B + I_{CEO}$$

- Leakage current I_{co} increases due to increase in temperature.
- Increase in I_{co} increases I_c .
- Rise in I_c increases temperature.
- Rise in Temp. further increases I_c .
- Rise in I_c further increases Temp. , Temp. rise further increases I_{co} , increase in I_{co} further increases I_c and hence temp and so on.

Cumulative Effect: **THERMAL RUNAWAY**

Self destruction of transistor


Operation point stabilization

The process of making operating point independent of temperature changes or inherent variation in transistor parameters is called STABILIZATION

TRANSISTOR BIASING

What is transistor DC biasing ?

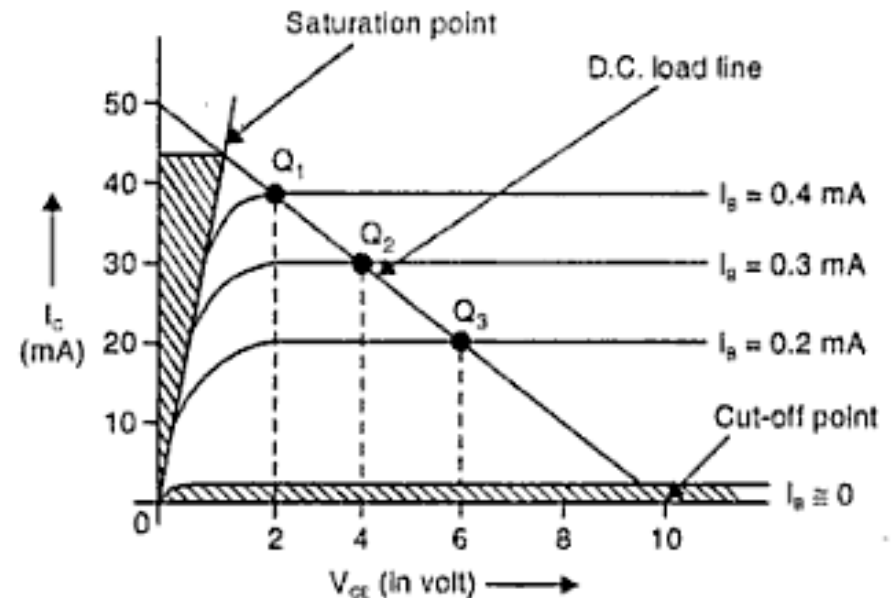Biassing is selection of operating point (Quiescent point) to operate a transistor in a desired region (Active, cutoff, saturation)



Biassing Circuit:


The circuitry which provides the necessary conditions of transistor biasing is known as biasing circuit.

Need of Transistor Biasing


For Transistor as an amplifier:

After applying input AC signal

 Operating point should always remain in ACTIVE REGION




Operating Point in ACTIVE REGION ?

 


Output characteristics if D is selected as the operating point.

Operating Point in ACTIVE REGION ?

 

Output characteristics if E is selected as the operating point.

Operating Point in ACTIVE REGION ?

 

Output characteristics if C is selected as the operating point.

Requirements of Transistor Biasing Circuit ?

1. It should ensure proper zero signal I_C and V_{CE}

*i.e. operating point should be established in the center of the **active region** of the characteristics, so that signal may not cutoff at any part.*

2. It should make the operating point independent of transistor parameters.

So that it does not shift when the transistor is replaced with another of the same type in the circuit.

3. Stabilize the collector current against temperature variation.

Different Biasing Circuits

1. Fixed Biasing or Base Resistor Bias.
2. Collector to base Biasing.
3. Emitter resistor biasing
4. Potential divider biasing

Analysis of fixed bias circuit

Operating Point:


To find I_C and V_{CE}

To find I_C ?

Apply KVL to the input side and find I_B

Find I_C by equation: $I_C = \beta I_B$

 
Find V_{CE} by applying KVL to the outer loop



Fixed biasing circuit for npn transistor.

Fixed Bias (Base Resistor Biasing)

 1. In this biasing a high valued resistor is connected between the supply and base of the transistor.
2. The Base emitter junction is forward biased and the base collector junction is reverse biased by the supply voltage V_{cc} .
3. For a pnp transistor the negative end of the supply is to be connected to the R_c and R_b .



Fixed biasing circuit for npn transistor.

Q : Draw and Explain Base resistor method of biasing

*Q : Draw and Explain Base resistor
method of biasing*

To calculate I_C :

Apply KVL to the input section

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B + I_{CEO}$$

Neglecting , I_{CEO}


$$I_C = \beta I_B$$

To calculate V_{CE} :

Apply KVL to outer loop:

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$

 

*Fixed biasing circuit for
npn transistor.*

Operating point : (I_C, V_{CE})

Advantages of Fixed Bias:

- Calculations are simple
- Simple in construction

Only two resistors and a battery is needed

- Easy to fix the operation point anywhere in the active region of the characteristic.

By simply changing the value of R_b .

Q : Draw and Explain Base resistor method of biasing

Disadvantages of Fixed Bias:

- Operating point can be fixed in the center of the active region.

But it miserably fails in the other two requirements of the biasing circuit.

- Operating point is not stable w.r.t temperature rise and transistor parameter β


Q : Draw and Explain Base resistor method of biasing

Collector to Base Biasing

 1. In this biasing a very high value resistance R_b is connected between the collector and base, and R_c is connected between Supply voltage and collector of transistor .
2. The base current I_b feedbacks from the output.

The base current I_b depends upon the collector voltage.

*This circuit is also called as
VOLTAGE FEEDBACK BIASING CIRCUIT.*



Collector-to-base biasing for an npn transistor.

Analysis of Collector to base bias

To calculate I_c :

Apply KVL to inner loop:

$$V_{CC} - (I_B + I_C) R_C - I_B R_B - V_{BE} = 0$$

$$I_C = \beta I_B$$


$$\therefore V_{CC} - V_{BE} = (I_B + \beta I_B) R_C + I_B R_B$$

$$\therefore V_{CC} - V_{BE} = I_B [(1 + \beta) R_C + R_B]$$

\therefore

$$I_B = \frac{V_{CC} - V_{BE}}{(1 + \beta) R_C + R_B}$$

$$I_C = \beta I_B$$

 

Collector-to-base biasing for an npn **transistor**.

Collector to Base Biasing

To calculate V_{CE} :

Apply KVL to outer loop:

$$V_{CC} = (I_C + I_B) R_C + V_{CE}$$

$$V_{CE} = V_{CC} - (I_B + I_C) R_C$$

Advantages of collector to base bias

Tendency of the circuit to stabilize the operating point against temperature variations and transistor parameter variations

Advantages of collector to base bias

- If there is an increase in β due to piece variation. OR
- If there is a increase in β and I_{CO} due to the change in temperature.

$$I_C = \beta I_B + I_{CEO}$$

I_C increases

$$V_{CE} = V_{CC} - I_C R_C$$

V_{CE} decreases

$$I_B = \frac{V_{CE} - V_{BE}}{R_C + R_B}$$


I_B decreases

$$I_C = \beta I_b$$

I_C decreases

Rising tendency in I_C is checked

Advantages of collector to base bias

 

Rising tendency of I_C with increase in temp is checked

Advantages of collector to base bias

- I_c depends on I_b .
- Decrease in I_b reduces the original increase in I_c (Negative feedback).
- Therefore the circuit maintains a stable value of collector current, keeping Q point fixed.


Collector to Base bias is seldom used ?

- The resistor R_B also provides ac feedback.

This reduces the voltage gain of the amplifier.

Emitter Resistor Biasing

 - It is just a modification to the Base Resistor Biasing circuit.
- In this biasing an additional resistor R_E is connected in the emitter.
- Hence, this circuit contains three resistors R_B , R_C and R_E .



*Emitter biasing
circuit for an npn **transistor**.*

Analysis of operating point

Writing the loop equation for input circuit, we get

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$


$$V_{CC} = I_B R_B + V_{BE} + (\beta + 1) I_B R_E \quad (\text{since } I_E = (\beta + 1) I_B)$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Neglecting V_{BE} since it is very small


$$I_B \approx \frac{V_{CC}}{R_B + \beta R_E}$$
 
$$\text{Collector current, } I_C = \beta I_B = \frac{\beta V_{CC}}{R_B + \beta R_E} = \frac{V_{CC}}{R_E + (R_B / \beta)}$$



*Emitter biasing circuit for an npn **transistor**.*

Analysis of operating point

 

Emitter biasing circuit for an npn transistor.

Writing the loop equation for the output circuit, we get

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = V_{CC} - (R_C + R_E) I_C \quad (I_C \approx I_E)$$

Thus, operating point can be obtained from above equations.

Similarly, for the given operating point, the value of R_B and R_E can be determined from the above equations provided the other data via V_{CC} , R_C and β are known.


Stabilization

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$I_B = \frac{V_{CC} - I_E R_E - V_{BE}}{R_B}$$

(since V_{BE} is very small)
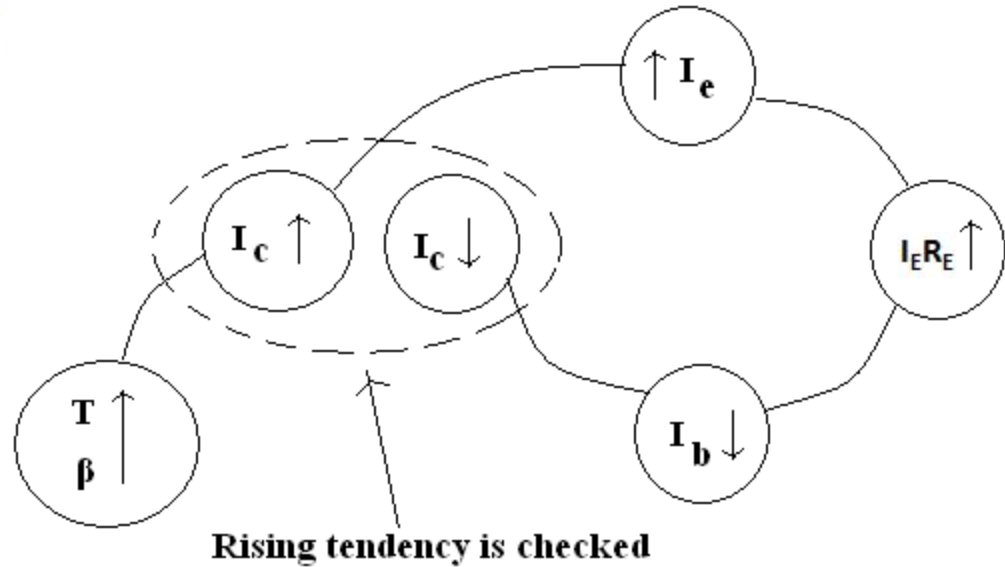
$$I_B \approx \frac{V_{CC} - I_E R_E}{R_B}$$



• Thus, an increase in collector current is brought back to its previous value by the sequence of events.

• Hence, the stability of the operating point is improved to large extent by inserting a resistor in emitter circuit.

Advantages

- The stability factor of this biasing is quite high.
- Hence, the operating point does change, although to lower extent, due to temperature rise or inherent variations in parameters.
- The **DC feedback** helps in the stabilization of operating point .
- But at the same time **AC feedback** reduces the voltage gain of the amplifier.
- This is an undesirable feature.
- However, this drawback can be remedied by **putting a capacitor C_E across the resistor R_E** . The capacitor C_E offers very low impedance to the AC current and does not allow it to pass through R_E and hence AC feedback is restricted. Thus, the process of amplification remains unaffected

Drawback of Emitter bias

This biasing circuit is also **not practically used** because of the following reason:

$$I_c = \beta I_b$$

$$\text{i.e. } I_c = \frac{V_{CC}}{R_E + (R_B / \beta)}$$

For stability, I_c should be independent of β

i.e denominator should be independent of β

$$R_E \gg R_B / \beta$$


$$\text{i.e. } I_C = \frac{V_{CC}}{R_E + (R_B/\beta)}$$

$$R_E \gg R_B/\beta$$

- This condition can only be obtained either using R_E of very large value or by using R_B of very small value.
- Now, a large value of R_E will cause a large voltage drop across it and to obtain a required operating point, we have to apply a voltage source V_{CC} of high value.
- On the other hand, if R_B is of very low value, a separate low voltage supply has to be used for base circuit.
- ***Both these alternatives are quite impractical. Hence, this biasing circuit is not used practically.***

Voltage Divider Bias


- Most widely used biasing circuit.

 

**Voltage
divider bias circuit**


Q : Draw and Explain Voltage Divider method of biasing

 Analysis of Operating Point: (I_C and V_{CE})



Voltage divider bias circuit

Input Circuit

 

Base circuit

V_B can be given by

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

Voltage Divider Bias

Output Circuit

Now, let us consider the **collector circuit**

Voltage across R_E (V_E) can be obtained as,

$$V_E = I_E R_E = V_B - V_{BE}$$


$$\therefore I_E = \frac{V_B - V_{BE}}{R_E}$$

$$I_C \approx I_E$$

Applying KVL to the **collector circuit** we get,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$


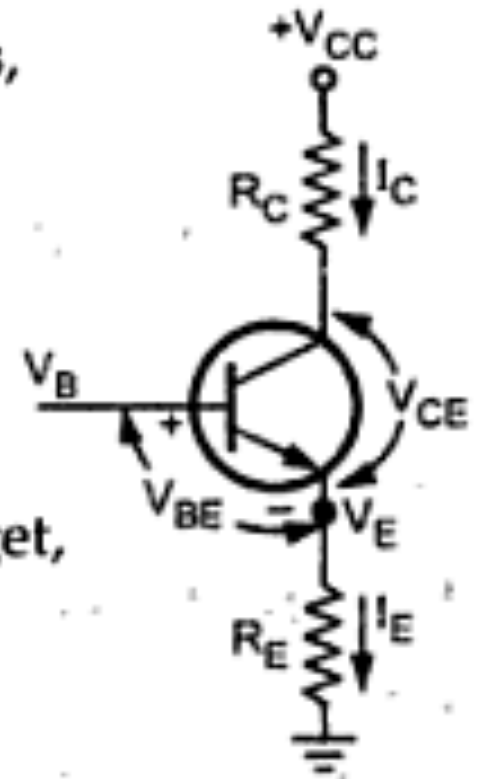
$$\therefore V_{CE} = V_{CC} - I_C R_C - I_E R_E$$



Operating point : (I_C , V_{CE})

Problems

  1. For the circuit shown plot the DC load line



The collector-emitter voltage V_{CE} is given by :

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = 0$$

$$V_{CE} = V_{CC} = 12.5 \text{ V}$$

This locates the point B of the load line on the collector-emitter voltage axis.

When $V_{CE} = 0$

$$I_C = \frac{V_{CC}}{R_C} = \frac{12.5 \text{ V}}{2.5 \text{ k}\Omega} = 5 \text{ mA}$$

This locates the point A of the load line on the collector current axis. By joining these two points, we get the d.c. load line AB

2. In a transistor circuit, collector load is $4 \text{ k}\Omega$ whereas quiescent current (zero signal collector current) is 1 mA .

(i) What is the operating point if $V_{CC} = 10 \text{ V}$?

(ii) What will be the operating point if $R_C = 5 \text{ k}\Omega$?

$$V_{CC} = 10 \text{ V}, I_C = 1 \text{ mA}$$

(i) When collector load,

$$R_C = 4 \text{ k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1 \text{ mA} \times 4 \text{ k}\Omega = 10 - 4 = 6 \text{ V}$$

\therefore Operating point is $6 \text{ V}, 1 \text{ mA}$.

(ii) When collector load,

$$R_C = 5 \text{ k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1 \text{ mA} \times 5 \text{ k}\Omega = 10 - 5 = 5 \text{ V}$$

\therefore Operating point is $5 \text{ V}, 1 \text{ mA}$.

3.

A base resistor biasing circuit is shown in Fig. Determine (assume $V_{BE} = 0.6 \text{ V}$ and $\beta = 60$).

- (i) The collector current I_C
- (ii) Collector emitter voltage V_{CE}

Given


$$V_{BE} = 0.6 \text{ V}$$

$$V_{CC} = 10 \text{ V}$$

$$\beta = 60$$

$$R_B = 20 \text{ k}\Omega$$

$$R_C = 300 \Omega$$

 


Applying KVL in the input section.

$$10 - I_B R_B - V_{BE} = 0.$$

$$I_B = \frac{10 - V_{BE}}{R_B} = \frac{10 - .6}{20 \text{ k}\Omega} = \frac{9.4 \text{ V}}{20 \text{ k}\Omega} = .47 \text{ mA}.$$
 
$$I_C = \beta I_B = 60 \times .47 = 28.2 \text{ mA. } \mathbf{Ans.}$$




(ii) Again, applying the KVL in the output section

$$10 - I_C R_C - V_{CE} = 0.$$

$$V_{CE} = 10 - I_C R_C$$

$$= 10 - 28.2 \times 300 \times 10^{-3}$$
 
$$V_{CE} = 1.54 \text{ V. } \mathbf{Ans.}$$



4.

Draw the dc load line and locate the operating point for the fixed biasing transistor circuit shown in. (assume $V_{BE} = .6 \text{ V}$)

DC Load Line

Applying KVL to the output the circuit.

$$V_{CC} - I_C R_C - V_{CE} = 0$$



On putting the value $V_{CE} = 0$ in eqn. (1), we get

$$I_C = \frac{V_{CC}}{R_C} = \frac{9}{2 \text{ k}\Omega} = 4.5 \text{ mA (assume OA)}$$

On putting the value of $I_C = 0$. In eqn. (1), we get,

$$V_{CE} = V_{CC} = 9 \text{ V (assume OB)}$$

  To draw the load line join the values OA and OB.



4.

Operating Point

$$\text{Now, } I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{9 - .6}{8 \text{ k}\Omega} = \frac{8.4}{8} = 1.05 \text{ mA}$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$= 9 - \beta I_B R_C$$

$$= 9 - 2 \times 1.05 \times 2 = 9 - 4.2 = 4.8 \text{ V}$$

$$I_C = \beta I_B = 2 \times 1.05 = 2.1 \text{ mA}$$

 Hence, operating point $Q (V_{CE}, I_C) = 4.8 \text{ V}, 2.1 \text{ mA}$.



5.

For the circuit determine the emitter current the collector voltage V_C

Neglecting V_{BE} .

Since emitter is grounded so

$$\left. \begin{aligned} V_{CE} &= V_C & \therefore & V_{CE} = V_C - V_E \\ & & & = V_C - 0 \\ & & & = V_C \end{aligned} \right\}$$

Now applying KVL to the input side


$$V_{CC} - I_E (600) - I_B \times 600 \times 10^3 - V_{BE} = 0$$

$$V_{CC} - (I_B + I_C) 600 - I_B \times 600 \times 10^3 = 0 \quad (\because V_{BE} = 0)$$

$$V_{CC} - (I_B + I_B \beta) 600 - I_B \times 600 \times 10^3 = 0$$

$$I_B = \frac{V_{CC}}{600 \times 10^3 + 100 \times 600}$$
 
$$= \frac{12}{600 \times 10^3 + 100 \times 600} = 18.18 \mu\text{A}$$




5.

Now, applying KVL to the output circuit.

$$V_{CE} = V_C = V_{CC} - I_C R_C = 12 - 1.818 \times 10^{-3} \times 600 \\ = 10.91 \text{ V.}$$

$$I_C = \beta I_B = 100 \times 18.18 \text{ } \mu\text{A} = 1.818 \text{ mA.}$$
 
$$I_E = I_C + I_B = 1.818 \text{ mA} + 18.18 \text{ } \mu\text{A} \cong 1.818 \text{ mA.}$$




6.

For the circuit given in Fig. is used in self-biasing arrangement with $\beta = 44$, $R_L = 1.51 \text{ k}\Omega$, $R_E = 270 \text{ k}\Omega$, and $V_{CC} = 4.5 \text{ V}$. (Assume $V_{BE} = 0$) Estimate

(a) quiescent point


(b) Stability factor.

 

 (a) First we will take the Thevenin equivalent model.

$$V_{th} = 4.5 \times \frac{2.7}{2.7 + 27} = .40 \text{ V}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{27 \times (2.7)}{27 + 27} = 2.45 \text{ k}\Omega$$



6.

Now applying KVL to the input circuit,

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$


$$V_{th} - I_B R_{th} - V_{BE} - (I_B + I_C) R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (I_B + \beta I_B) R_E = 0 \quad (\because I_C = \beta I_B)$$

$$I_B = \frac{V_{th} \cdot \beta}{R_{th} + \beta R_E} \quad (\because V_{BE} = 0)$$

$$I_C = \beta I_B = \frac{44 (.40)}{2.45 \text{ k}\Omega + 44 \times .270 \text{ k}\Omega}$$

$$I_C = 1.228 \text{ mA}$$

 


6.

And, applying KVL to the output section,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$
 
$$\begin{aligned} V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 4.5 - 1.228 (1.5 + .270) \\ &= 4.5 - 2.173 = 2.326 \text{ V} \end{aligned}$$



Quiscent Point = (1.228mA, 2.326V)

Stability factor for potential divider biasing

$$S = (\beta + 1) \left[\frac{1 + \frac{R_{th}}{R_E}}{1 + \beta + \frac{R_{th}}{R_E}} \right] = (44 + 1) \left[\frac{1 + \frac{2.45}{.27}}{1 + 44 + \frac{2.45}{.27}} \right]$$

$$= 45 \left[\frac{1 + 9.07}{1 + 44 + 9.07} \right] = 8.38 \text{ Ans.}$$

7. For the circuit shown in Fig. $\beta = 100$ for the silicon transistor. Calculate V_{CE} and I_C .


$$V_B \cong \frac{R_2}{R_1 + R_2} V_{CC}$$
$$= \frac{5 \times 10^3}{10 \times 10^3 + 5 \times 10^3} \times 10 = 3.33 \text{ V}$$

$$V_E = V_B - V_{BE} = 3.33 - 0.7 = 2.63 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.63 \text{ V}}{500} = 5.26 \text{ mA}$$

$$I_B = \frac{I_E}{1 + \beta} = \frac{5.26 \times 10^{-3}}{101} = 52.08 \mu\text{A}$$
 
$$I_C = \beta I_B = 100 \times 52.08 \times 10^{-6} = 5.208 \text{ mA}$$



7.

Applying KVL to the collector circuit we get,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 10 - 5.208 \times 10^{-3} \times 1 \times 10^3 - 5.26 \times 10^{-3} \times 500 = 2.162V$$

