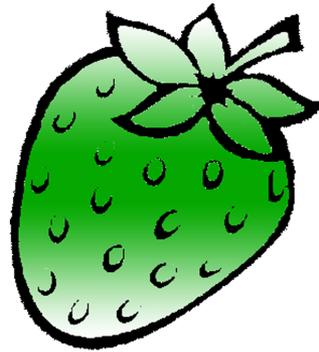


STRAWBERRY



 /strawberrydevelopers

 /strawberry_app

For more visit:

Strawberrydevelopers.weebly.com

FET (Field Effect Transistor)

Contents

- Junction FET
- Symbol
- Input/Output Characteristic
- Parameters
- JFET Biasing Methods

Contents (Contd.)


- MOSFET
- Symbol
- Input/Output Characteristic
- Parameters
- MOSFET Biasing Methods
- Applications – Switch, Digital Logic Gate and Amplifier.
- Temperature effects in MOSFETS
- Input Protection in MOSFET
- The Power FET (VMOS)

Introduction

1. Field effect transistors control current by voltage applied to the gate.
2. The FET's major advantage over the BJT is high input resistance (typically many megaohms).
3. It is simpler to fabricate and occupies less space than bipolar transistor
4. It is less noisy than BJT.
5. Its operation depends on the flow of majority charge carriers only (unipolar).
6. Overall, the purpose of the FET is the same as that of the BJT.

BJT vs JFET


Bipolar Junction Transistor

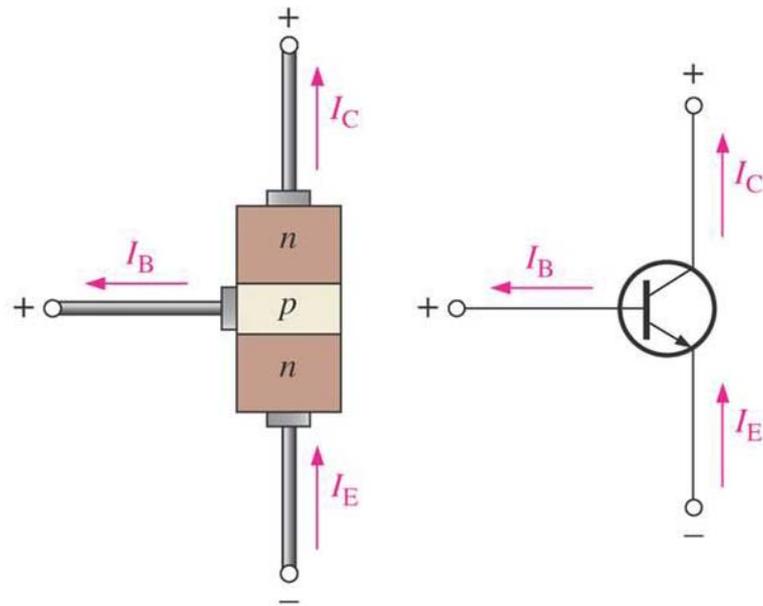

(a) npn

- Current-based device
- I_{Base} controls $I_{CollectorEmitter}$

Junction Field Effect Transistor

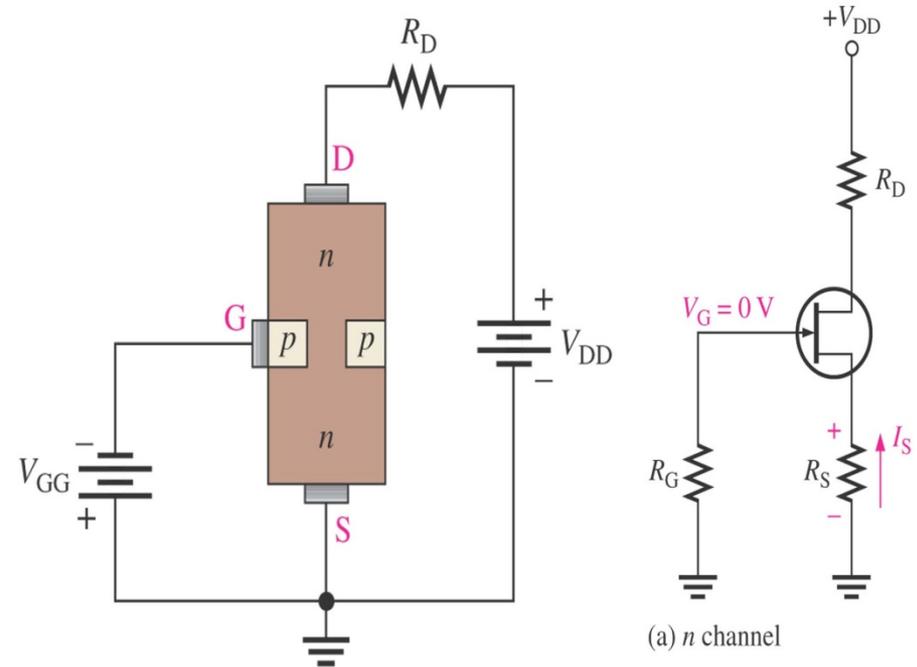


(a) n channel

- Current-based device
- V_{Gate} controls $I_{SourceDrain}$

The JFET – Primary Characteristics

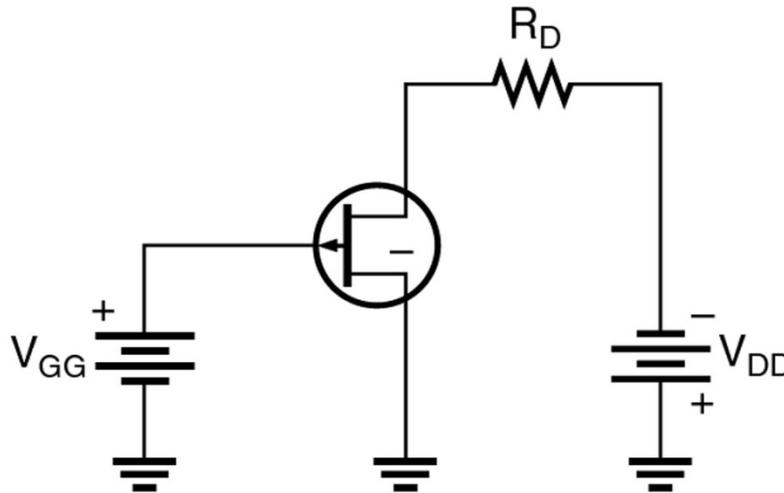- Junction field effect transistor controls current flow.
- The JFET uses voltage to control the current flow.
- You will recall, the transistor uses current flow through the base-emitter junction to control current.
- JFETs can be used as an amplifier just like the BJT.



- V_{GG} voltage level controls current flow in the V_{DD} , R_D circuit.

The Field Effect Transistor (FET)


- The FET was known as a “**unipolar**” transistor.
- The term refers to the fact that current is transported by carriers of one polarity (majority), whereas in the conventional bipolar transistor carriers of both polarities (majority and minority) are involved.

Field-effect transistors are so named because a weak electrical signal coming in through one electrode creates an electrical field through the rest of the transistor.

Few important advantages of FET over conventional Transistors

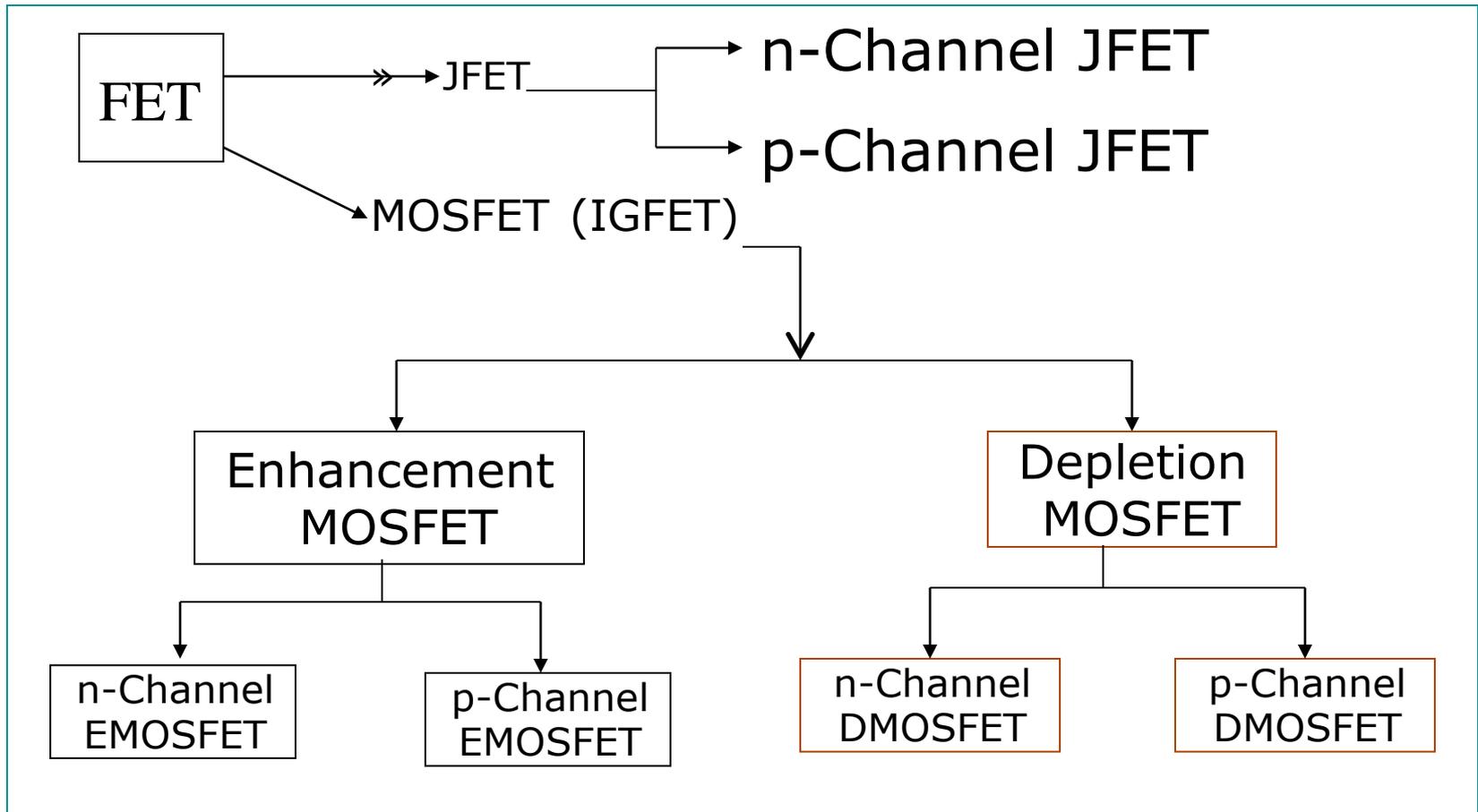1. Unipolar device i. e. operation depends on only one type of charge carriers (h or e) (MAJORITY CHARGE CARRIERS)
2. Voltage controlled Device (gate voltage controls drain current)
3. Very high input impedance ($\approx 10^9$ - $10^{12} \Omega$)
4. Source and drain are interchangeable in most Low-frequency applications
5. Low Voltage Low Current Operation is possible (Low-power consumption)
6. Less Noisy as Compared to BJT
7. No minority carrier storage (Turn off is faster)
8. Self limiting device
9. Very small in size, occupies very small space in ICs
10. Low voltage low current operation is possible in MOSFETS
11. Zero temperature drift of out put is possible.

Types of Field Effect Transistors (The Classification)



The Field Effect Transistor (FET)



The family of FET devices may be divided into :

- Junction FET
- Depletion Mode MOSFET
- Enhancement Mode MOSFET


Structure of
The Junction Field Effect Transistor (JFET)

Basic structure of JFETs

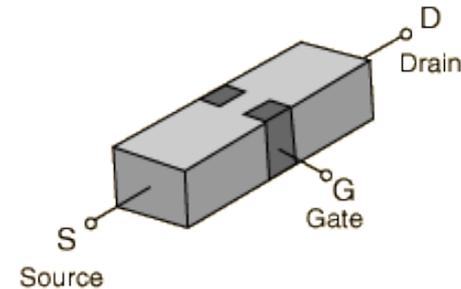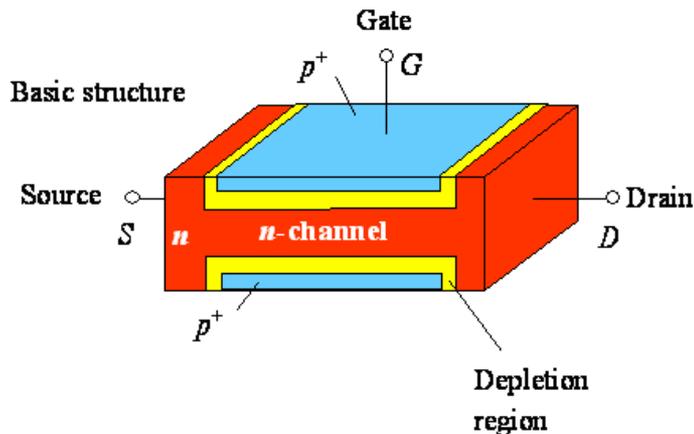- JFETs consists of a piece of high-resistivity semiconductor material (usually Si) which constitutes a **channel** for the majority carrier flow.
- Conducting semiconductor channel between two ohmic contacts – **source & drain**



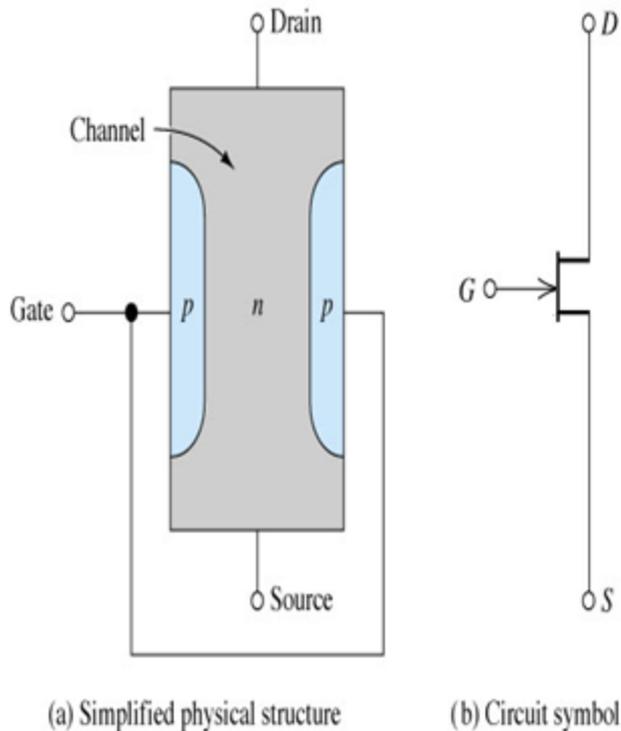N channel Junction Field Effect Transistor (JFET)



- The magnitude of this current is controlled by a voltage applied to a gate, which is a **reverse-biased**.
- The fundamental difference between JFET and BJT devices: when the JFET junction is reverse-biased **the gate current is practically zero**, whereas the base current of the BJT is always some value greater than zero.


Figure: *n*-Channel JFET.

Basic structure of JFETs

- JFET is a high-input resistance device, while the BJT is comparatively low.
- If the channel is doped with a **donor impurity**, n-type material is formed and the channel current will consist of electrons.
- If the channel is doped with an **acceptor impurity**, p-type material will be formed and the channel current will consist of holes.
- N-channel devices have greater conductivity than p-channel types, since electrons have higher mobility than do holes; **thus n-channel JFETs are approximately twice as efficient conductors compared to their p-channel counterparts.**

Basic structure of JFETs

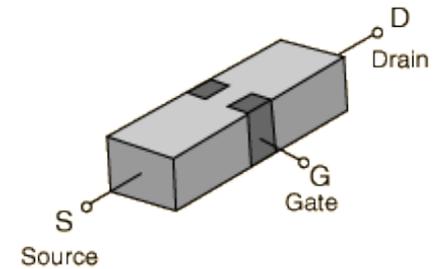
- In addition to the channel, a JFET contains two ohmic contacts: the **source** and the **drain**.
- The JFET will conduct current equally well in either direction and the source and drain leads are usually interchangeable.




The JFET - Labels

The terminals of a JFET are the source, gate, and drain.


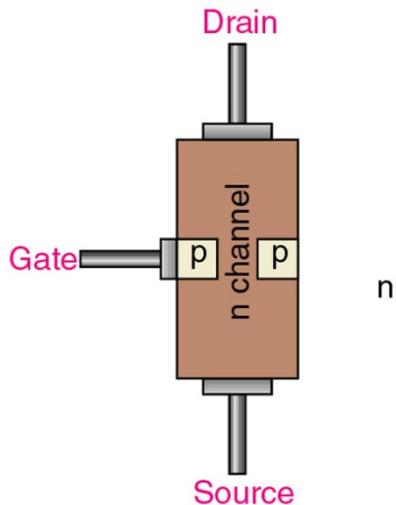
A JFET can be either p channel or n channel.



(a) n channel

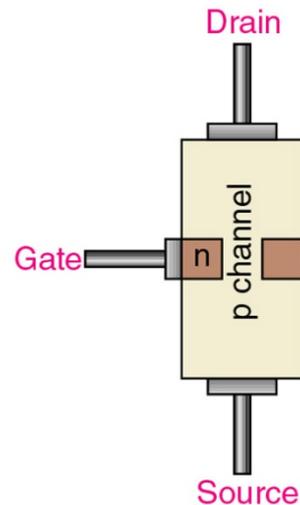


(b) p channel

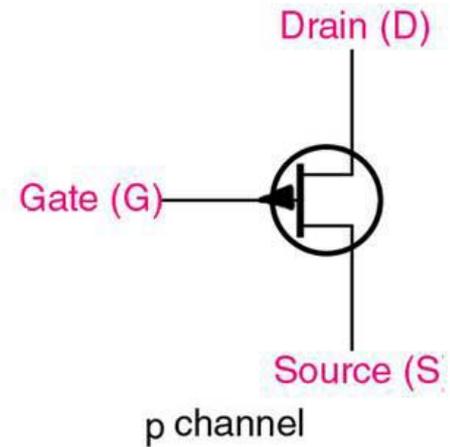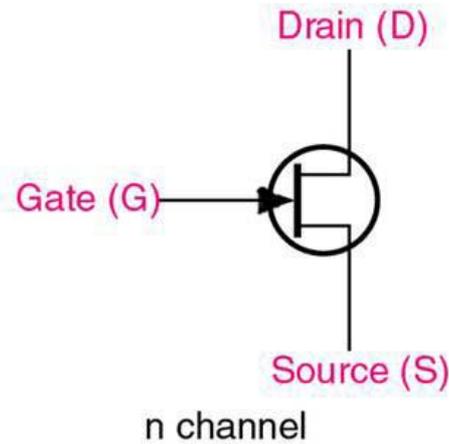

The JFET - Biasing

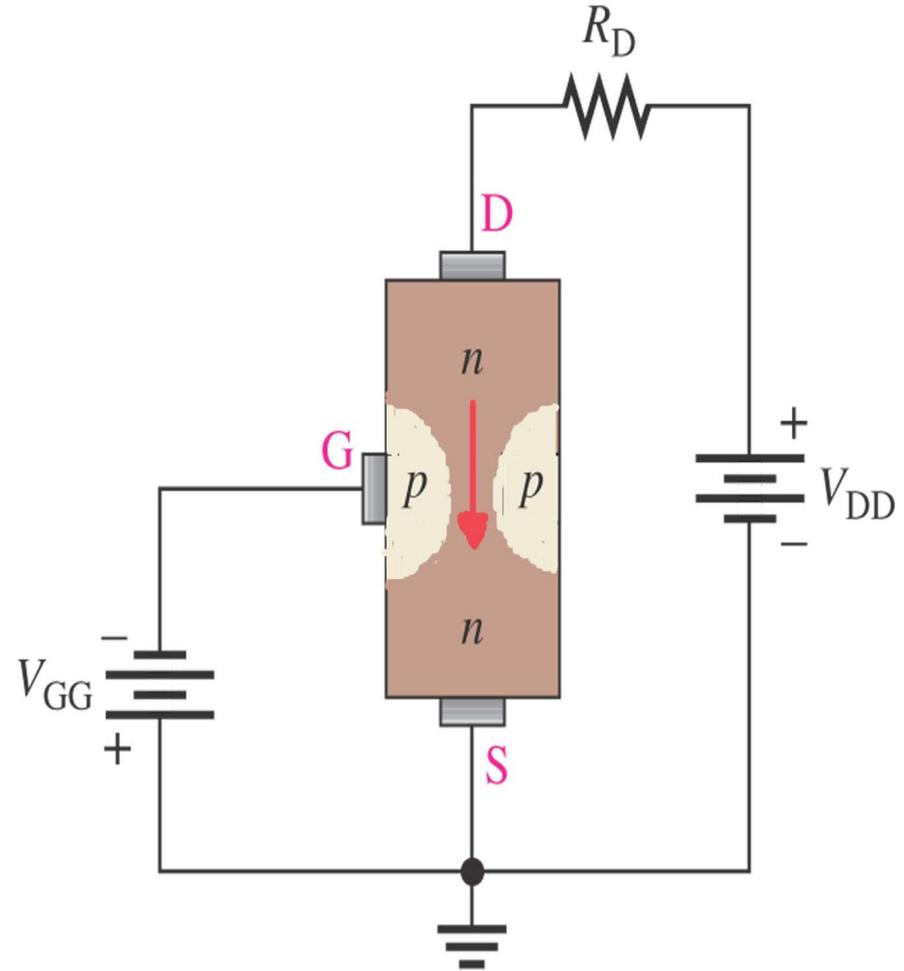- The “source-drain” current is controlled by a voltage field at the “gate”.
- That field is developed by the reverse biased gate-source junction (gate is connected to both sides).
- With more V_{GG} (reverse bias) the field grows larger.
- This field or resistance limits the amount of current flow through R_D .
- With low or no V_{GG} current flow is at maximum.





JFET Characteristics and Parameters Pinch-Off

The point when I_D ceases to increase regardless of V_{DD} increases (constant current source) is called the **pinch-off voltage** (point **B**) (*Note: $V_{GS} = 0$*).


This current is called maximum drain current (I_{DSS}).

Breakdown (point C) is reached when too much voltage is applied. This is undesirable, so JFETs operation is always well below this value.

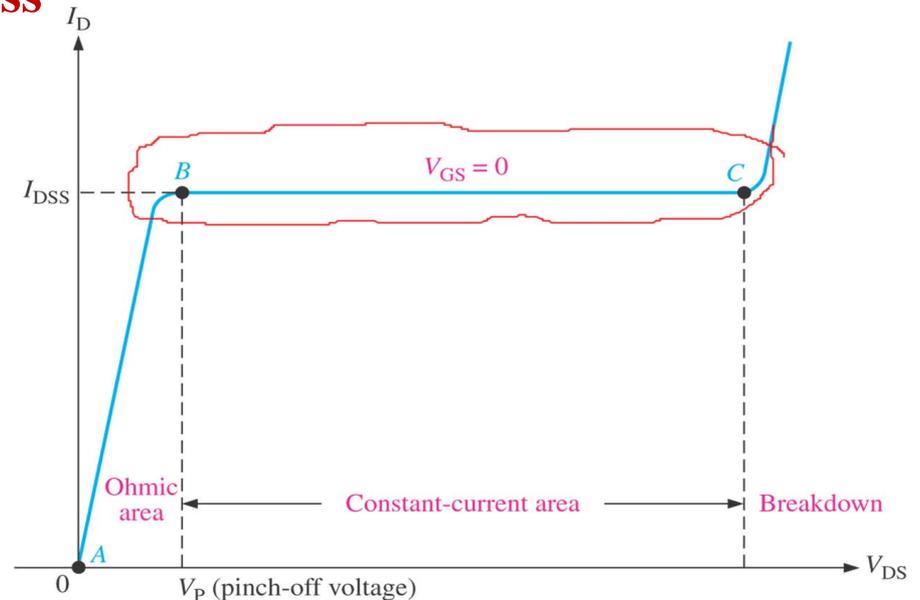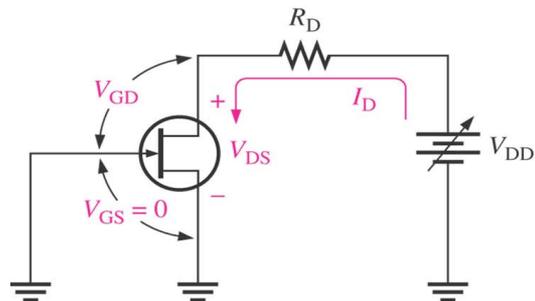Pinch off voltage V_p is the value of V_{ds} for $V_{gs} = 0V$ at which drain current I_d becomes constant i.e. I_{dss}



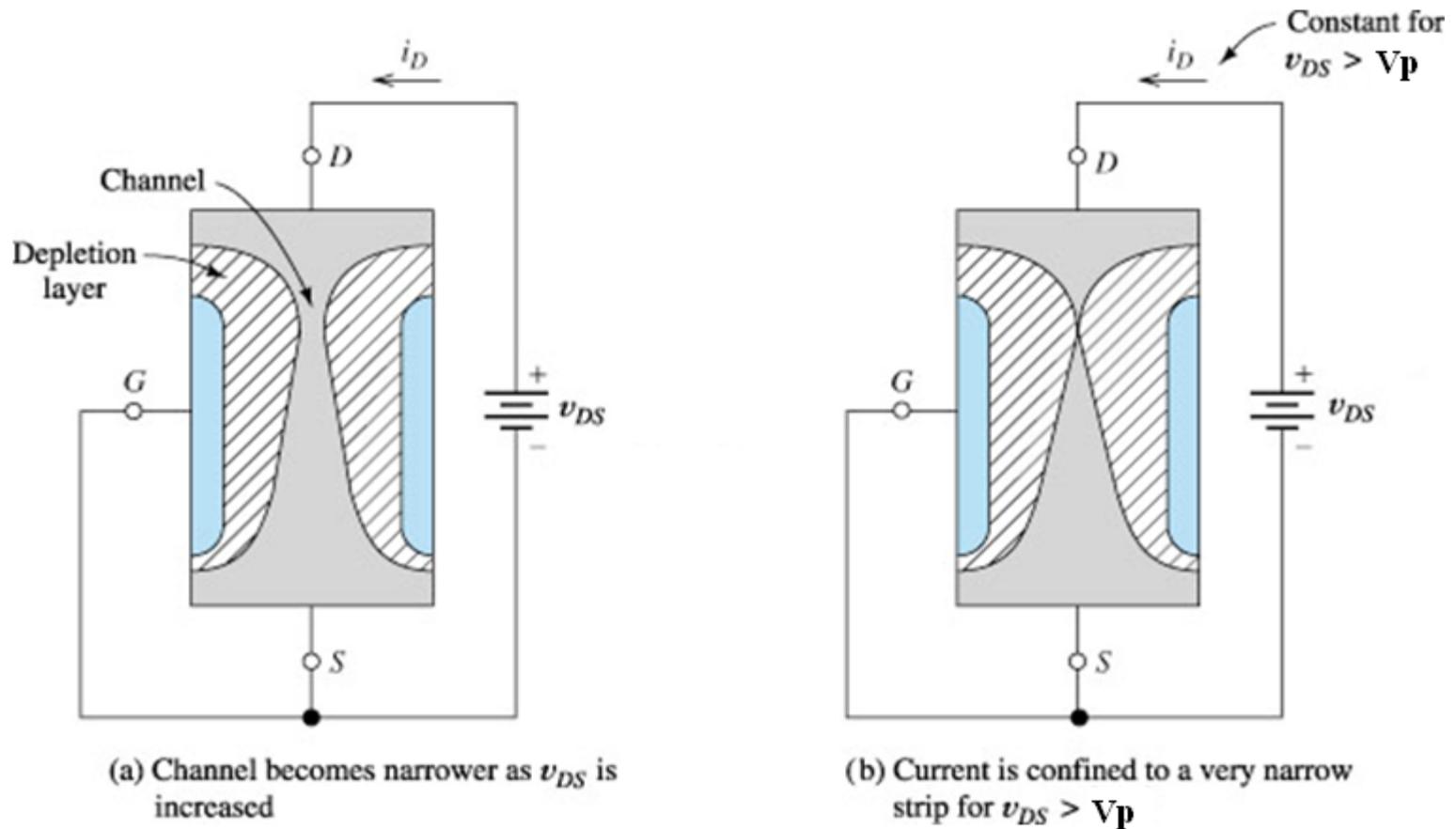JFET Characteristics and Parameters Pinch-Off




JFET Characteristics and Parameters Drain Curves


From this set of curves you can see increased negative voltage applied to the gate ($\downarrow -V_{GS}$) produces no change in I_D . I_D is limited and the pinch-off voltage (V_P) is reduced.

Note: V_{GS} controls I_{DSS}

This is the normal work zone for a JFET

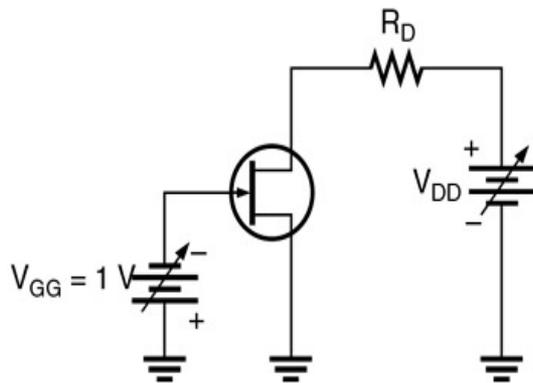


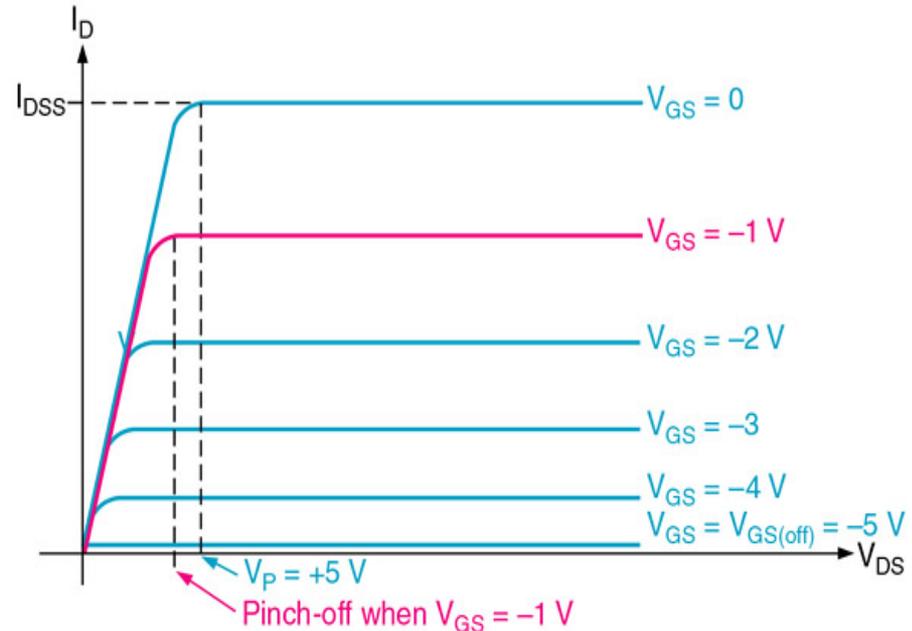(a) JFET biased at $V_{GS} = -1\text{ V}$



(b) Family of drain characteristic curves

Operation of a JFET

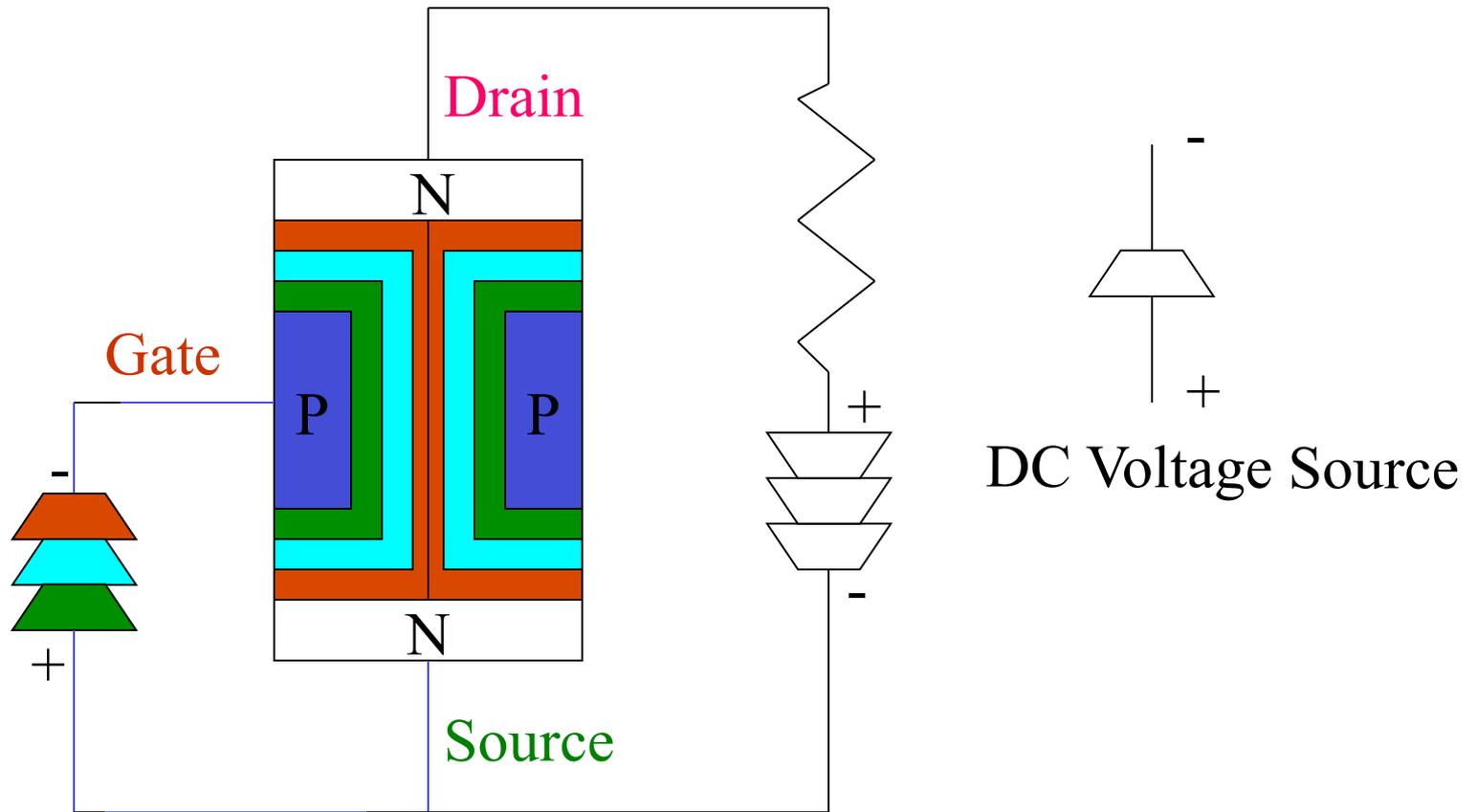

JFET Characteristics and Parameters Cutoff

We know that as V_{GS} is increased I_D will decrease.

The point that I_D ceases to increase is called cutoff.

The amount of V_{GS} required to do this is called the **cutoff voltage** (V_P).


The depletion region grows such that it allows practically no current to flow through.

Cutoff voltage is the value of V_{GS} called $V_{GS(off)}$ at which drain current I_D ceases to flow.

It is interesting to note that pinch-off voltage ($V_{GS(off)}$) and cutoff voltage (V_P) are the same value but opposite polarity.


Pinch-Off “ V_P ” vs Cutoff “ $V_{GS(off)}$ ”

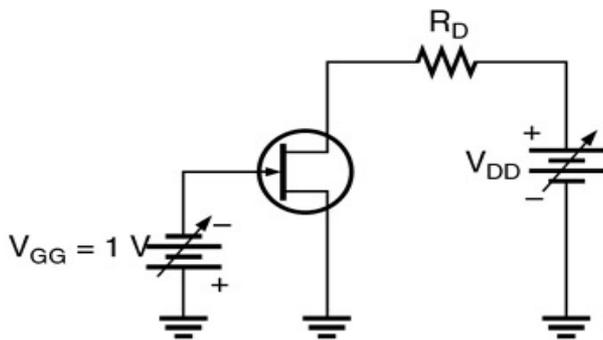- $V_{GS(off)}$ and V_P are always = and opposite is sign
- $V_{P(inch\ off)}$ - the value of V_{DS} where I_D becomes constant with $V_{GS} = 0$.
- $V_{P(inch\ off)}$ also occurs for $V_{DS} < V_P$ if $V_{GS} \neq 0$.
 Note: Although V_P is constant, V_{DSmin} where I_D is constant, varies.



(a) JFET biased at $V_{GS} = -1\text{ V}$

See Example 7-1

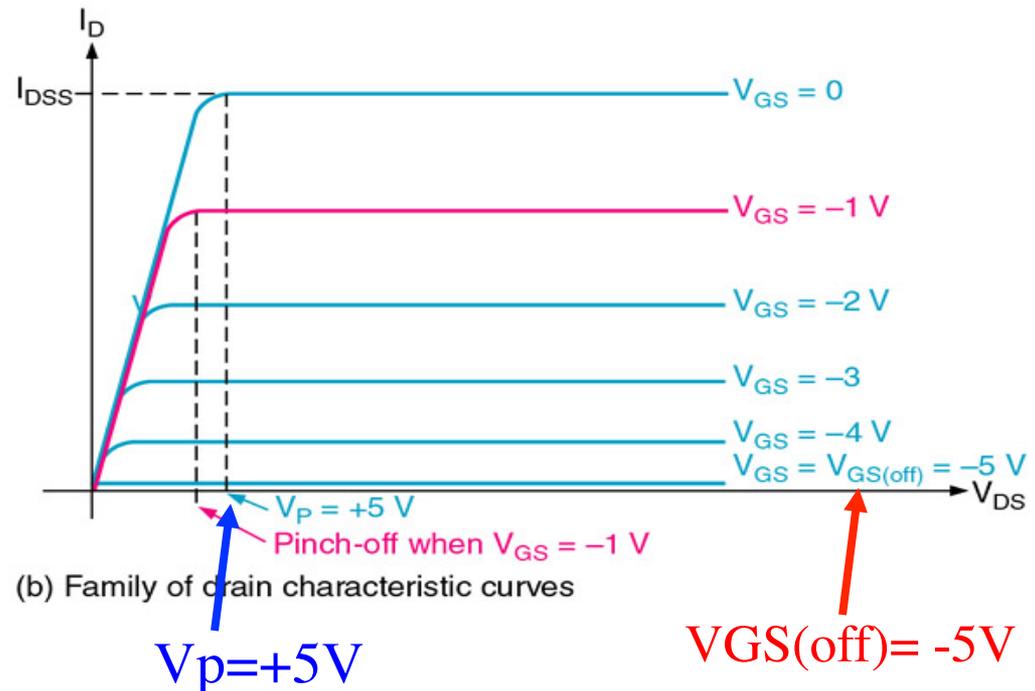

(b) Family of drain characteristic curves

JFET Characteristic

- **Output characteristic (Drain Characteristic).**

Curve drawn between I_D and Drain Source voltage V_{DS} with gate source voltage V_{GS} as parameter.

- **Transfer Characteristic.**

Curve between I_D and V_{GS}

Output or Drain (V_D - I_D) Characteristics of n-JFET

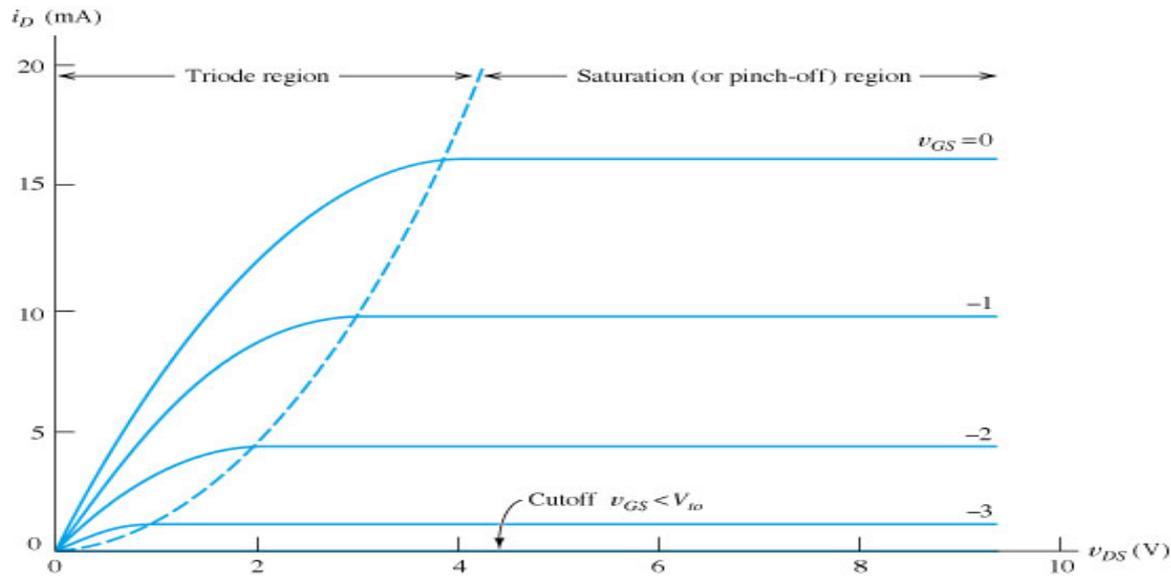
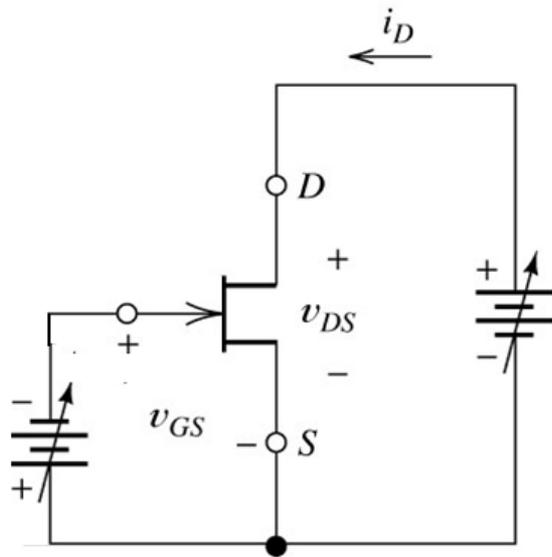


Figure: Circuit for drain characteristics of the n -channel JFET and its Drain characteristics.

N-Channel JFET Characteristics and Breakdown

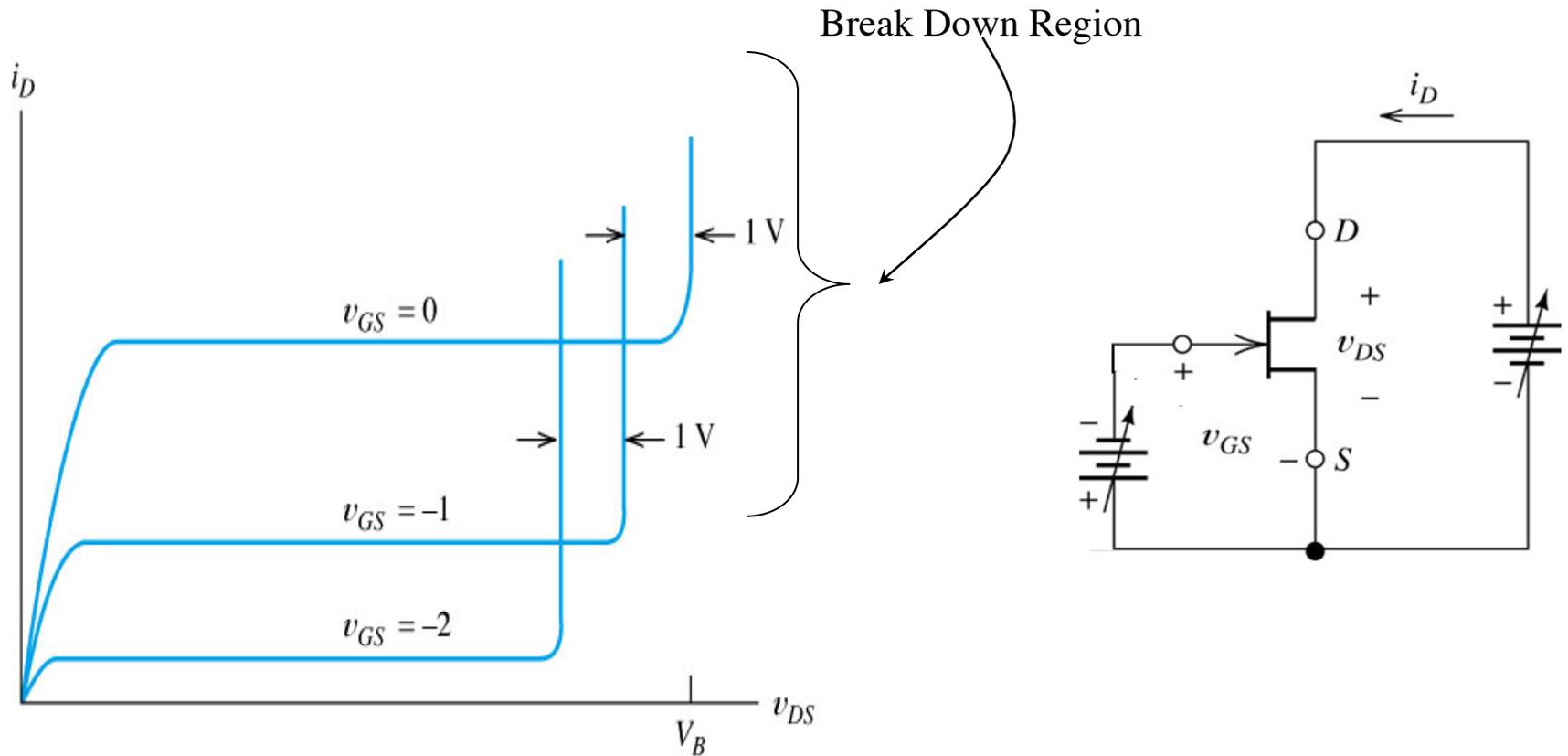


Figure: If v_{DS} exceeds the breakdown voltage V_B , drain current increases rapidly.

Regions of a JFET Operation

Cut-off region:

The transistor is off.

There is no conduction between the drain and the source when the gate-source voltage is greater than the cut-off voltage.

$$(I_D = 0 \text{ for } V_{GS} > V_{GS,off})$$

Active region (also called the Saturation region / Pinch off Region):

The transistor is on.

The drain current is controlled by the gate-source voltage (V_{GS}) and relatively insensitive to V_{DS} .

In this region the transistor can be an amplifier.

In the active region:

$$V_{DS} \geq (V_{GS} - V_P)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS,off}} \right)^2$$

Where, I_{DSS} is the short circuit drain current, V_P is the pinch off voltage

Ohmic region (Non Saturation Region) :

The transistor is on, but behaves as a voltage controlled resistor. When V_{DS} is less than in the active region, the drain current is roughly proportional to the source-drain voltage and is controlled by the gate voltage. In the ohmic region drain current is given by:

$$V_{DS} < (V_{GS} - V_P)$$

$$I_{DS} = \frac{2I_{DSS}}{V_P^2} \left[(V_{GS} - V_P)V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Where, I_{DSS} is the short circuit drain current, V_P is the pinch off voltage

Transfer Characteristics of n-Channel JFET

The *transfer characteristic curve* illustrates the control V_{GS} has on I_D from cutoff ($V_{GS(off)}$) to pinch-off (V_P). Note the parabolic shape. The formula below can be used to determine drain current.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$

Note: ($V_{GS} = 0$ to $V_{GS(off)}$ controls I_D)


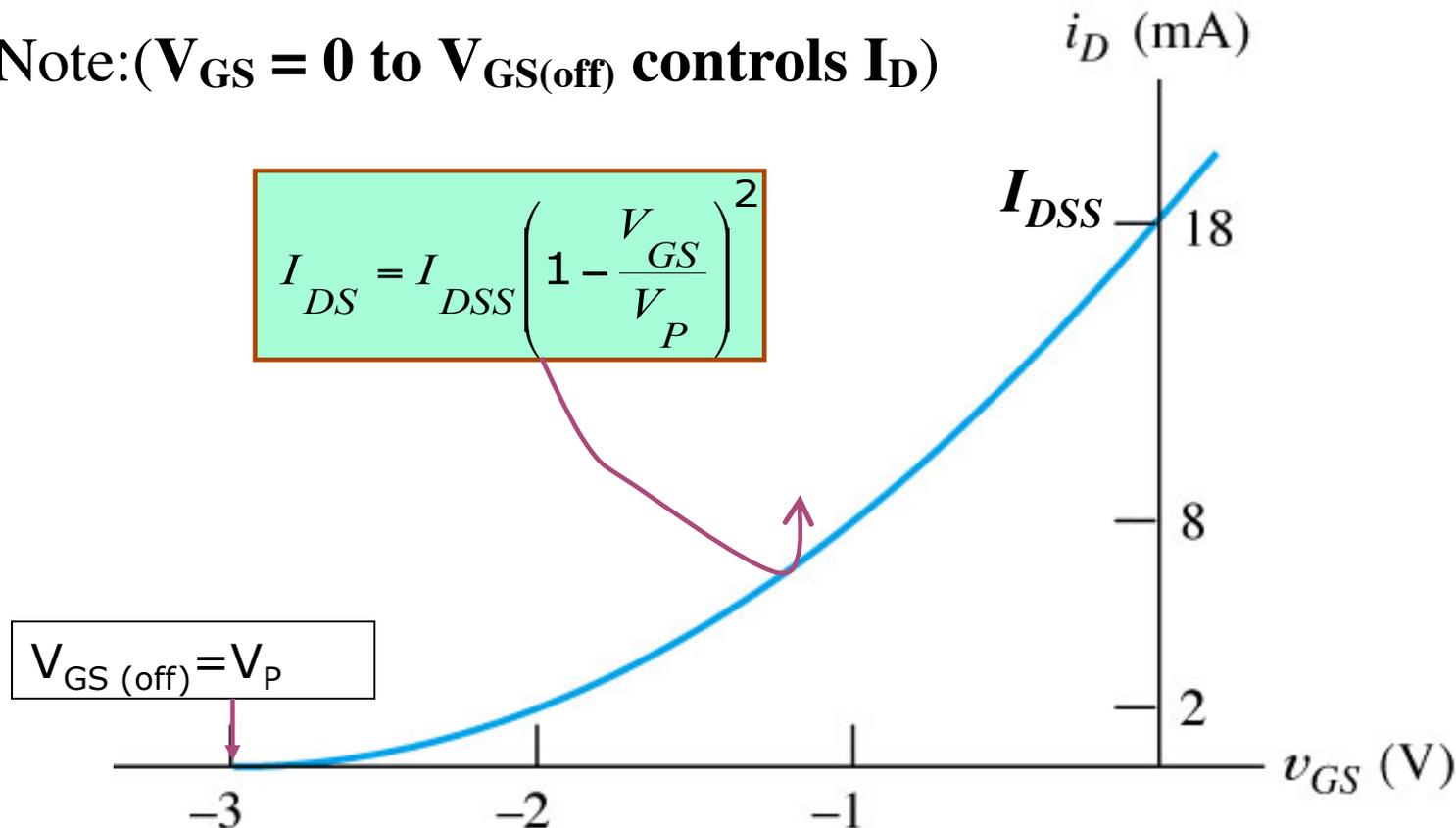


Figure: Transfer Characteristics of n-Channel JFET

JFET Transfer Curve

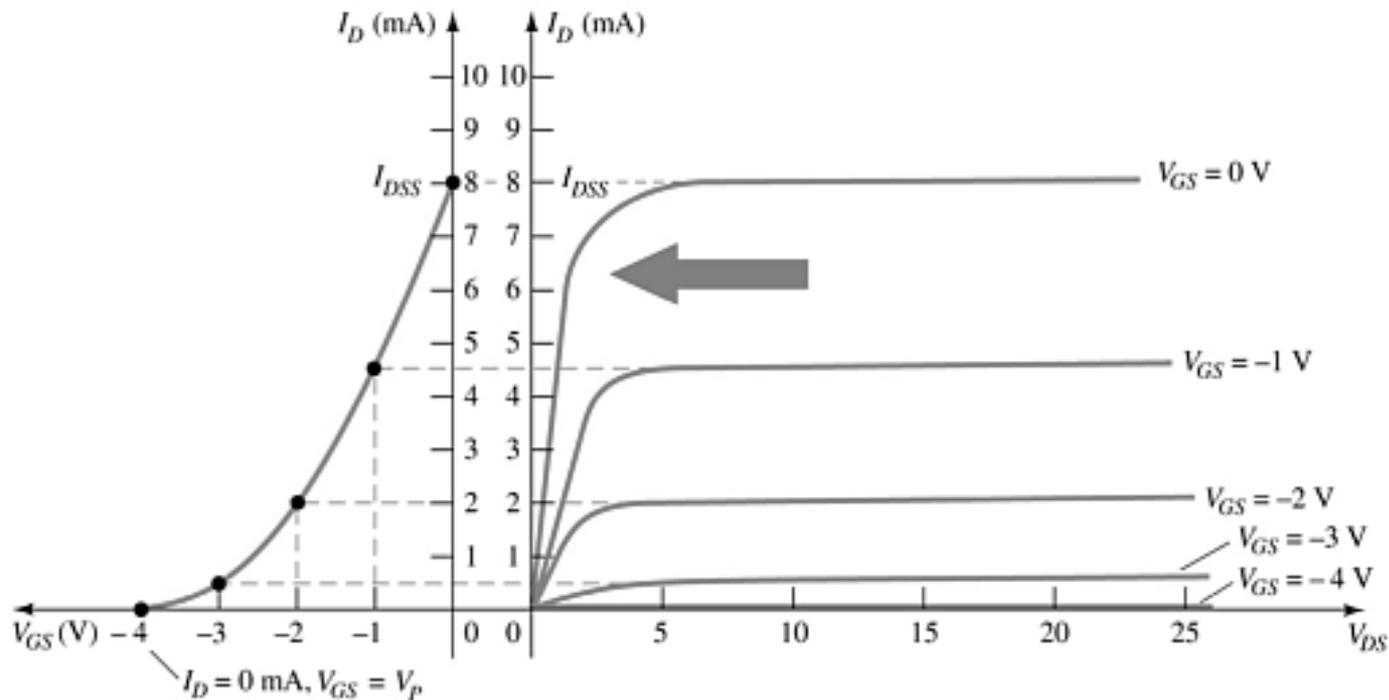This graph shows the value of I_D for a given value of V_{GS}



JFET Characteristics and Parameters

I_{DSS} : Drain Source Saturation Current

Signifies the drain saturation current when $V_{GS} = 0V$.

Dynamic Drain Resistance at an operating point is the ratio of changes of V_{DS} to I_D keeping the gate source voltage constant. Large changes in V_{DS} produce very small changes in I_D .

$$r_d = \Delta V_{DS} / \Delta I_D \text{ (for constant } V_{GS})$$

Drain resistance is the AC resistance between the drain and the source terminals when the JFET is operating in the pinch off region.

It is the output resistance of the diode.


JFET Characteristics and Parameters

Forward transfer conductance (g_m) (*Forward Transconductance*).

Transconductance at an operating point is defined as the ratio of small change in drain current I_D to the small change in V_{GS} keeping drain voltage constant.

$$g_m = \Delta I_D / \Delta V_{GS} \quad \text{for constant } V_{ds}$$

It is measured in Siemens (S)

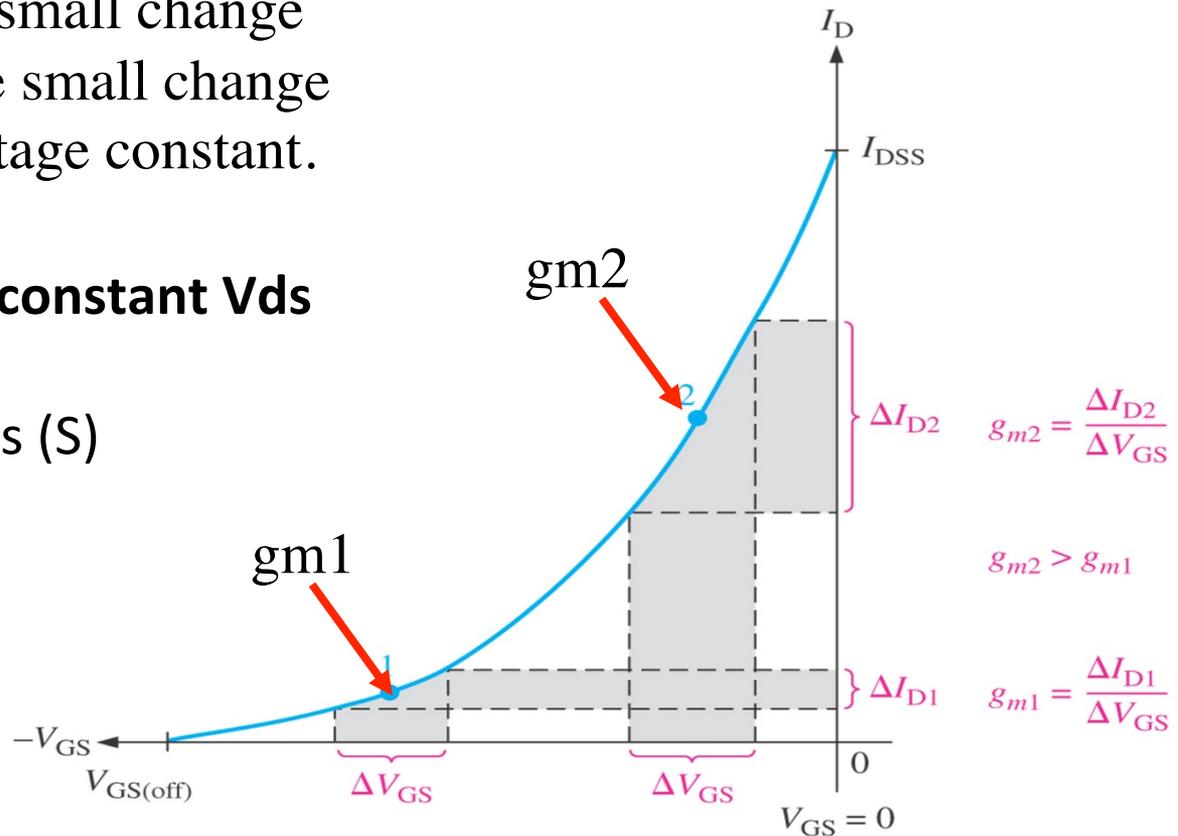

JFET Characteristics and Parameters

Input resistance for a JFET is high since the gate-source junction is reverse-biased.

$$R_{IN} = |V_{GS} / I_{GSS}|$$

where: I_{GSS} is the "gate reverse current"
@ a certain "gate-to-source" voltage.

Gate Cutoff Current or Gate Reverse Current (I_{GSS}):

The gate channel junction in a JFET is reverse biased, a minority charge carrier current flows called as Gate Source cutoff current or Gate reverse current.

JFET Characteristics and Parameters

Amplification Factor is defined as the ratio of small change in drain voltage V_{DS} to the small change in gate voltage V_{GS} when drain current I_D is kept constant.

$$\mu = \Delta V_{DS} / \Delta V_{GS} \quad \text{for constant } I_D$$

$$\mu = r_d g_m$$

JFET Characteristics and Parameters

Breakdown Voltage :

BV_{DGO} : Drain gate breakdown voltage with the source terminal open circuited.

BV_{GSS} : Gate source breakdown voltage with drain terminal shorted to the source.


Both are specifications of the voltage at which the gate channel junctions might breakdown.

Biasing Circuits used for JFET

- Fixed bias circuit
- Self bias circuit
- Potential Divider bias circuit

JFET (n-channel) Biasing Circuits

Fixed-bias
[JFET or D-MOSFET]

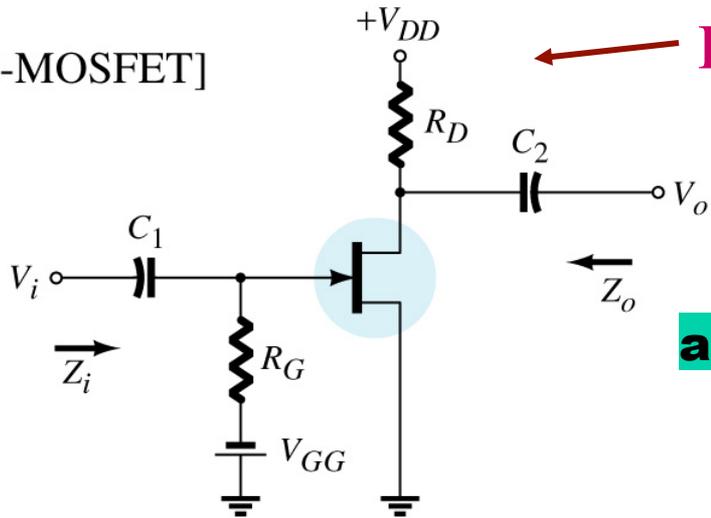

For Fixed Bias Circuit

Applying KVL to gate circuit we get

$$V_{GG} = I_G R_G + V_{GS} = V_{GS} = \text{Fixed}, \because I_G = 0$$


and

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\text{and } V_{DS} = V_{DD} - I_{DS} R_D$$

Where, $V_p = V_{GS\text{-off}}$ & I_{DSS} is Short ckt. I_{DS}

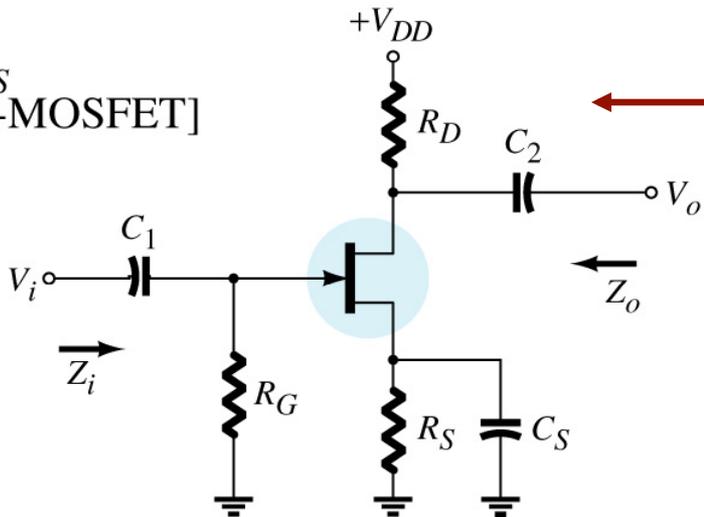Self-bias
bypassed R_S
[JFET or D-MOSFET]




For Self Bias Circuit

$$V_{GS} + I_{DS} R_S = 0$$

$$\therefore I_{DS} = -\frac{V_{GS}}{R_S}$$

JFET Biasing Circuits Count...

Gate Bias: or Fixed Bias Ckt.

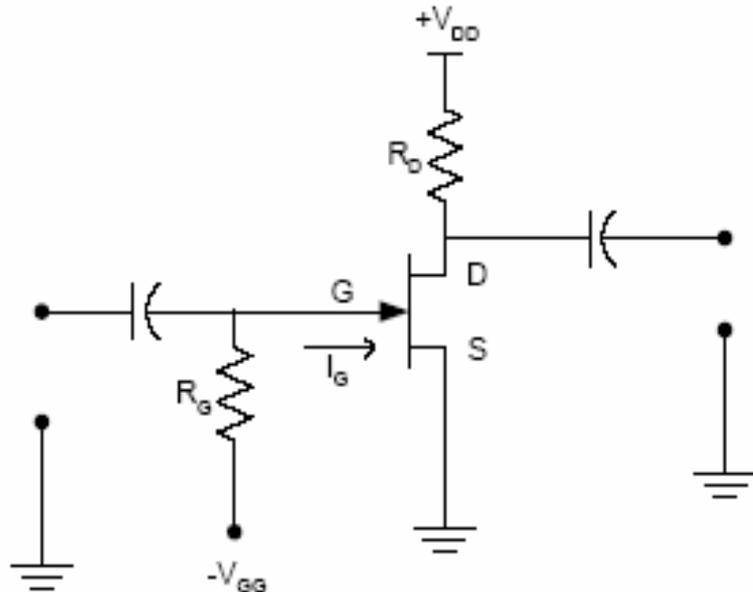

Since $I_G = 0$,

$$V_{GS} = V_{GG}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$


- Example: Determine the Q-point values for the gate biasing circuit if $V_{GG} = -0.5 \text{ V}$, $V_{GS(off)} = -7 \text{ V}$, $I_{DSS} = 9 \text{ mA}$, $V_{DD} = 5 \text{ V}$ and $R_D = 500 \Omega$.

$$I_D = (9 \text{ mA}) \left(1 - \frac{-0.5}{-7}\right)^2$$

$$= 7.76 \text{ mA}$$


$$V_{DS} = 5 - (7.76 \text{ mA})(500)$$

$$= 1.12 \text{ V}$$

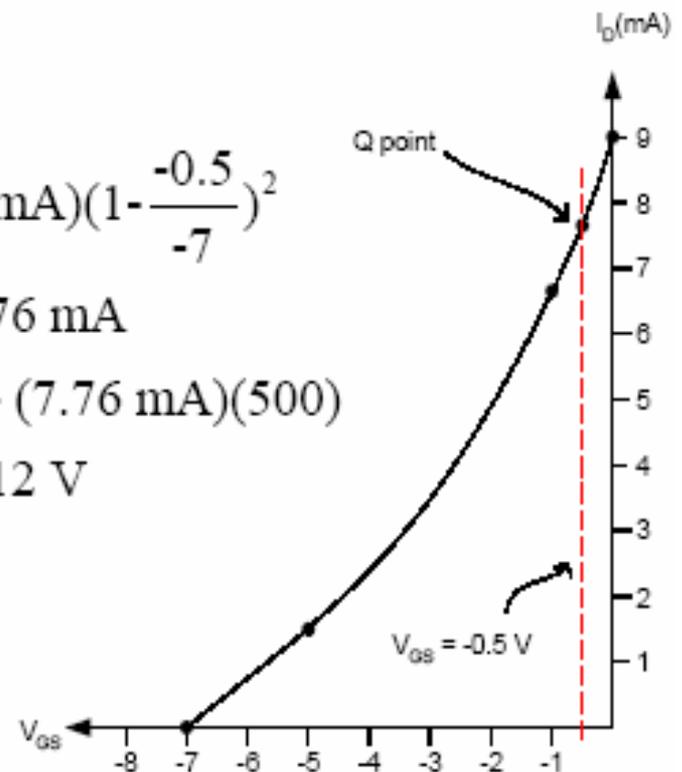

JFET Self (or Source) Bias Circuit

Self bias:

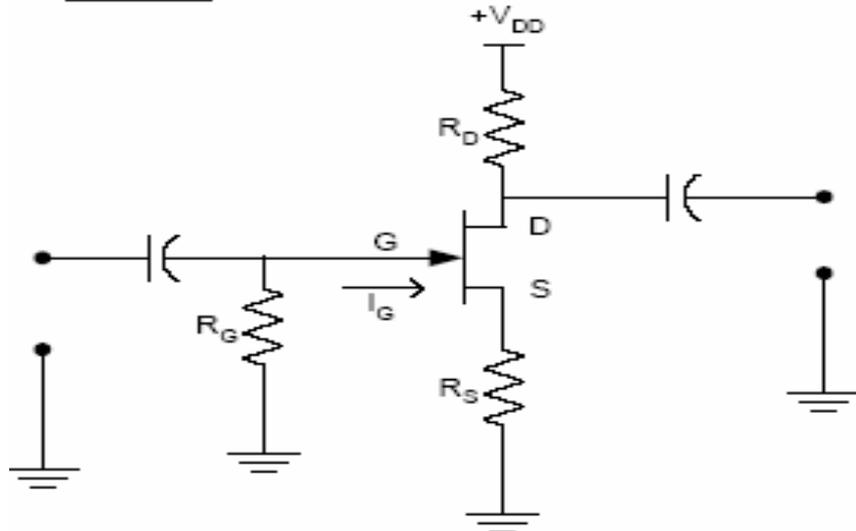

Since $I_G = 0$, $V_G = 0$

$$V_S = I_D R_S$$


$$I_D = \frac{-V_{GS}}{R_S}$$

$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$\text{and } I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

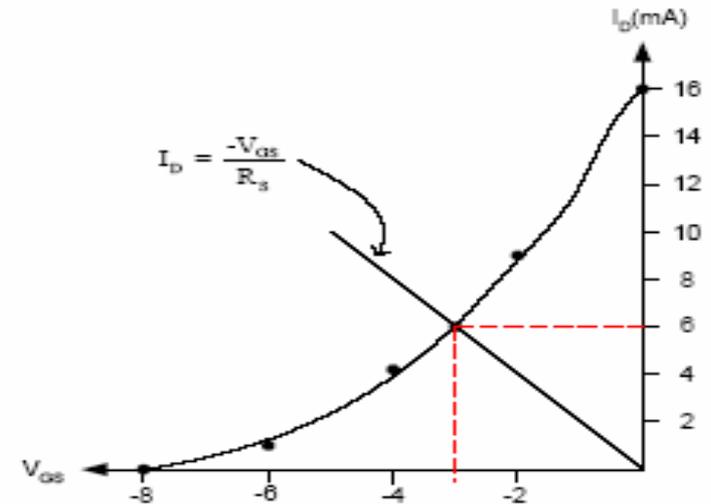- Example:** Determine the Q-point values for the self biasing circuit if $V_{GS(off)} = -8 \text{ V}$, $I_{DSS} = 16 \text{ mA}$, $V_{DD} = 10 \text{ V}$, $R_D = 500 \text{ } \Omega$, $R_G = 1 \text{ M}\Omega$ and $R_S = 500 \text{ } \Omega$.



$$I_D = 6 \text{ mA}$$


$$V_{DS} = 10 - (6\text{mA})(500+500) = 4 \text{ V}$$

$$I_{DSS} \left[1 - 2 \frac{V_{GS}}{V_P} + \left(\frac{V_{GS}}{V_P} \right)^2 \right] + \frac{V_{GS}}{R_S} = 0$$

This quadratic equation can be solved for V_{GS} & I_{DS}

The Potential (Voltage) Divider Bias

Voltage-divider bias:

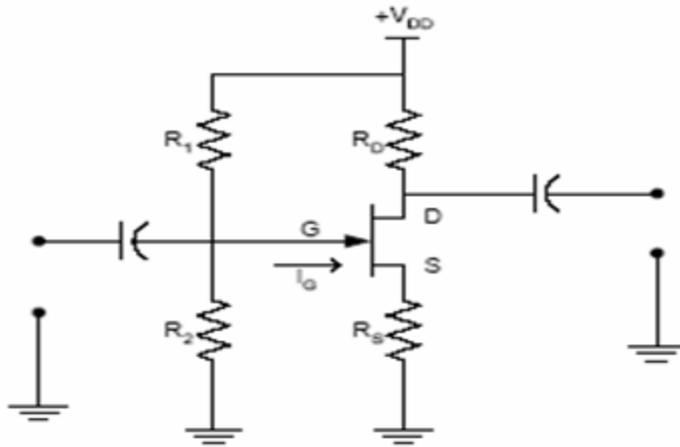

Since $I_G = 0$,


$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$

$$\therefore I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 - \frac{V_G - V_{GS}}{R_S} = 0$$

Solving this quadratic equation gives V_{GS} and I_{DS}

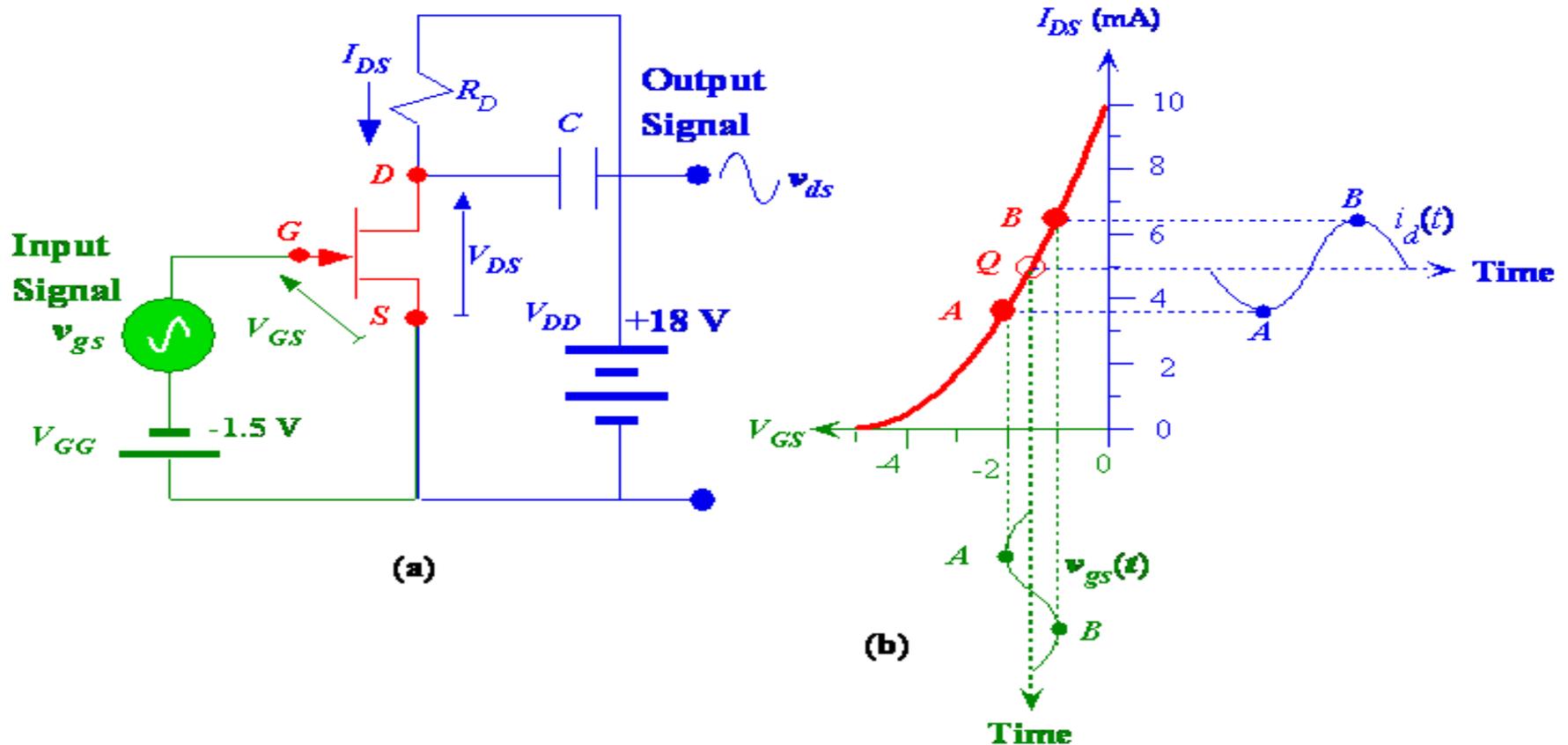A Simple CS Amplifier and Variation in I_{DS} with V_{GS}



(a) Common source (CS) ac amplifier using a JFET.

(b) Explanation of how I_D is modulated by the signal v_{gs} in series with the dc bias voltage V_{GG}

MOSFET

METAL OXIDE SEMICONDUCTOR FET

IGFET (INSULATED GATE FET)

- Importance for LSI/VLSI
 - Low fabrication cost
 - Small size
 - Low power consumption
- Applications
 - Microprocessors
 - Memories
 - Power Devices
- Basic Properties
 - Unipolar device
 - Very high input impedance
 - Capable of power gain
 - 3/4 terminal device, G, S, D, B
 - Two possible device types: enhancement mode; depletion mode
 - Two possible channel types: n-channel; p-channel

ENHANCEMENT MOSFET

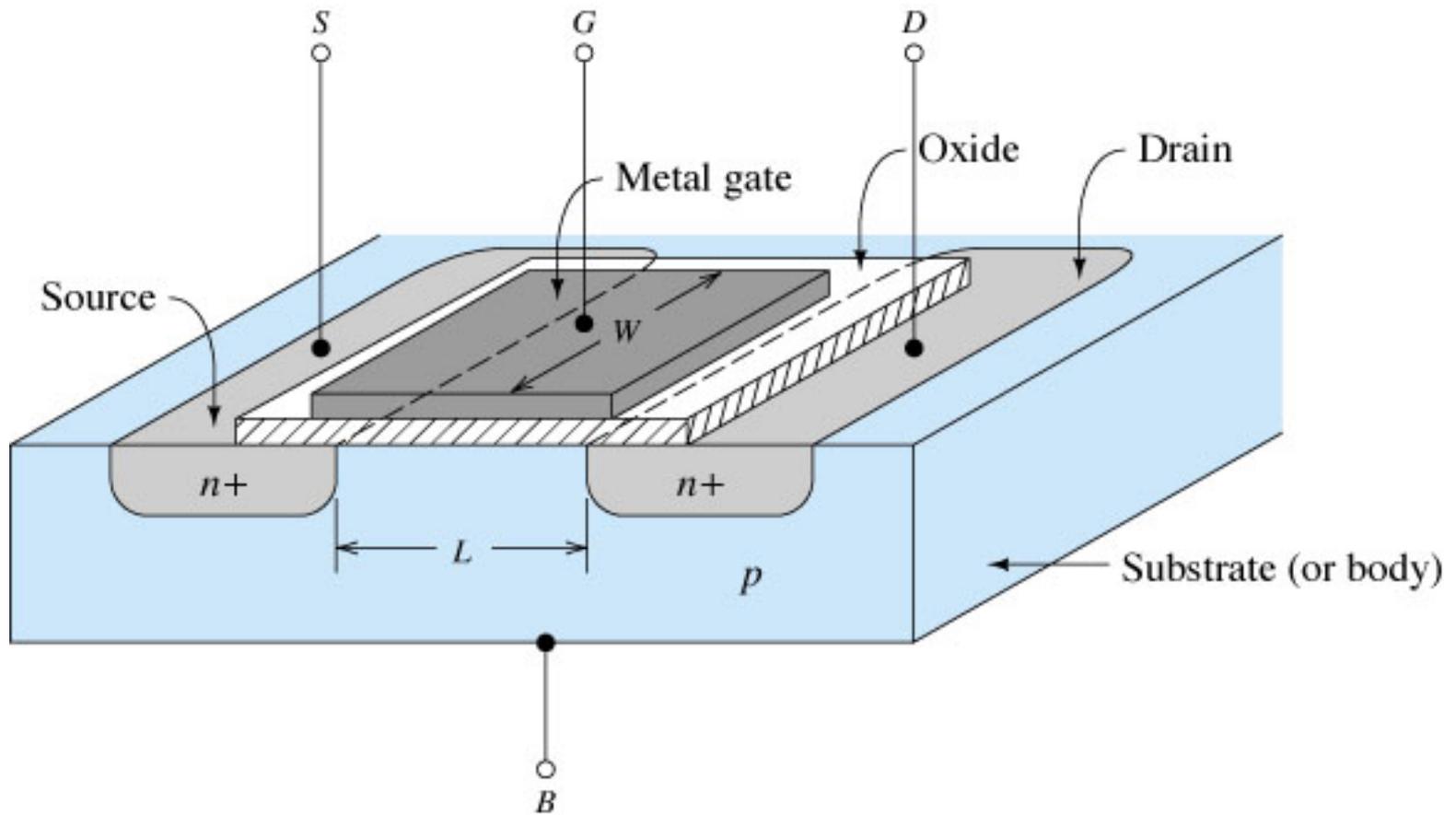


Figure: n -Channel Enhancement MOSFET showing channel length L and channel width W .

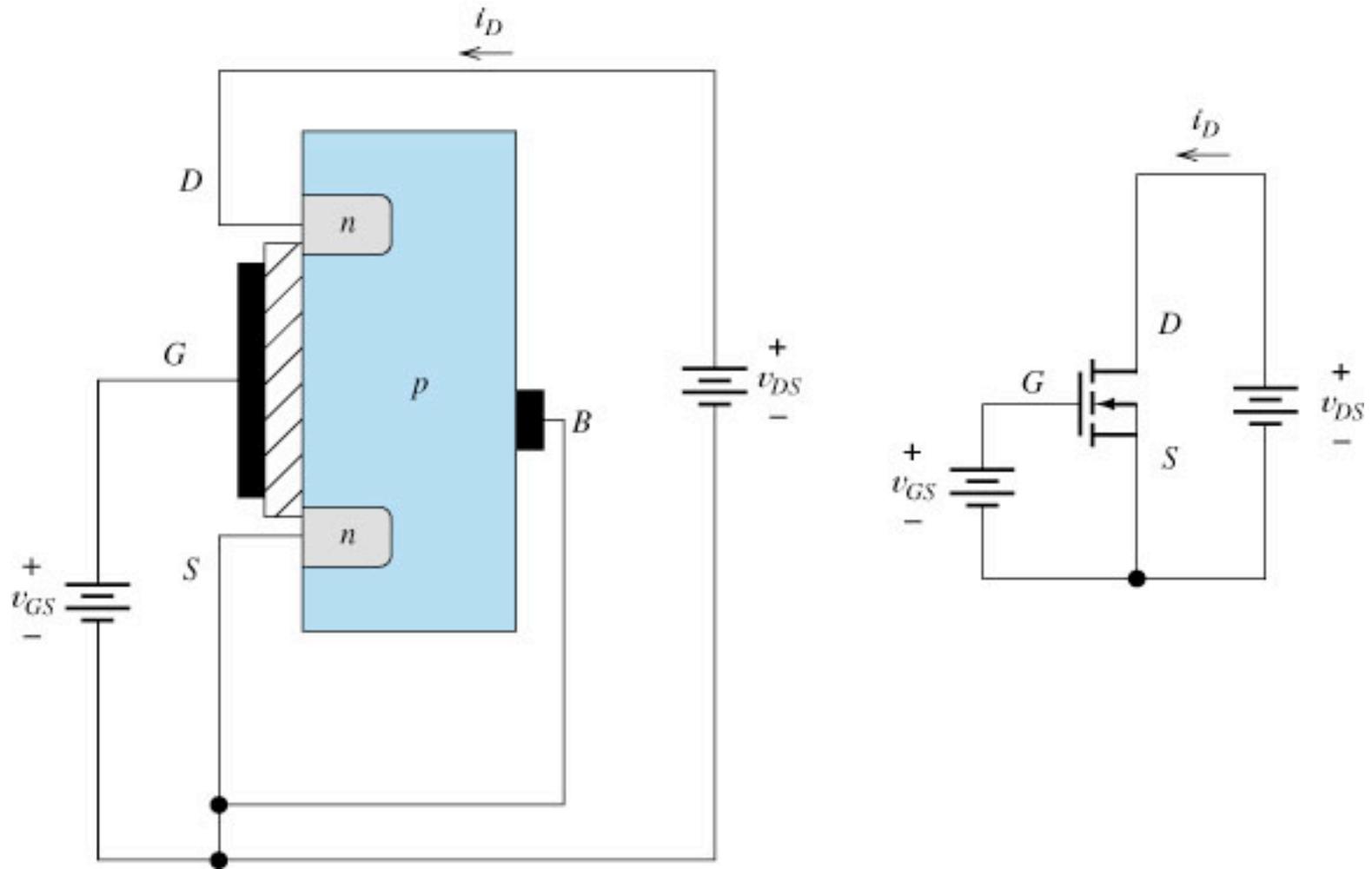


Figure: For $v_{GS} < V_{to}$ the pn junction between drain and body is reverse biased and $i_D=0$.

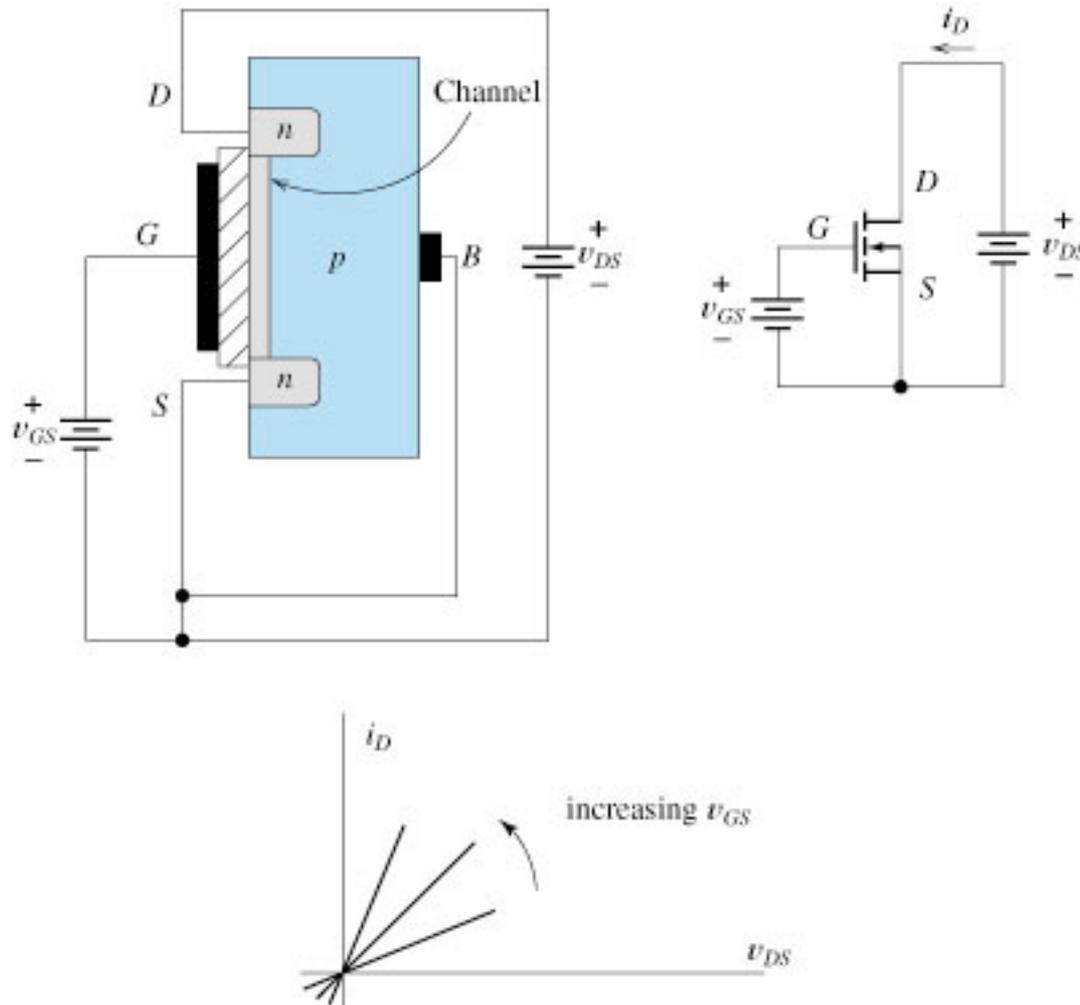


Figure: For $v_{GS} > V_{to}$ a channel of n -type material is induced in the region under the gate. As v_{GS} increases, the channel becomes thicker. For small values of v_{DS} , i_D is proportional to v_{DS} . The device behaves as a resistor whose value depends on v_{GS} .



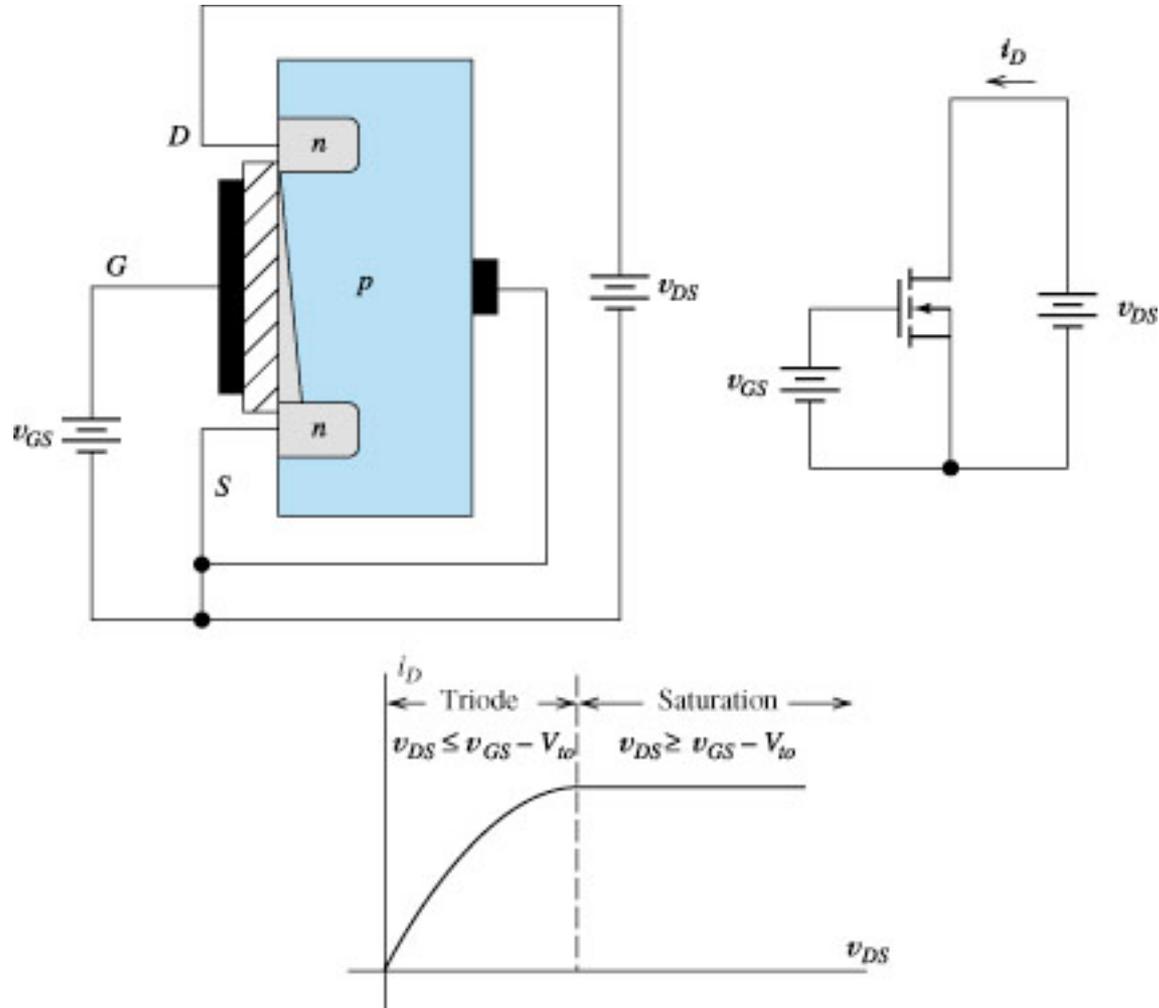


Figure: As v_{DS} increases, the channel pinches down at the drain end and i_D increases more slowly. Finally for $v_{DS} > v_{GS} - V_{to}$, i_D becomes constant.

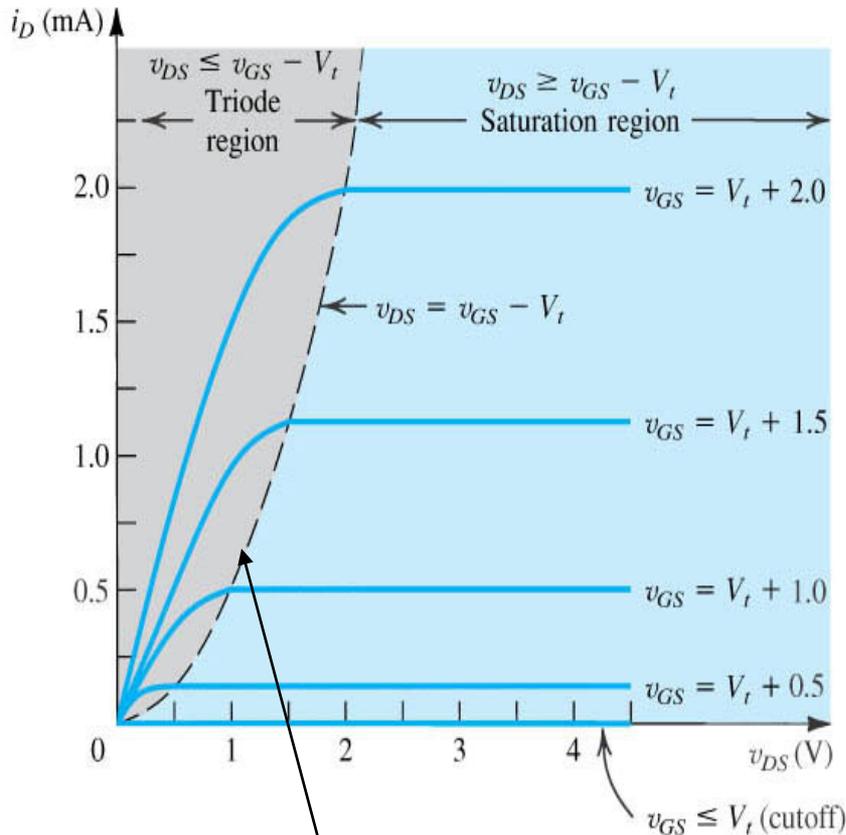Current-Voltage Relationship of n-EMOSFET



(b)

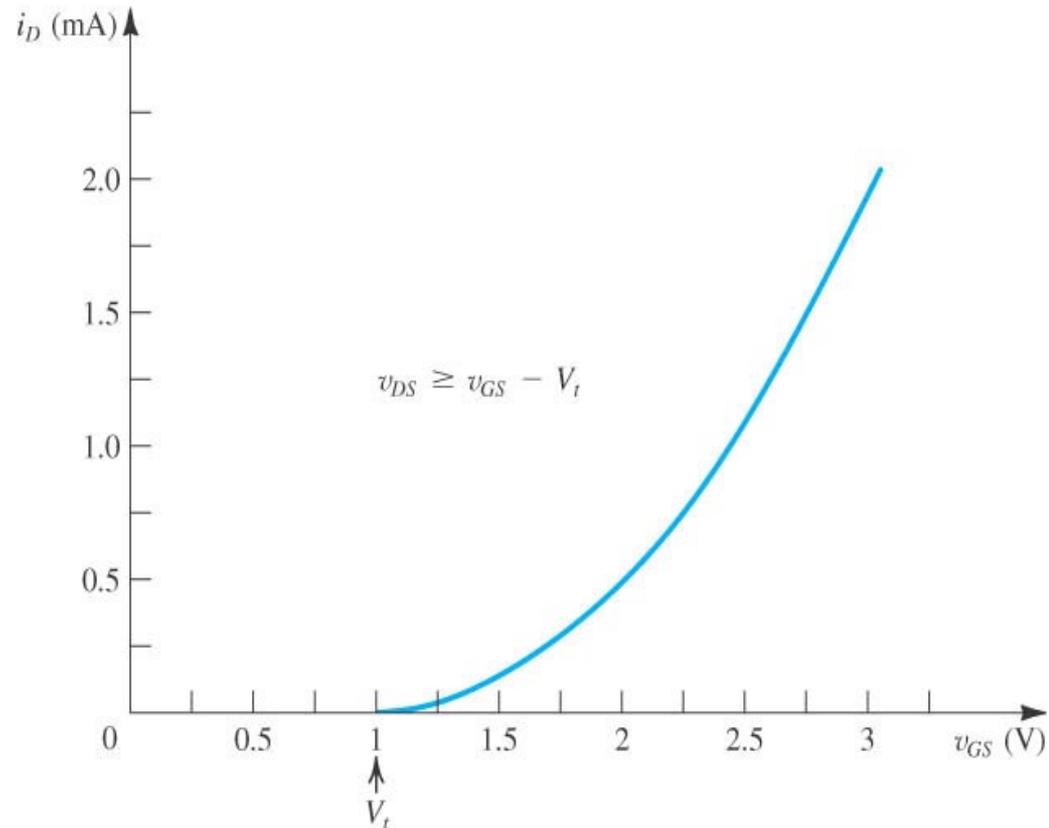

Locus of points where

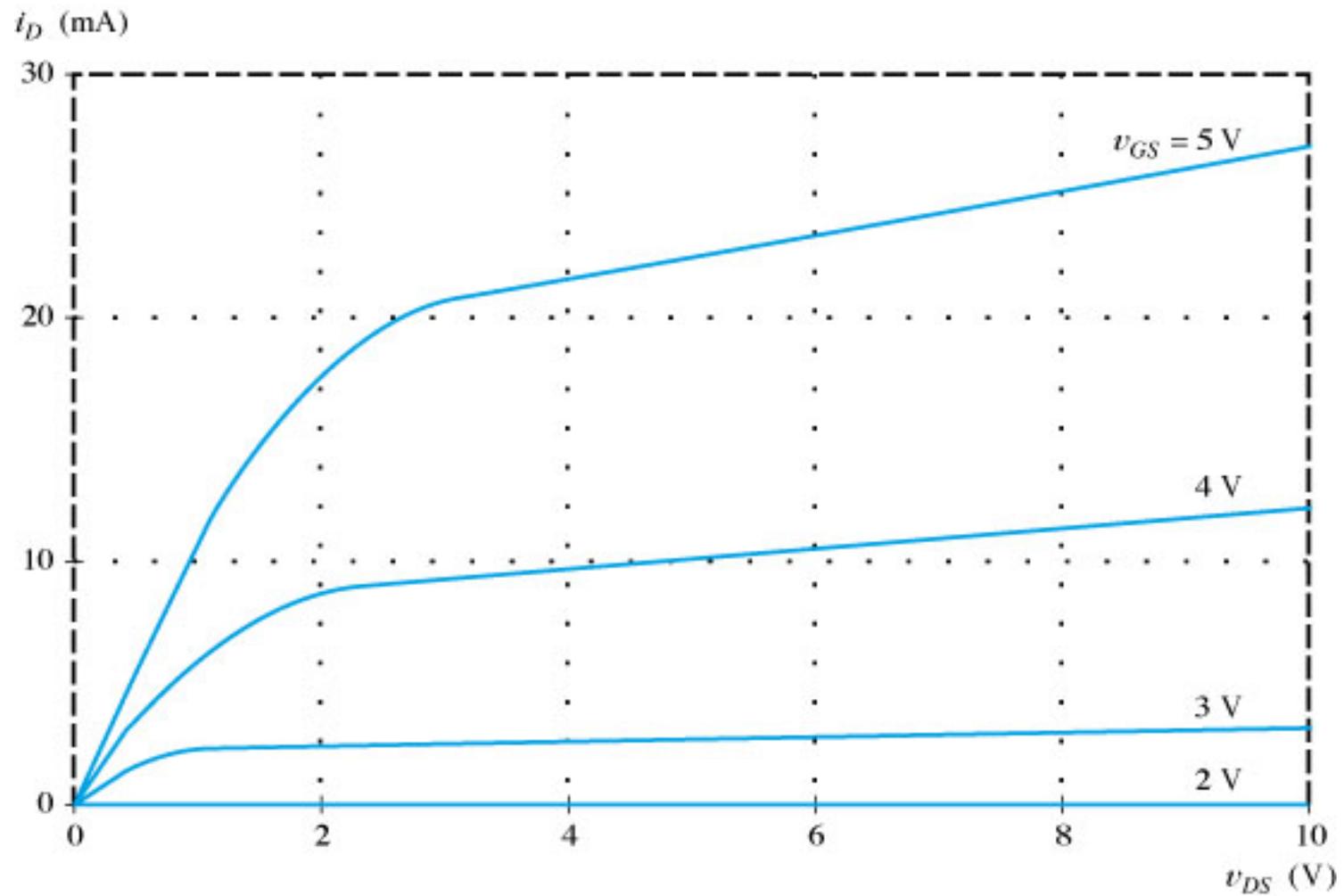


Figure: Drain characteristics

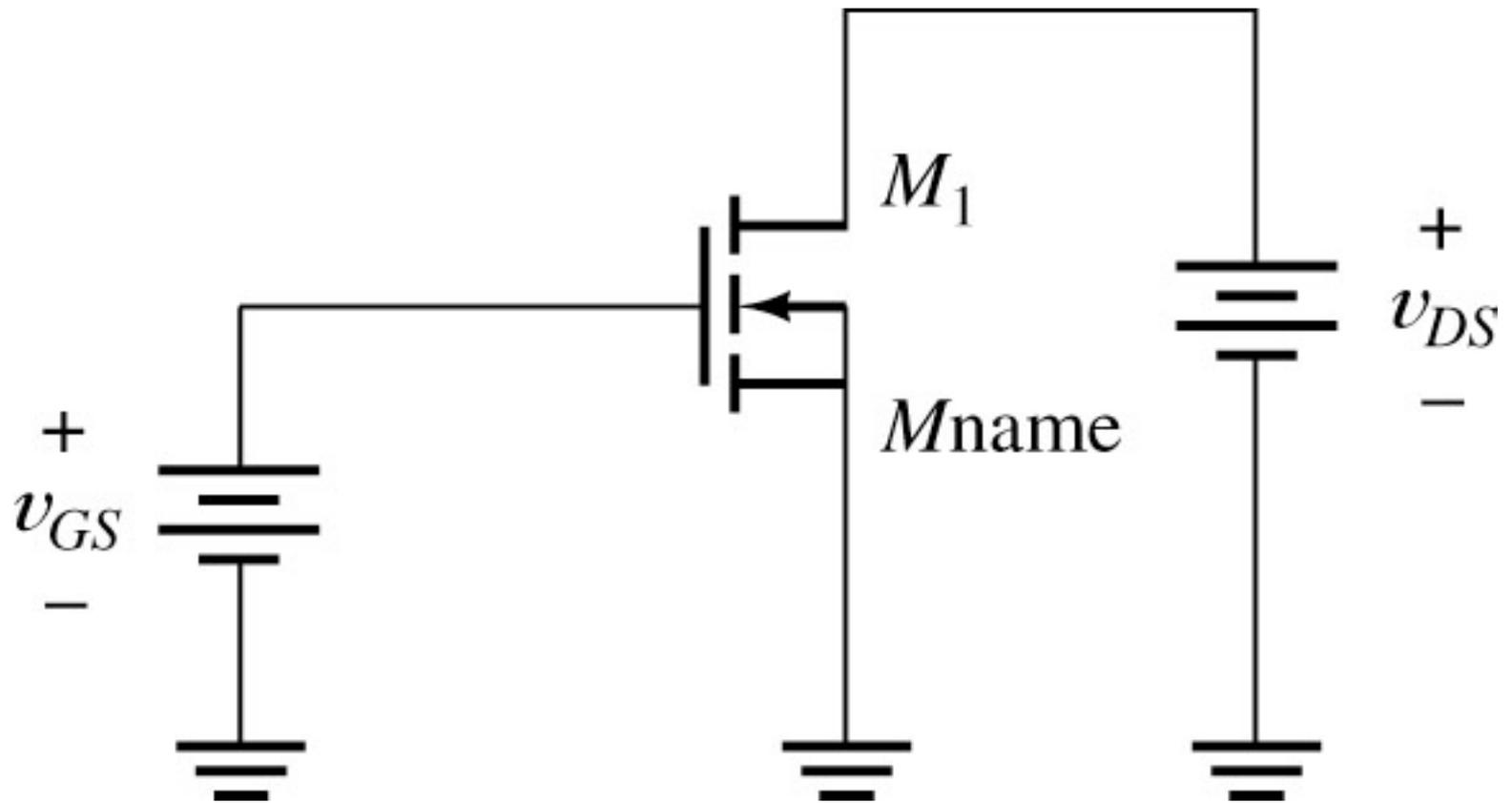


Figure: This circuit can be used to plot drain characteristics.

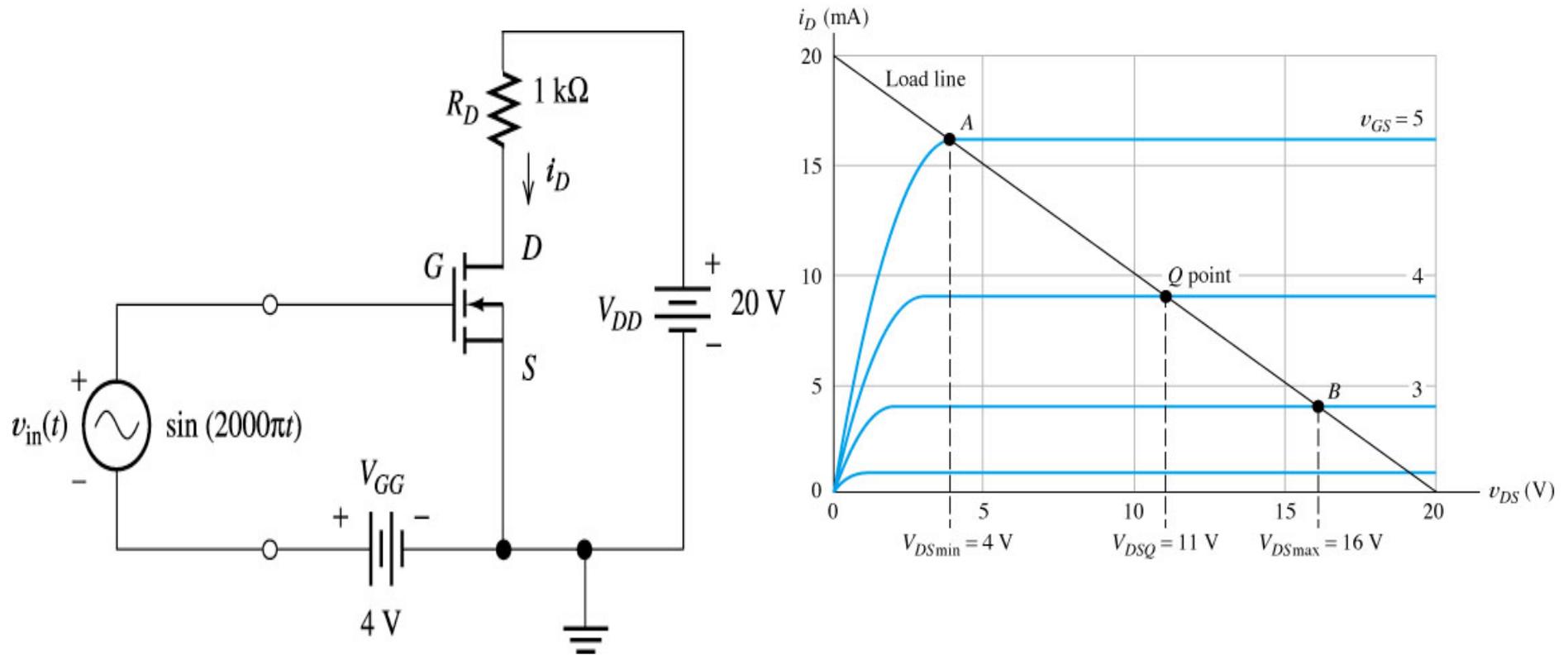


Figure: Simple NMOS amplifier circuit and Characteristics with load line.

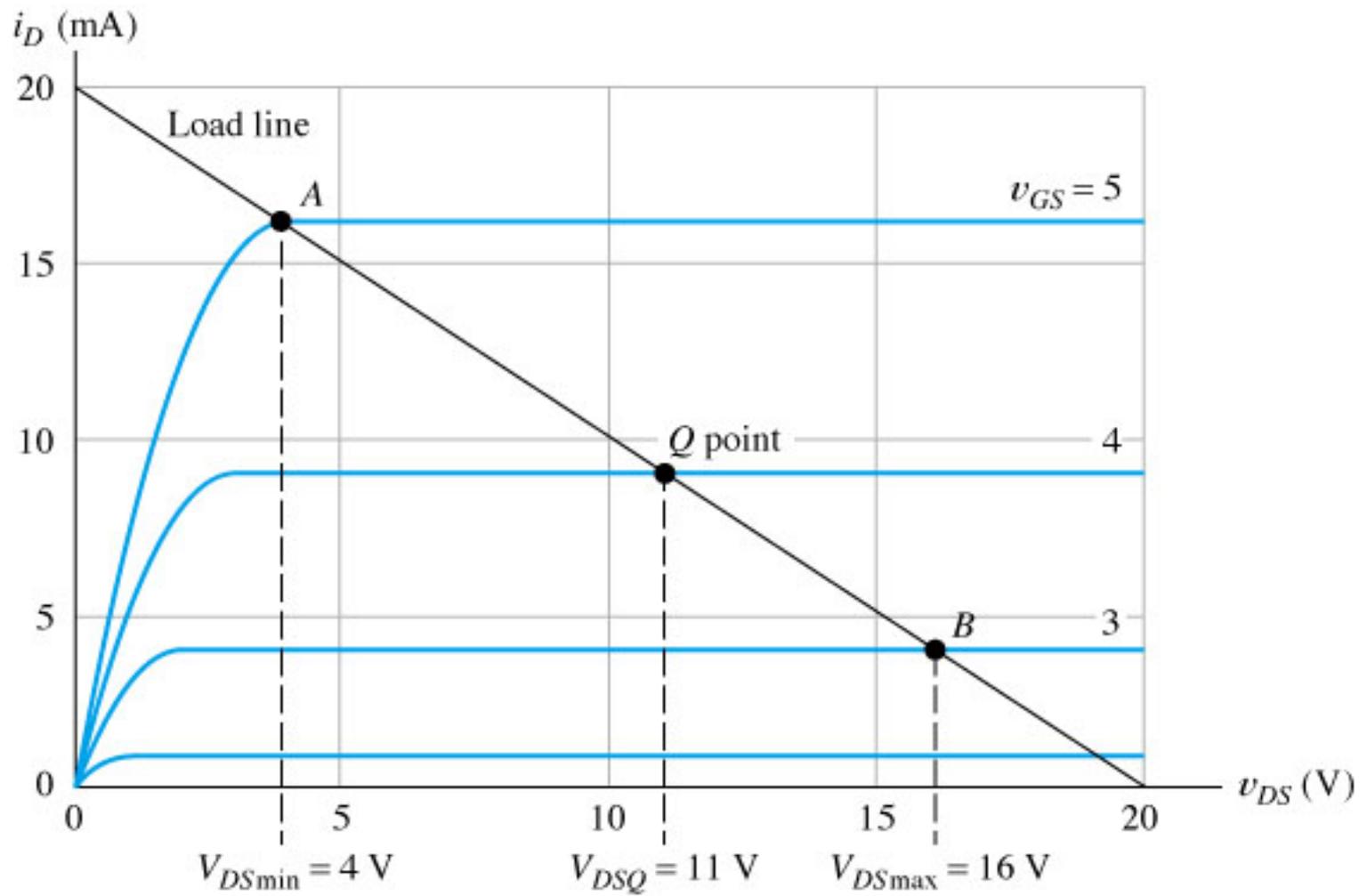


Figure: Drain characteristics and load line



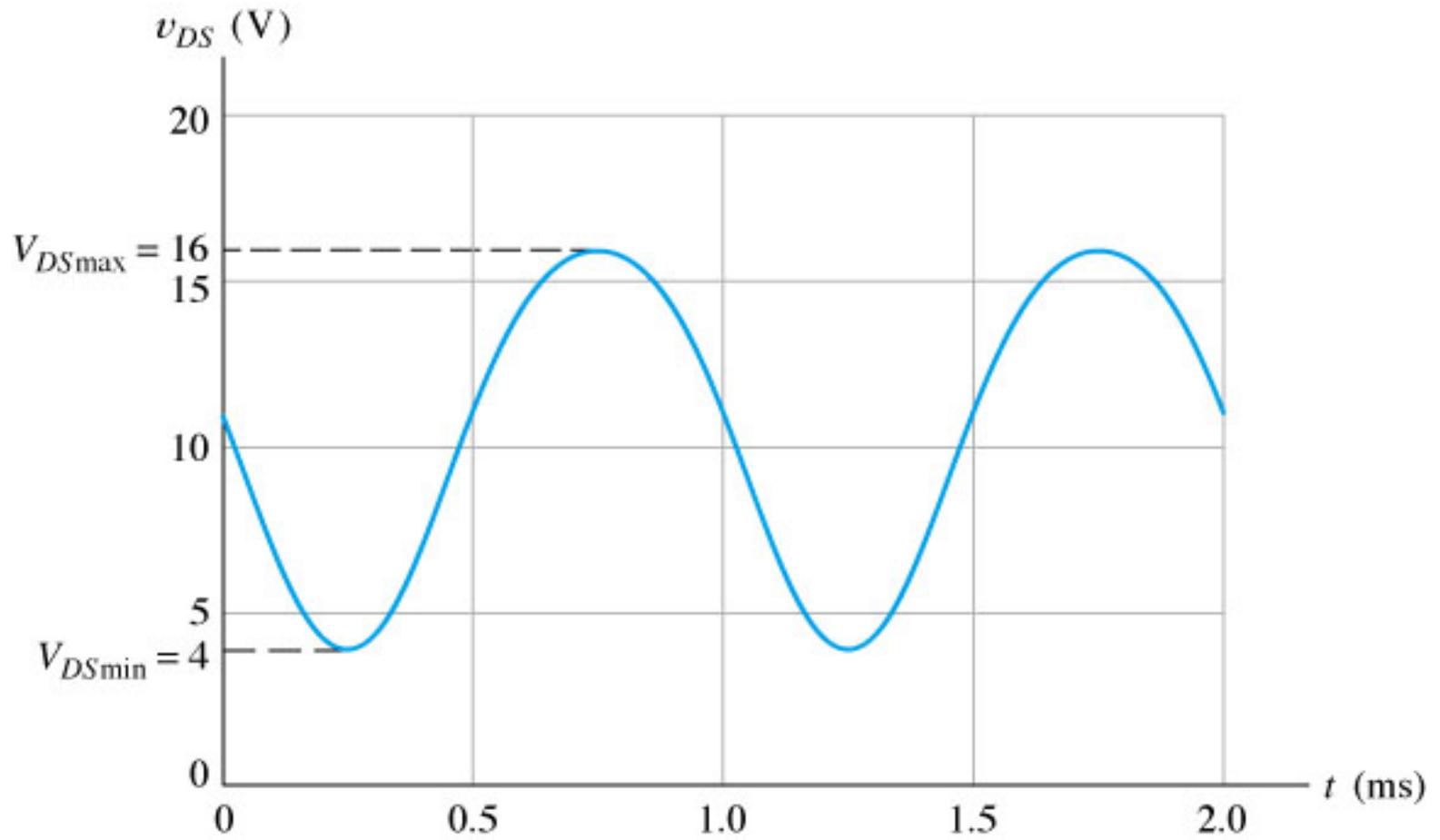


Figure v_{DS} versus time for the circuit of Figure 5.13.

DEPLETION MOSFET

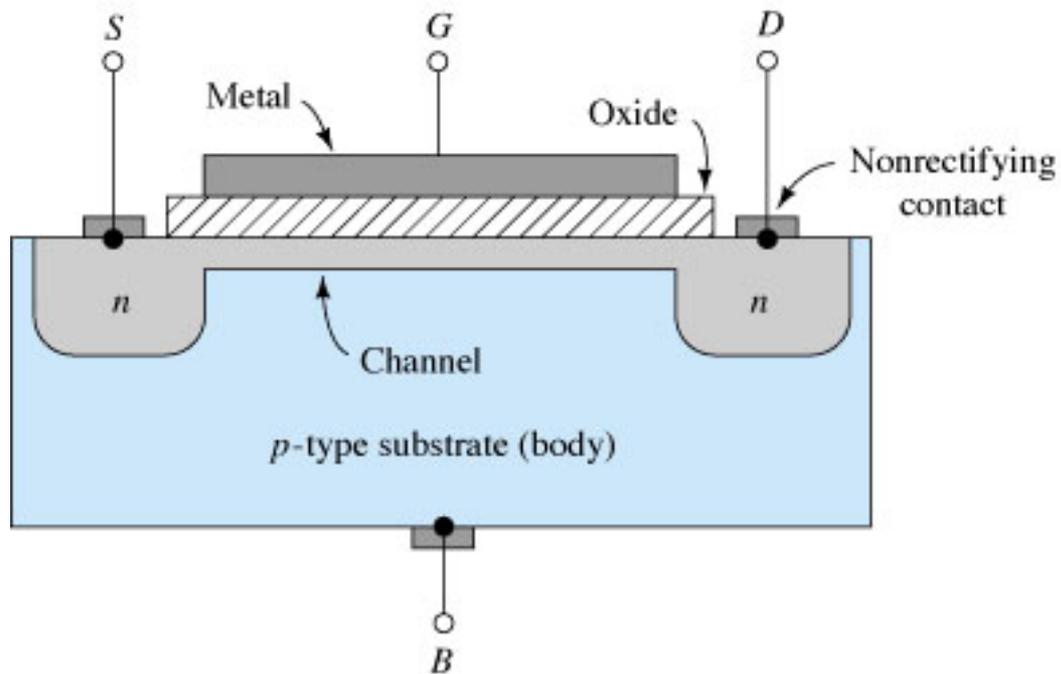

(a) Physical structure

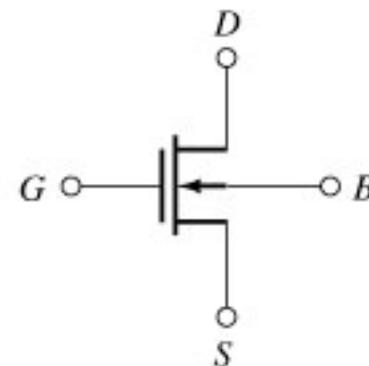

(b) Circuit symbol

Figure n -Channel depletion MOSFET.

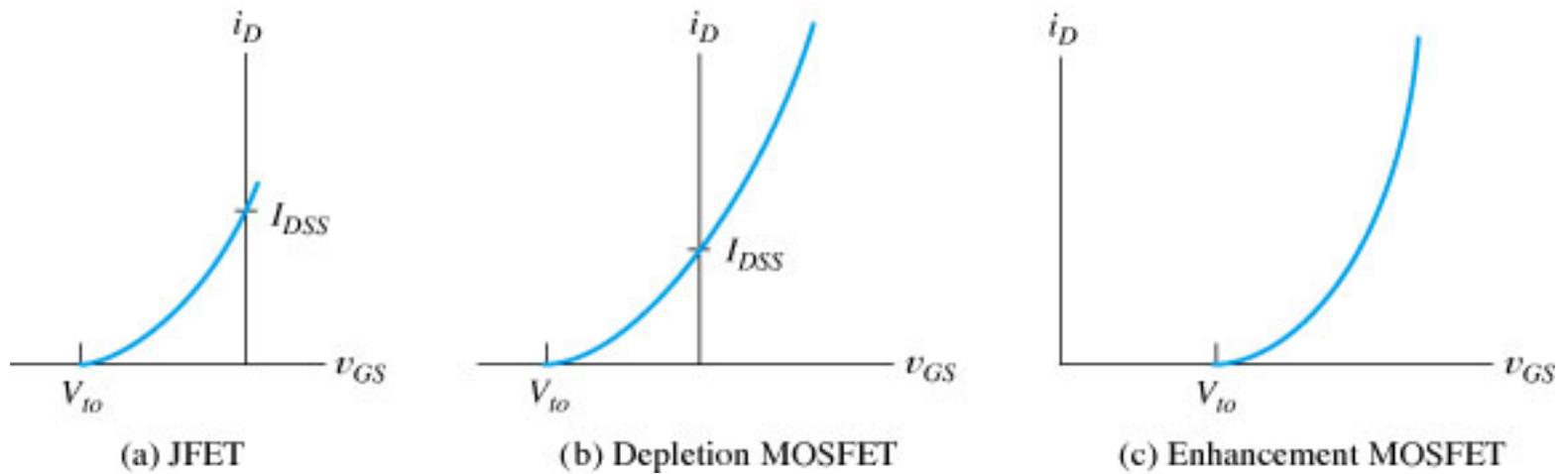


Figure Drain current versus v_{GS} in the saturation region for n -channel devices.