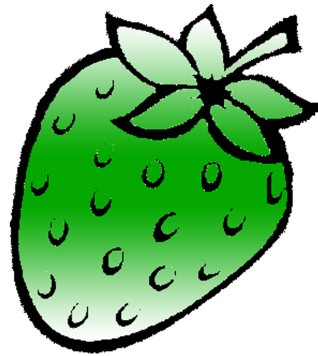


# STRAWBERRY



 /strawberrydevelopers

 /strawberry\_app

*For more visit:*

*Strawberrydevelopers.weebly.com*


# Unit 5

## Silicon Controlled Rectifier

# Contents


- Construction
- Working
- Characteristic
- Two transistor Analogy
- Controlled Rectifier

# SCR

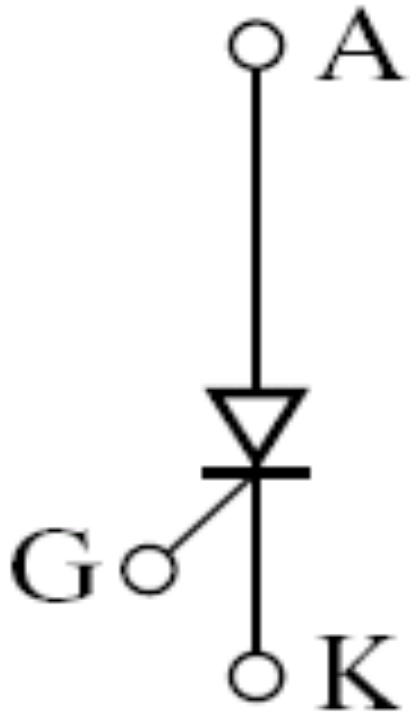

Symbol of  
Silicon Controlled Rectifier

# Device Operation

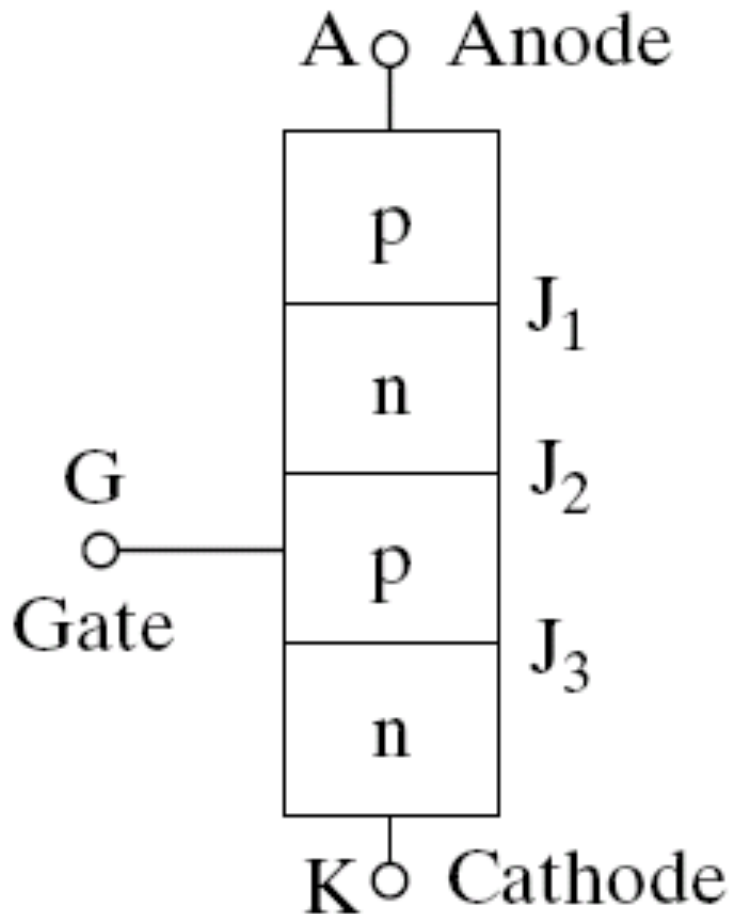

Simplified model of a  
thyristor

# Working

- Forward Blocking State (OFF state)

SCR is Forward Biased, i.e. anode is positive w.r.t cathode  $V_{AK} < V_{BO}$


- Forward Conduction State (ON state)

SCR is Forward Biased, i.e. anode is positive w.r.t cathode  $V_{AK} > V_{BO}$

- Reverse Blocking State (OFF state)

SCR is reverse biased, cathode is Positive w.r.t anode

# V-I Characteristics

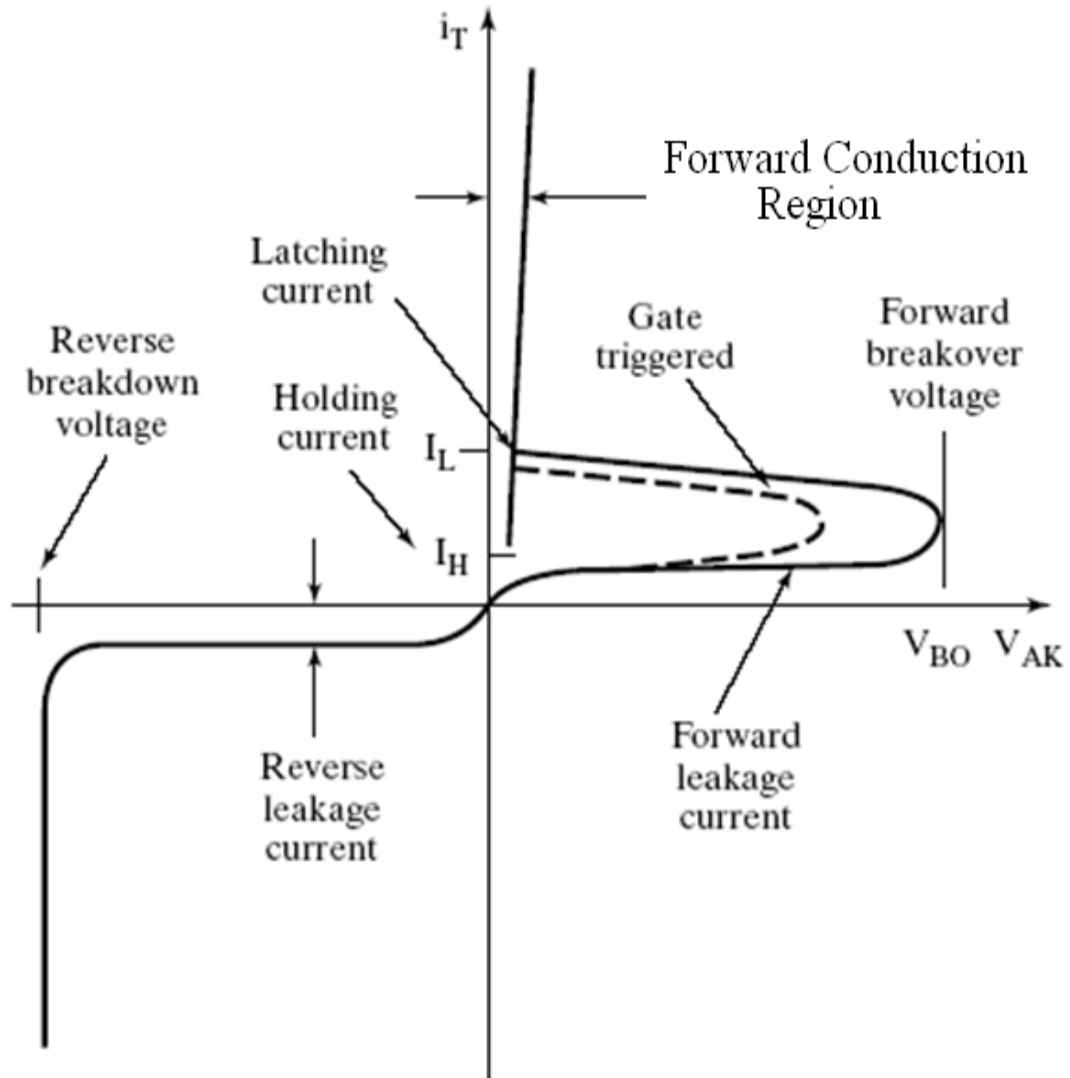


# Effect of Gate Signal

- Thyristor turns on before  $V_{BO}$ .
- The forward voltage  $V_{AK}$  at which the thyristor turns ON depends on the gate current magnitude.
- Higher the gate current , lower is the forward breakover voltage  $V_{BO}$  .



# Effects of gate current

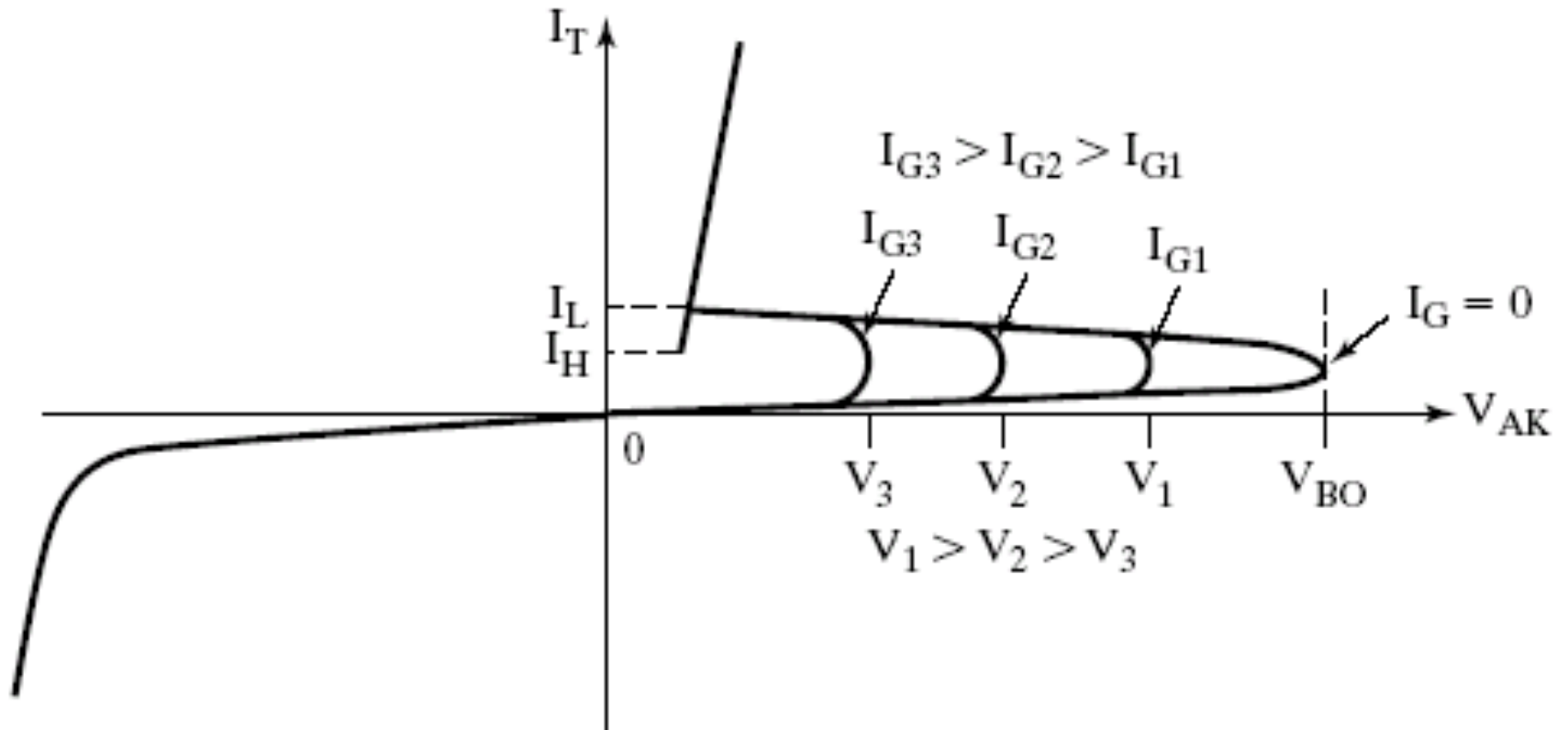


# Latching Current



- Latching current is the minimum anode current that must flow through the SCR in order to latch it into ON state.
- Once  $I_a > I_{latch}$  the SCR does not turn OFF even if the gate signal is removed.

# Holding Current

- Holding current  $I_h$  is the minimum anode current that must flow through the SCR in order to 'hold' it in ON state.
- Once SCR is on, it will go into OFF state only if the anode current falls below the minimum level called the HOLDING CURRENT ( $I_h$ )

# Two Transistor Model of SCR

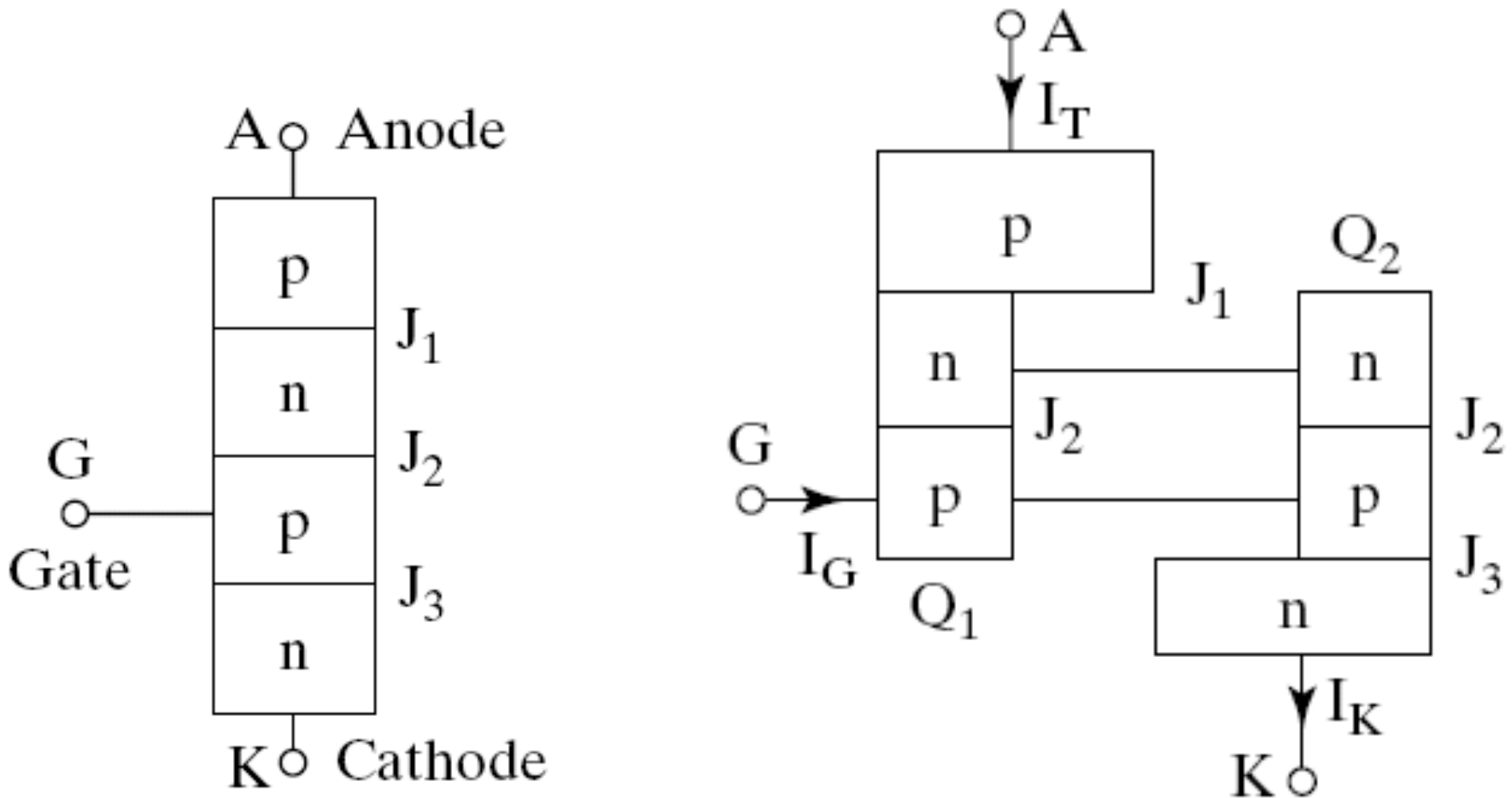

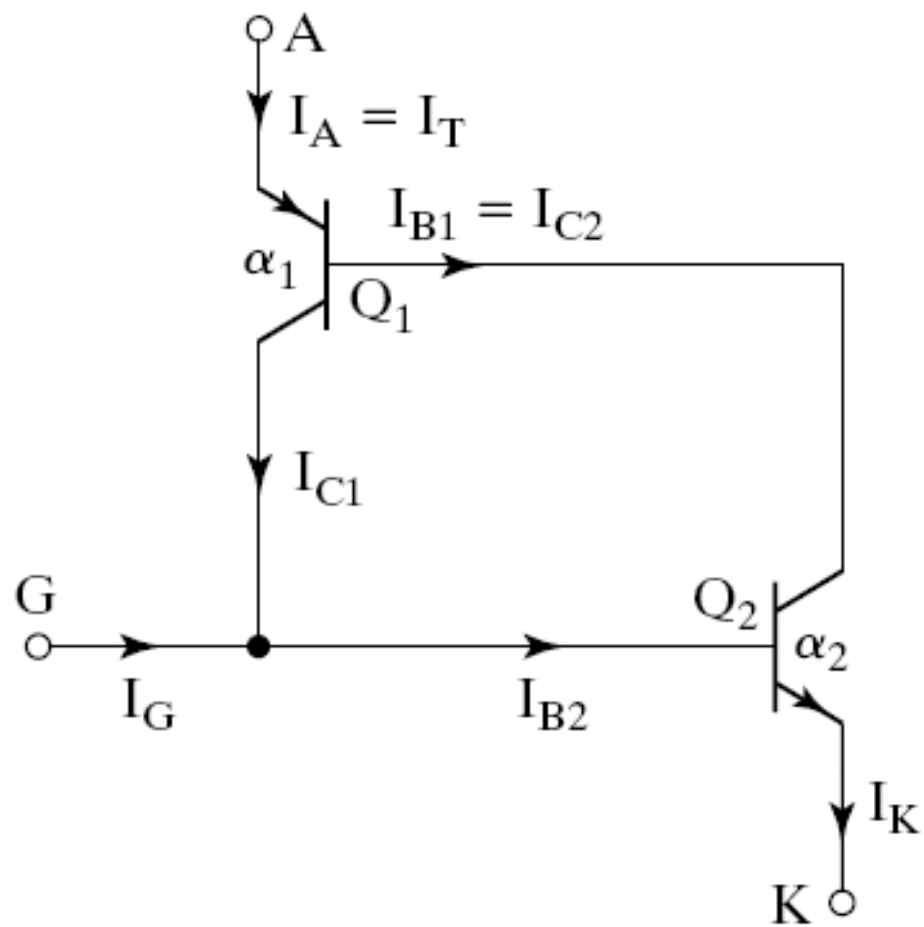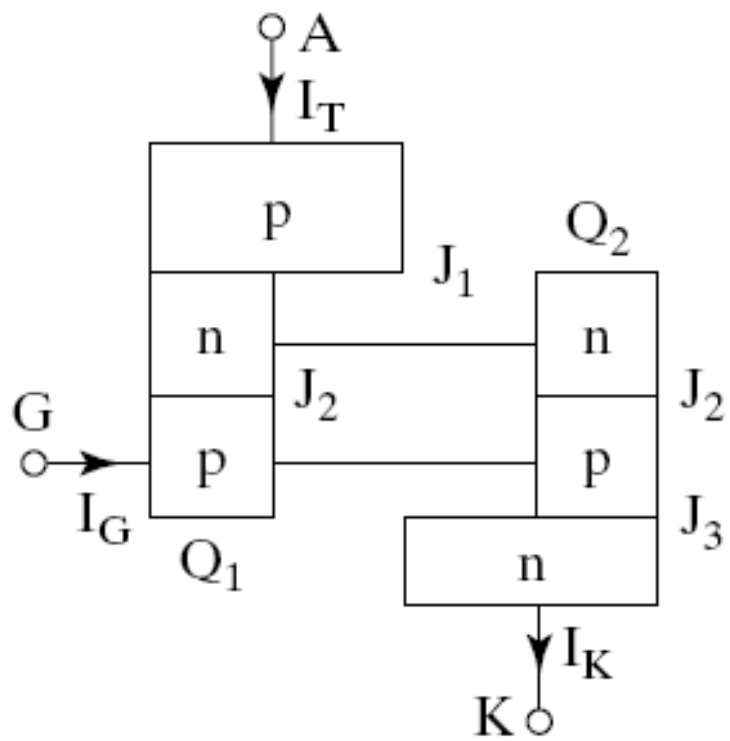

## Derivation of anode current equation

$$I_A = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$

The general transistor equations are,


$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$I_B = I_E (1 - \alpha) - I_{CBO}$$
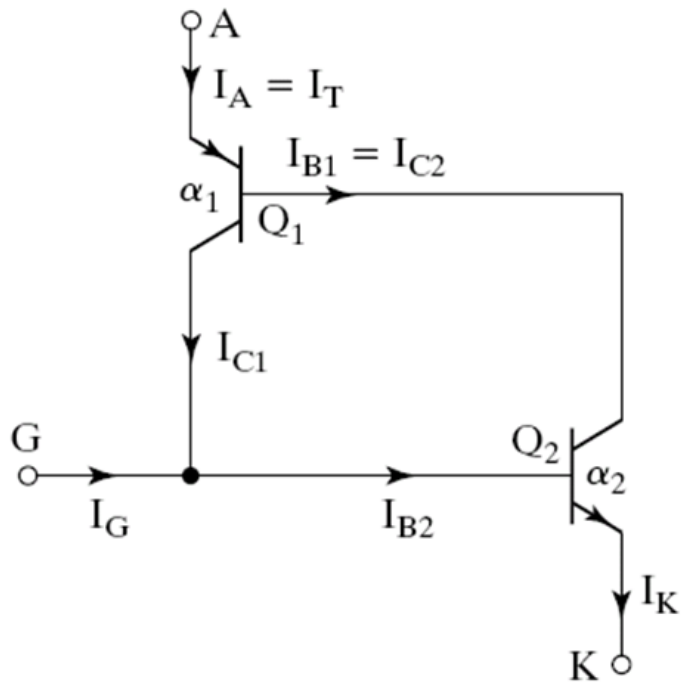
# Applying the Eqns to the Transistor analogy



We have the following relations for T1 and T2


$$I_{C1} = \alpha_1 I_{E1} + I_{CO1} \quad \text{--- (1)}$$

$$I_{C2} = \alpha_2 I_{E2} + I_{CO2} \quad \text{--- (2)}$$

where  $\alpha_1, \alpha_2$  are the common base current gain

$I_{CO1}, I_{CO2}$  are the reverse leakage currents of

the reverse biased  $J^1 J_2$

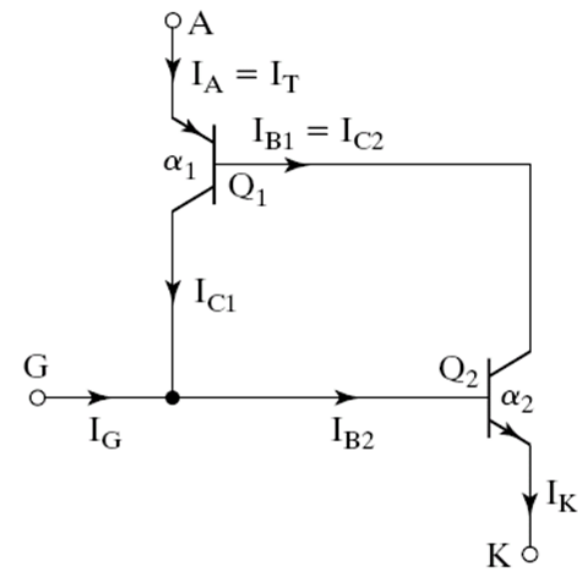

For Tx.  $T_1 \rightarrow I_{b1} = I_{e1} - I_{c1}$

$$\text{Sub. } I_{c1} = \alpha_1 I_{e1} + I_{co1}$$


$$I_{b1} = I_{e1} - \alpha_1 I_{e1} - I_{co1}$$

$$I_{b1} = (1 - \alpha_1) I_{e1} - I_{co1} \text{ ——— (A)}$$

From fig. (a)  $I_a = I_{e1}$
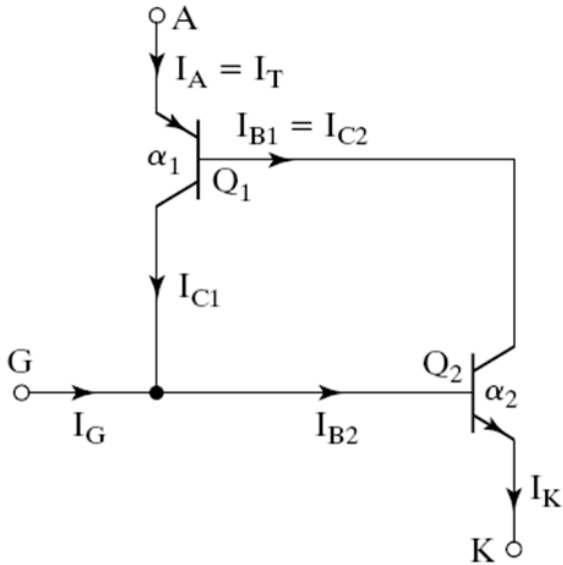
$$\therefore I_{b1} = (1 - \alpha_1) I_a - I_{co1}$$





For  $T_1, T_2 \rightarrow I_{C2} = \alpha_2 I_{E2} + I_{CO2}$

From fig. (a)  $I_{E2} = I_K$ .

$\therefore I_{C2} = \alpha_2 I_K + I_{CO2}$  — (B)

Since  $I_{B1} = I_{C2}$

Equating eqn A and B we get

$(1 - \alpha_1) I_a - I_{CO1} = \alpha_2 I_K + I_{CO2}$  — (C)

From Fig it is seen that

$I_K = I_a + I_g$  sub, in eqn C

$(1 - \alpha_1) I_a - I_{CO1} = \alpha_2 (I_a + I_g) + I_{CO2}$

$(1 - \alpha_1 - \alpha_2) I_a = \alpha_2 I_g + I_{CO1} + I_{CO2}$

$$[1 - (\alpha_1 + \alpha_2)] I_a = \alpha_2 I_g + I_{c01} + I_{c02}$$

$$I_a = \frac{\alpha_2 I_g + I_{c01} + I_{c02}}{[1 - (\alpha_1 + \alpha_2)]}$$

Assuming the leakage currents of T1 and T2 are negligible

$$I_a = \frac{\alpha_2 I_g}{1 - (\alpha_1 + \alpha_2)}$$

# Significance of the anode current eqn.

$$I_a = \frac{\alpha_2 I_g}{1 - (\alpha_1 + \alpha_2)}$$

- Turn ON condition of SCR  
(Regenerative action)

$$\{(\alpha_1 + \alpha_2) \geq 1\}$$

- As long as  $(\alpha_1 + \alpha_2) < 1$ , that is the current gains of both the transistors are small, anode current remains quite low ( $\mu\text{A}$ ) and SCR is in BLOCKING STATE
- When  $(\alpha_1 + \alpha_2) \geq 1$ , REGENERATIVE ACTION begins and device goes from OFF to ON state.

- This turn on condition of SCR

i.e.  $\{\alpha_1 + \alpha_2 \geq 1\}$ .

can be satisfied by the following ways

1. By raising temperature (Thermal triggering)
2. By applying high voltage (forward voltage triggering)
3. By increasing the gate current

# The Controlled Rectifier

- The controlled rectifier is the converter that changes the constant ac input to variable dc output.
- The ac input may be a single or three-phase supply
- Some rectifiers are based on semi controlled switching devices (mainly SCRs) others are based on fully controlled switching devices

# Controlled Rectifier Applications

Using controlled rectifiers is the basic way to obtain variable voltage dc supply, which has many practical applications, such as:

- To supply variable speed dc motors
- For high voltage DC transmission systems
- Battery chargers
- Other applications require controlled current:  
e.g. electric arc welding


# Single Phase Full Wave Controlled Rectifier

Rectification: is a process of converting AC to DC .

1. Uncontrolled Rectifier: uses only diodes and the dc output is fixed in amplitude by the amplitude of the AC supply.
2. Fully Controlled Rectifiers: There use thyristors as rectifying elements and the dc output voltage is a function of
  - The amplitude of the AC voltage applied
  - Output Voltage can be adjusted depending on the point of the AC input voltage at which the thyristor is triggered ( $\alpha$ )
3. Half Controlled Rectifiers: There use thyristors and diodes as rectifying elements and allow a more limited control over the dc o/p voltage level.


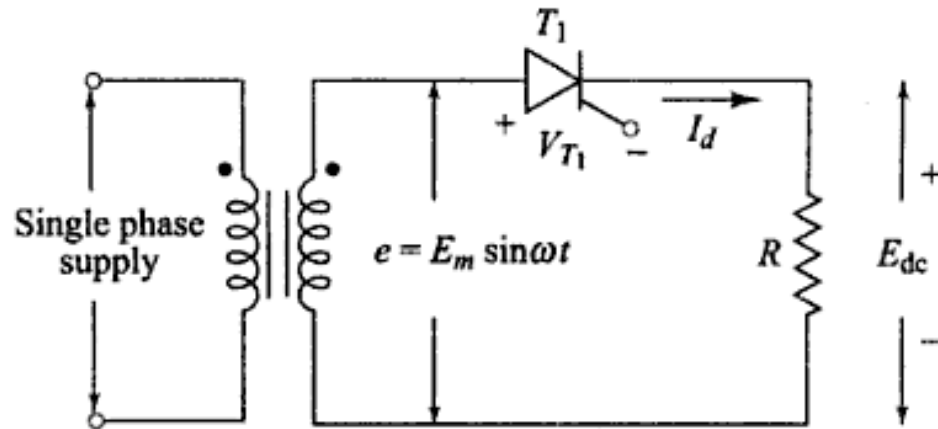
# Single Phase Half Wave Controlled Rectifier

Half Wave Controlled Rectifier with Resistive Load





# Waveforms for a half-wave circuit

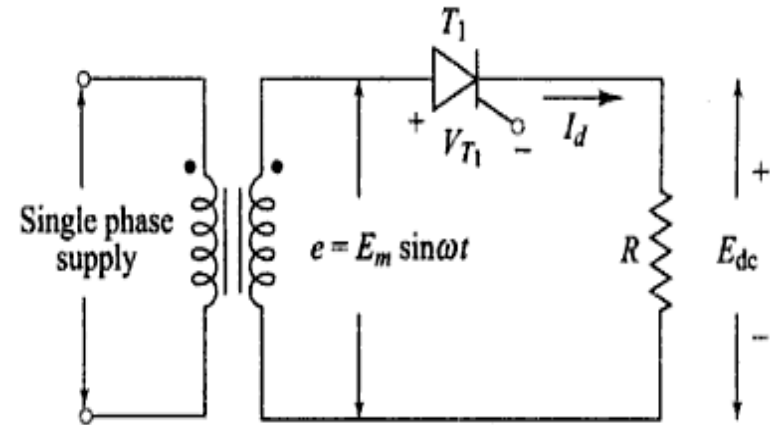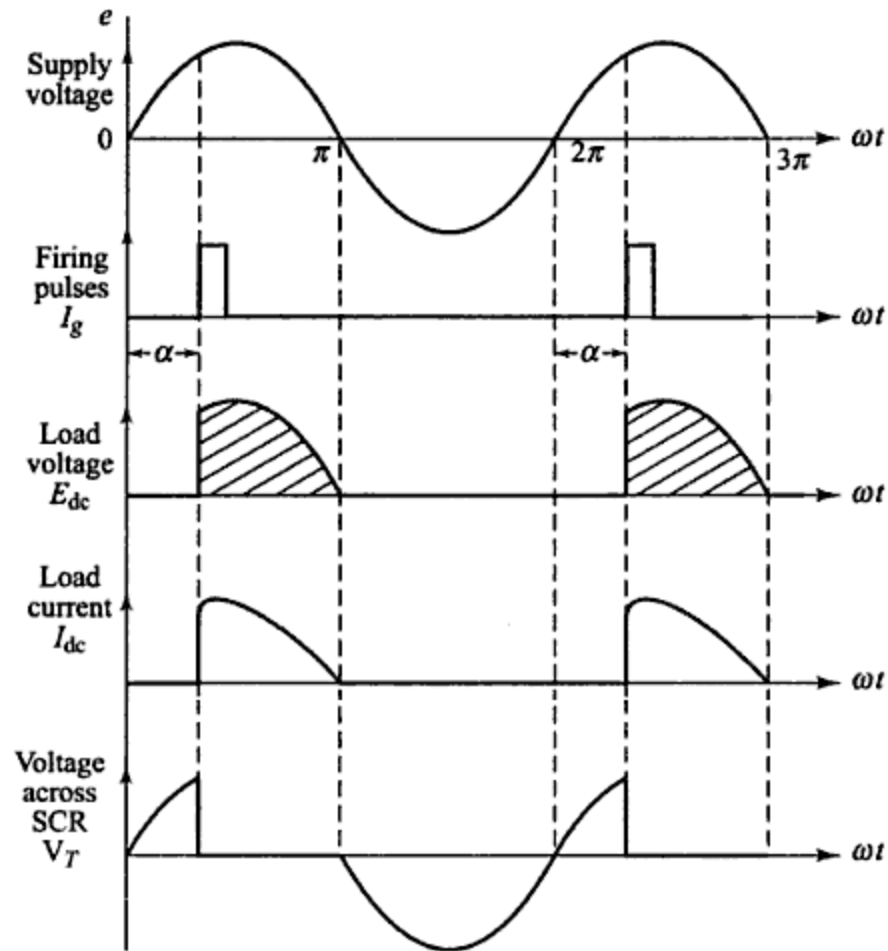

# Voltage and Current Relations

## **(a) Average Load Voltage**

$$E_{\text{dc}} = \frac{E_m}{2\pi} [1 + \cos \alpha].$$

where  $E_m$  is the peak value of the a.c. input voltage

The maximum output voltage is obtained when  $\alpha = 0$ .

$$E_{\text{dcmax}} = \frac{E_m}{\pi}$$

(b) **Average load current** With resistive load, the average load current is directly proportional to the average load voltage divided by the load resistance:

$$\therefore I_d = \frac{E_m}{2\pi R} [1 + \cos \alpha]$$

(c) **RMS load voltage** The RMS load voltage for a given firing angle  $\alpha$  is given by

$$E_{\text{rms}} = E_m \left[ \frac{\pi - \alpha}{4\pi} + \frac{\sin 2\alpha}{8\pi} \right]^{1/2}$$

$$\text{For firing angle } \alpha = 0, E_{\text{rms}} = \frac{E_m}{2}$$

# Equations to be remembered

**Average Load Voltage**  $E_{dc} = \frac{E_m}{2\pi} [1 + \cos \alpha].$

**Average load current**  $I_d = \frac{E_m}{2\pi R} [1 + \cos \alpha]$

**RMS load voltage**  $E_{rms} = E_m \left[ \frac{\pi - \alpha}{4\pi} + \frac{\sin 2\alpha}{8\pi} \right]^{1/2}$

# Single Phase Full Wave Controlled Rectifier


There are two basic configurations of full wave controlled rectifiers.

(1) Midpoint Converters

(2) Bridge Converters


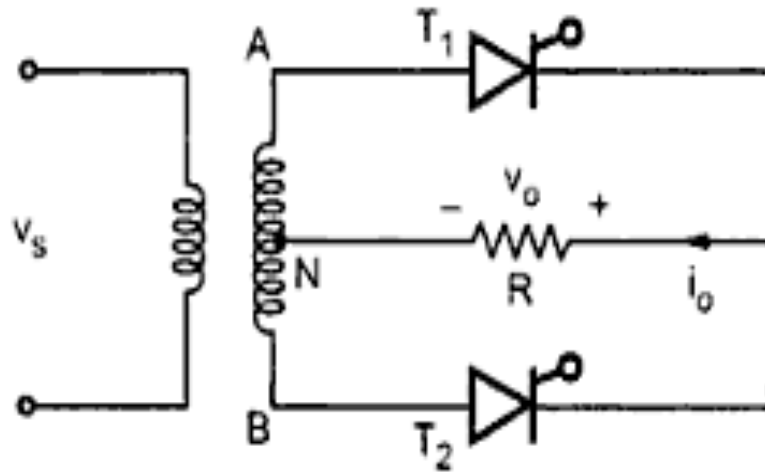
# Full Wave Midpoint Converter (M-2 Converter)

The full wave converter rectifies both, positive as well as negative half cycles of the supply.



**Circuit diagram of full wave mid point converter**

# Waveforms

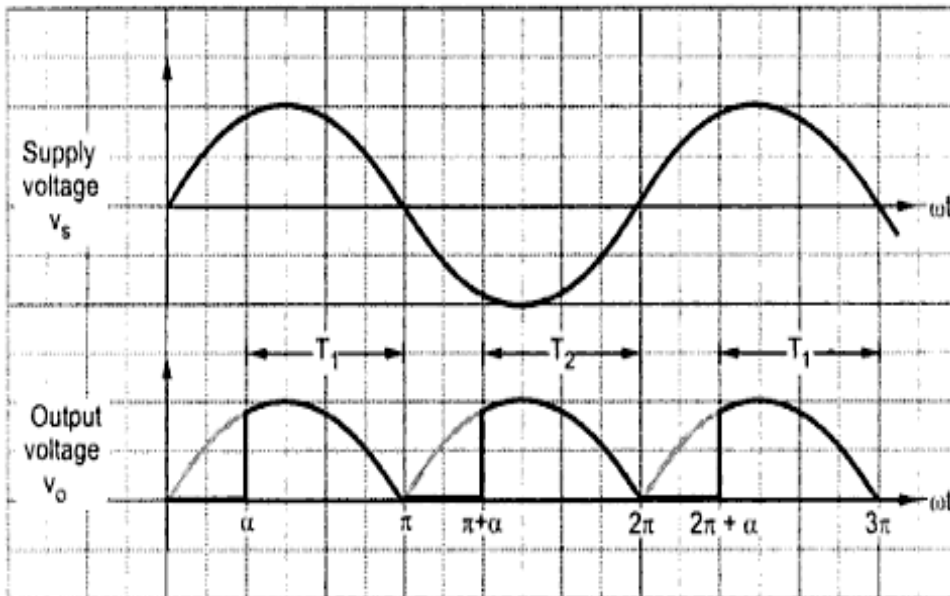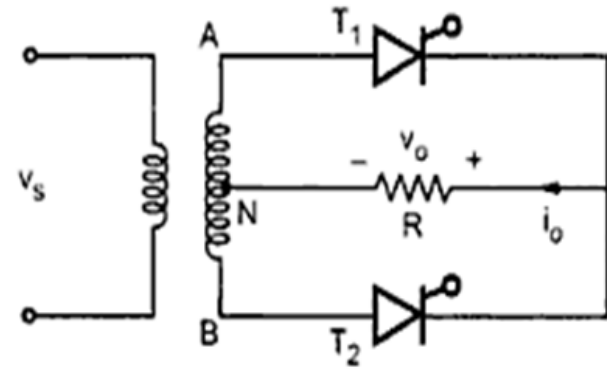

# Mathematical Analysis



**Average Load Voltage**  $E_{dc} = \frac{E_m}{\pi} [1 + \cos \alpha]$ .

**Average load current**  $I_d = \frac{E_m}{\pi R} [1 + \cos \alpha]$

**RMS load voltage**  $E_{rms} = E_m \left[ \frac{\pi - \alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right]^{1/2}$


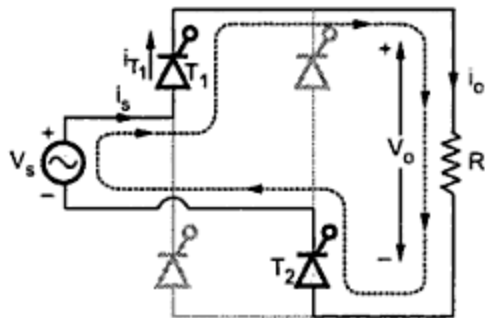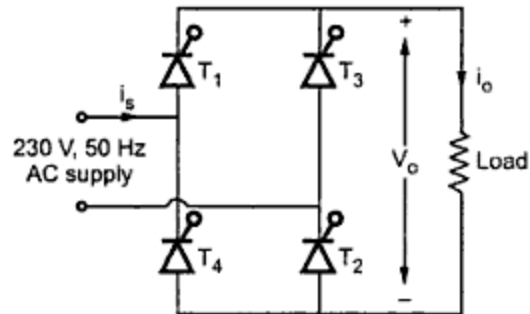
# Fully Controlled Bridge Rectifier with Resistive Load



Conduction of  $T_1$  and  $T_2$  in positive half cycle of the supply.  
Dotted line shows path of current flow

Supply Voltage

Trigger Signal for  $T_1$  and  $T_2$

Trigger Signal for  $T_3$  and  $T_4$

Output Voltage

Output Current

